

Problem HH8.8

Using logic gates, show how to make:

- a) An inverter from a NOR gate
- b) An OR gate from NOR gates
- c) An OR gate from NAND gates