

Field Effect Transistors and Op Amps I

The Field Effect Transistor

This lab begins with some experiments on a junction field effect transistor (JFET), type 2N5458, and then continues with an op amp chip from the TL081/082/084 family. Details of these devices, including pin-out, can be found on the data sheets in the supplementary reading section on your web page. Items marked with an asterisk (*) should be done before coming to lab.

1. Pinch-off bias

Set up the circuit below. Use the LabView program `c:\Phy440\NewJFET.vi` to measure the drain current I_D as a function of the Gate-Source voltage V_{GS} . Instructions on wire connections between the protoboard and the LabView circuitry can be found by following the selections within the program: File → VI Properties. Open the window “Documentation.” Remember that the variable gate voltage is negative and you should keep it within the range of $-5V$ to $0V$.

You should find that the drain current decreases with increasingly negative gate voltage until a point where it is essentially zero. This is the so-called pinch-off voltage. (a) Compare your answer for the pinch-off voltage with the rather liberal limits given on the data page for “Gate-Source Cutoff Voltage”. [3 p]

 


Figure 1: FET Circuit.

2. Common-source transfer characteristics


The program measures the current by measuring the voltage drop across the $1k\Omega$ drain resistor.

- Make a copy of the computer plot of drain current vs. gate-source voltage and paste it into your notebook. [3 p]
- Compare your plot to the one in the data sheet. Are the plots similar? Does your plot have the right curvature? [3 p]

 (c) The plot should have the form:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$


where I_D is the drain current, V_{GS} is the gate-source voltage, and I_{DSS} is the drain current at $V_{GS}=0$ V. From your plot determine the parameters I_{DSS} and V_P . [3 p]



3. Common-source JFET amplifier

Using the same transistor, build the circuit in Fig. 3 with a power supply for V_{DD} and a signal generator for the variable input voltages, as shown in Figure 3. For a good operating point, the drain voltage should be between 3 V and 7 V. Measure the quiescent drain voltage for your circuit. (The AC signal on the input is not relevant for quiescent conditions and may be disconnected for this part.) If your V_D is outside the above range, swap the resistor R_S from 1k to a different value, in order to get V_D within the desired range.

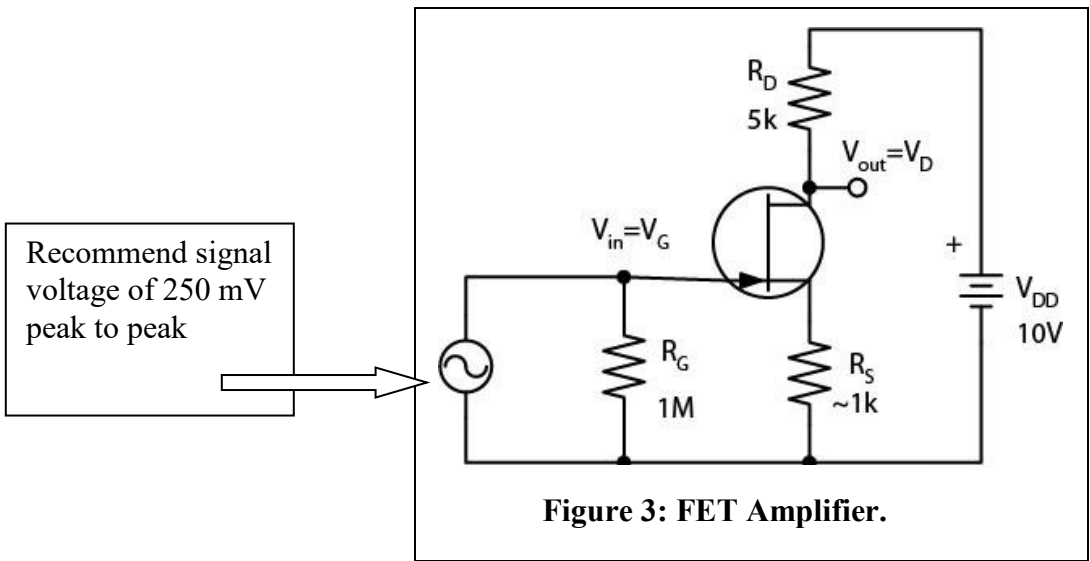(a) What is your final V_D ? What is your quiescent drain current now? [3 p]



The circuit above is an AC amplifier. The output signal at the drain will be larger than the input signal on the gate.

(b)*Explain why this is an inverting amplifier. [3 p]

(c) The gain of the amplifier depends upon the transconductance g_m . From your earlier measurements determine the value of $g_m = \Delta I_D / \Delta V_{GS}$ at your operating point. The units of this parameter are mhos (reciprocal ohms) or siemens (S). [3 p]

(d) *The gain is defined as $A_V = \Delta V_{out} / \Delta V_{in}$


Show that:
$$A_V = -\frac{g_m R_D}{1 + g_m R_S}$$

and therefore that you expect a gain of about 2.5, if $g_m = 1 \times 10^{-3}$ mhos, $R_D = 5k\Omega$ and $R_S = 1k\Omega$. [3 p]

 
(e) Measure the gain of your amplifier circuit and compare with the expectation. Can you confirm that the amplifier is inverting? [3 p]

Op Amps I

Build the circuits below using a TL082 dual op-amp chip. Each chip contains two amplifiers. Pin number 1 is probably indicated with a dimple on the chip case. You will need to use only one of those amplifiers within a chip in this lab. Remember to connect ± 15 volt supplies to the chip. Make sure that the grounds indicated for the circuits combine your power supply ground (0V) with the generator and DPO grounds.




4. The voltage follower

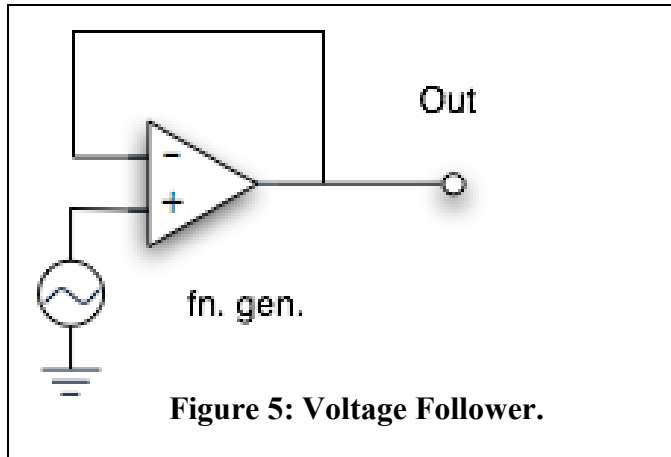


- (a) Use an oscilloscope to compare the input and output. Are they the same? Include a copy of the DPO output showing input and output wave forms. [4 p]
- (b) Make the input at zero volts by grounding it. Use a DMM to discover whether the output is precisely zero volts. Possibly the output will be at a few millivolts. That represents an offset within the op amp. [3 p]

5. The non-inverting amp

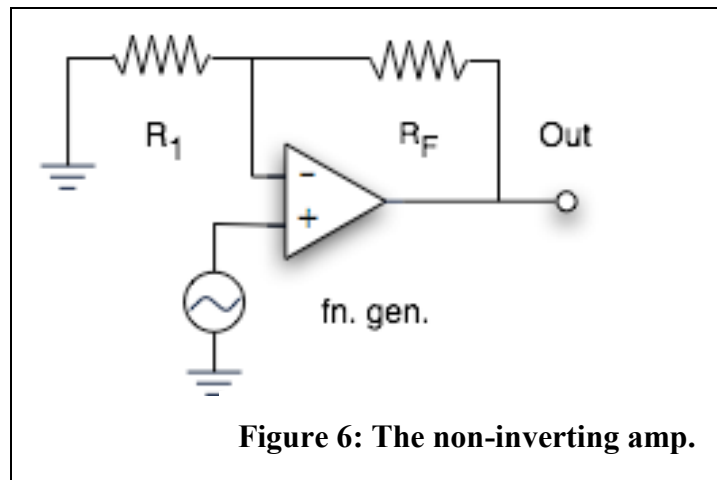

- (a) *Show mathematically that you expect the gain to be given by $1 + R_F/R_1$. Measure the gain to verify this using resistor values in the range 3K to 200K. Paste a copy of an example DPO screen in your notebook. [4 p]

6. The inverting amp

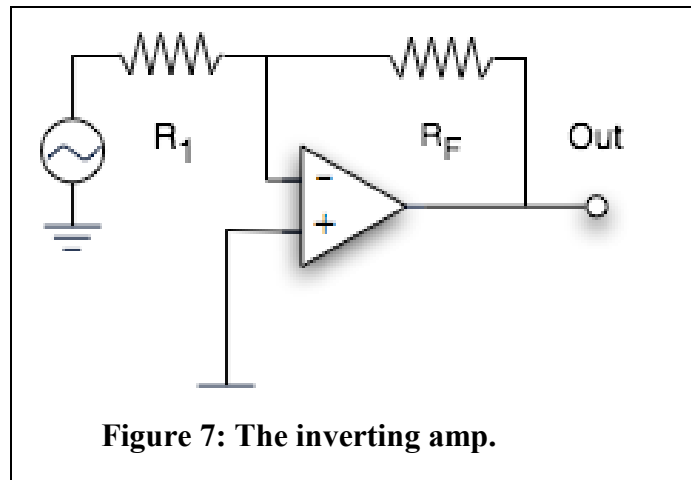

- (a) *Show mathematically that you expect the gain to be given by $-R_F/R_1$. Measure the gain to verify this using resistor values in the range 3K to 200K. Place a copy of a screen output in your notebook. [4 p]
- (b) Replace one of the fixed resistors by a trimmer potentiometer. Can you vary the gain of the amplifier using this control? [3 p]