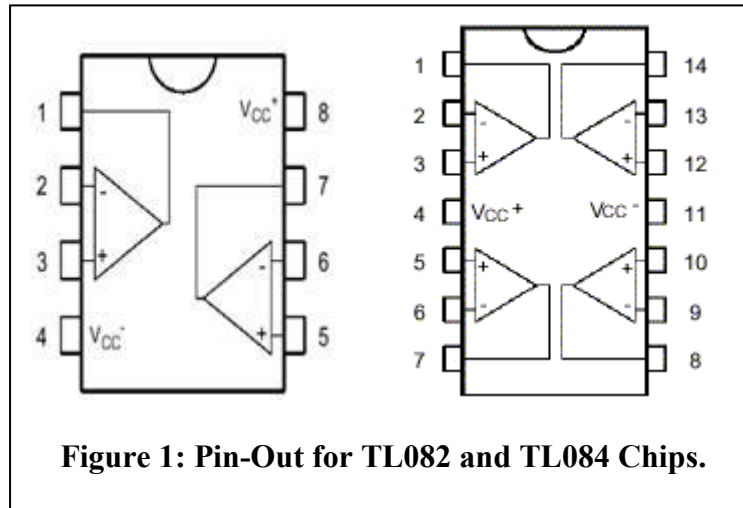



## Lab 9 Op Amps II

Questions indicated by an asterisk (\*) should be answered before coming to lab. In this lab you will be using TL082/TL084 op-amp chips. Remember to provide -15V ( $V_{CC-}$ ) and +15V ( $V_{CC+}$ ) power voltage to the chips.



It will be up to you to decide what specific resistor and capacitor values to use in the circuits.

### 1. Op-Amp Relaxation Oscillator

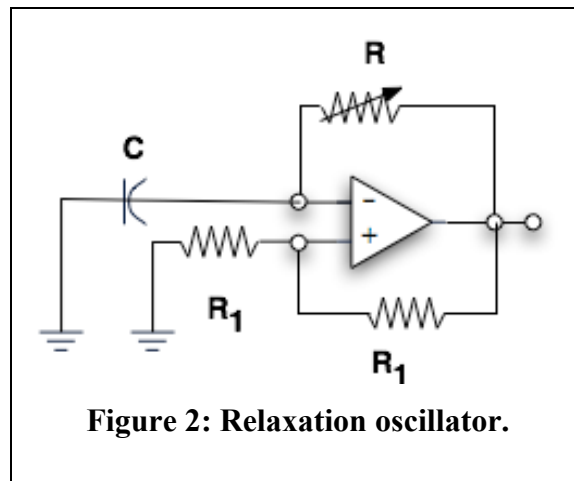

Build the relaxation oscillator shown in Figure 2 above. The output should be a square wave with a frequency  $f$  of about  $1/(2RC)$ . Resistor  $R_1$  can be any value between  $1k\Omega$  and  $1M\Omega$ . Resistor  $R$  is one side of a potentiometer.


(a) Indicate the values of the components you are using on a drawing in your notebook and compute the expected output frequency for  $x=0.5$ . [3 p]

(b) Connect an oscilloscope to display  $V_+$  and  $V_-$  and the output signal simultaneously on the same scale, to illustrate that the switching occurs at the crossover of  $V_+$  and  $V_-$ . Paste a plot of the 'scope display in your lab notebook. [4 p]

- (c) Determine the frequency range of your oscillator [4 p]  
 (d) \* How does this circuit work? Why does  $V_o$  resemble a triangular wave? [4 p]  
 (e) To make a musically useful signal, change the pot to a fixed resistor to get a frequency between 200 and 500 Hz. Record the value of the fixed resistor and the frequency. [3 p]  
 (f) **Do not** disassemble your circuit. You can have fun with it in Part 4 that follows.

## 2. Low-Pass Resonant Filter

This filter is made from a summer and three one-pole lowpass filters. All three filters have the same  $R$  and  $C$ .

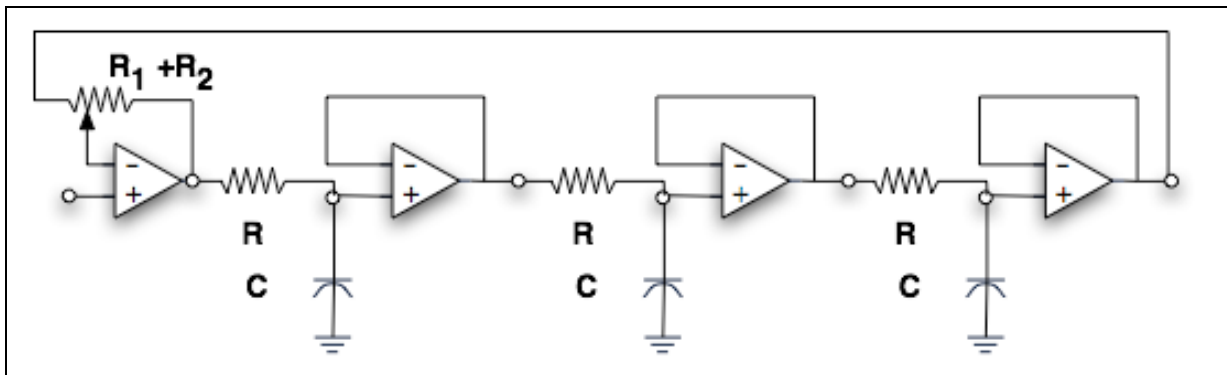

**Figure 3: Low-pass resonant filter.**

\*(a) Show that the transfer function for the low-pass resonant filter, shown in Figure 3, is given by:

$$H(\omega) = \frac{1}{1 - x + x(1 + j\omega\tau)^3} \quad (1)$$


where  $\omega$  refers to the angular frequency of an oscillator connected to the non-inverting input of the first (leftmost) op amp,  $\tau = RC$ , and  $x$  is the ratio of  $R_1$  to the total pot resistance  $R_1 + R_2$ . Here  $R_1$  is the part of the pot resistance between the filter main output (output of the final op-amp stage) and the sliding contact on the pot. The sliding contact is connected to the inverting input of the first op amp. Here  $R_2$  is the part of the pot resistance between the sliding contact and output of the first op amp. [5 p].

[Hint: Begin by naming the output voltages of each op amp, from left to right, as  $v_1$  through  $v_4$ . Then use the infinite gain assumption to show that:

$$\frac{(v_4 - v_m)}{R_1} = \frac{(v_m - v_1)}{R_2} \quad (2)$$

Next, use what you know about RC filters to find  $v_4$  in terms of  $v_1$ .]

The resonance depends on both  $x = \frac{R_1}{R_1 + R_2}$  and  $\omega\tau = \omega RC$ . Figure 4 shows the gain versus  $\omega\tau$  for four different values of  $x$ . It can be shown (you do not have to do this) that the real part of the denominator of Equation 1 vanishes when  $3x(\omega\tau)^2 = 1$ . That is the resonance condition. Furthermore, the gain is sharply peaked when  $\omega\tau = \sqrt{3}$  and  $x = \frac{1}{9}$ .

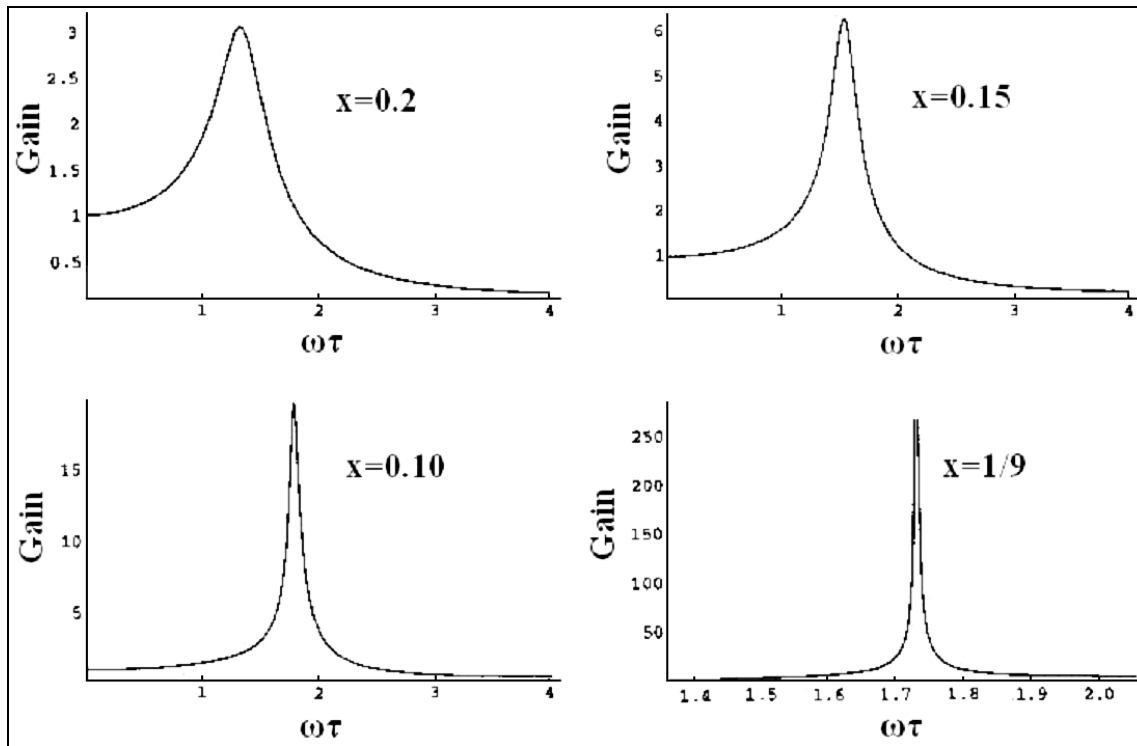

**Figure 4: Gain of the low-pass resonant filter for different resistance ratios.**

Note that parameter  $x$  controls both the resonant frequency and the  $Q$  of the filter. There are other filter circuits (e.g. the state variable filter) that afford independent control of the resonant frequency and the  $Q$ .

(b) When you understand the equation for the transfer function, build the circuit. It is convenient to use a TL084 with four op amps in a package, but you may also use two TL082 chips. Choose  $RC$  so that the resonant frequency is 2 to 5 kHz. (It is best to use a resistor  $\sim 5$  k $\Omega$ ). Begin by writing chip pin numbers on a hard copy of the circuit diagram. Examine the resonant behavior by feeding in a sine signal from a function generator. Specifically:

(1) Set the function generator to the  $x = \frac{1}{9}$  resonance frequency of  $f = \frac{\sqrt{3}}{2\pi RC}$ .

(2) Adjust the pot to maximize the output amplitude (now you should be close to  $x = \frac{1}{9}$ ).

Record the resonant frequency and the gain at resonance [4 p]

(3) Show your completed circuit to your instructor who will initial your drawing. [4 p]

(4) Find  $H(\omega)$  at the resonance frequency and for 5 higher frequencies and for 5 lower frequencies to make a Bode plot of the transfer function (magnitude in dB and phase vs base-10 log of  $f$ ). [4 p]

The Bode plot should show the character of the high-frequency roll off. To the extent that the theoretical transfer function is correct, the gain should be proportional to  $1/f^3$  at high  $f$ . Compare that power law with your Bode plot high-frequency limit. [3 p]

#### ***4. Filtering the square wave.***

Connect the output of the relaxation oscillator to the input of the filter using a voltage divider to reduce the oscillator output voltage by about a factor of 10..

- (a) What resistors are you using for the voltage divider? [2 p]
- (b) What does the filter do to the shape of the wave? [3 p]
- (c) Listen to your output and observe on the 'scope as you adjust the filter frequency. What do you hear? [2 p]