

Sketch the output waveforms expected when a 100Hz sine wave ($V_p=5V$) is applied to each of the following circuits:

