

T15

Using logic gates, design a 4-bit digital-to-analog converter that can produce voltages in the range 0V to 5V. (Hint: The highest output voltage that can be reached is actually below 5V.)