

Lecture 11

Chapter 26
Capacitance

Set #3, Problem #4


- Let $Q_1, Q_3 > 0$ and $Q_2 = -Q_1$ so

Q_1 is +

Q_3 is +

Q_2 is -

$$Q_1 = Q_2 = Q$$

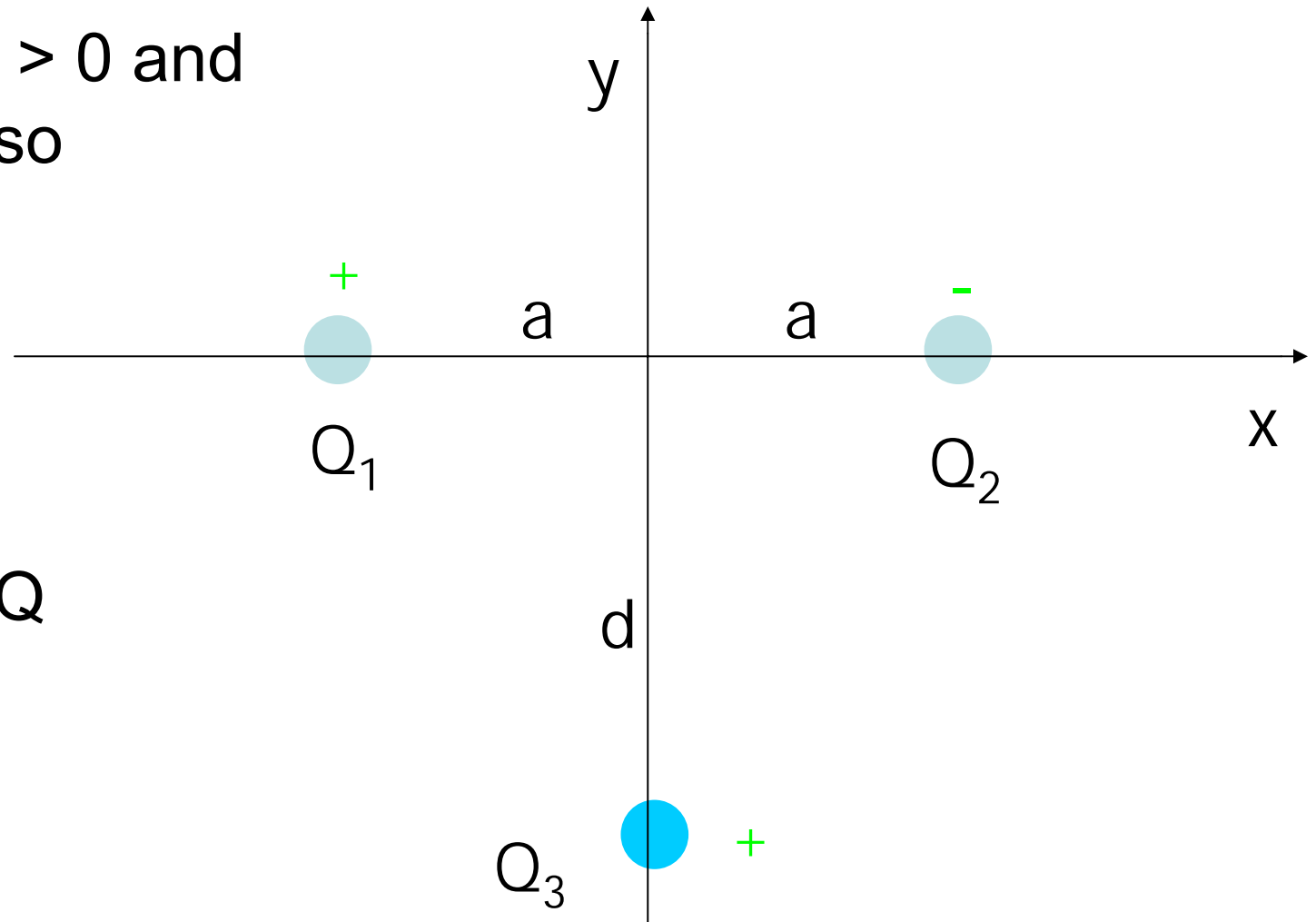

Set #3, Problem #4

True or false: V at $(0,0)$ is zero

FALS


E

$$V = \sum_1^n V = k(V_1 + V_2 + V_3)$$

$$V = k\left(\frac{Q_1}{a} + \frac{Q_2}{a} + \frac{Q_3}{d}\right) = k\left(\frac{Q}{a} - \frac{Q}{a} + \frac{Q_3}{d}\right)$$


$$V = k\left(\frac{Q_3}{d}\right)$$

V is + for any position along y-axis

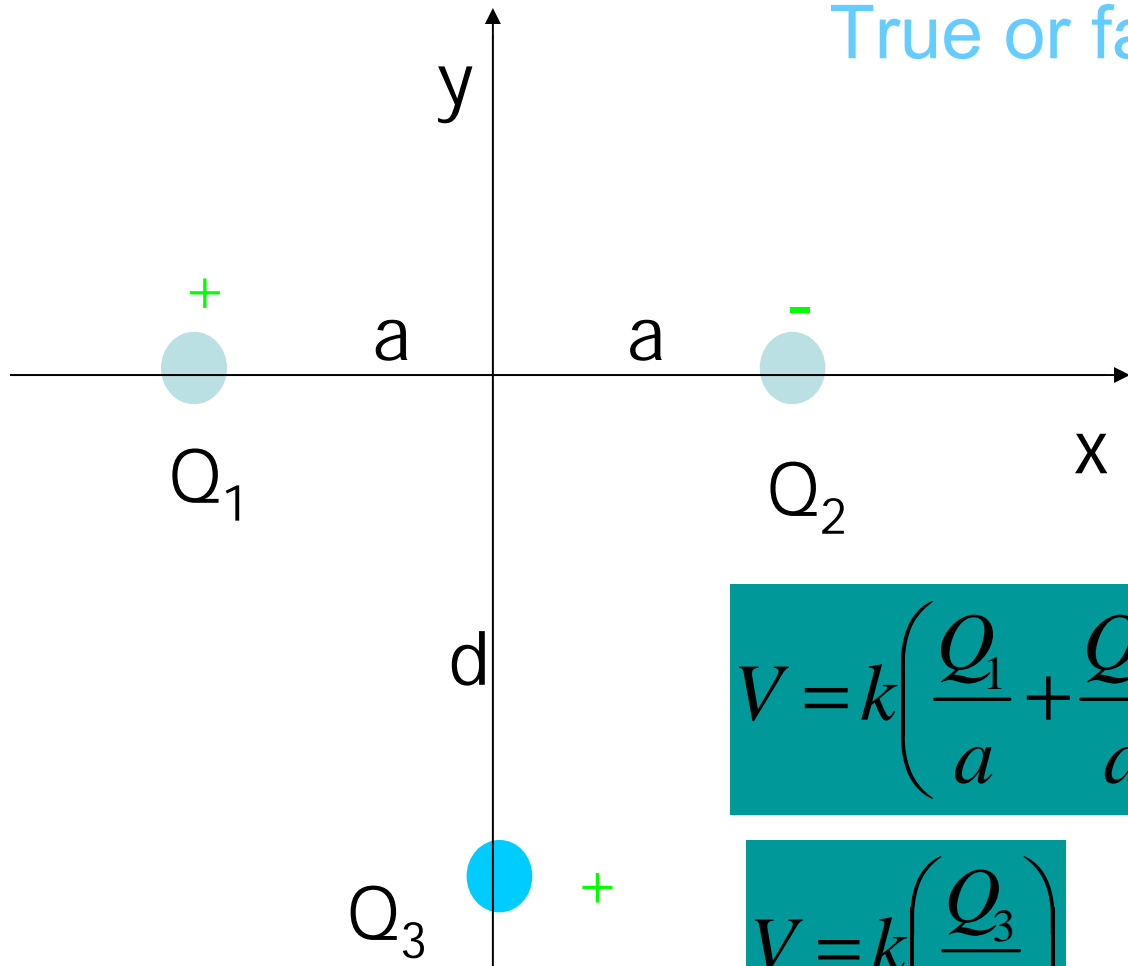

Set #3, Problem #4

Where does F point at Q_3 ?

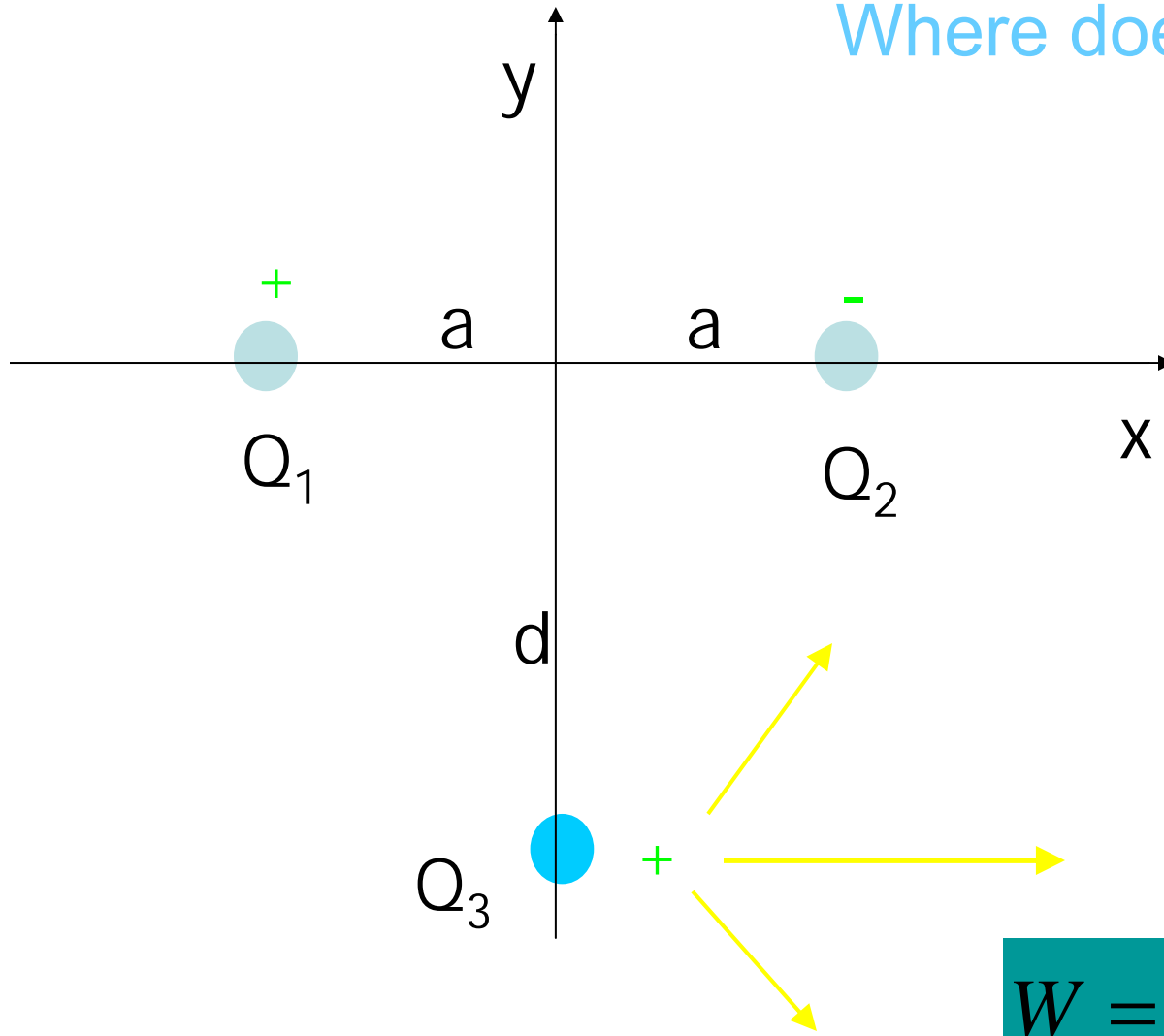

It is TRUE that:


Q_3 will accelerate to right

F_y on Q_3 due to other charges is zero

W to move Q_3 to origin is zero

$$W = \vec{F} \cdot \vec{d} = Fd \cos(90)$$

Set #3, Problem #4

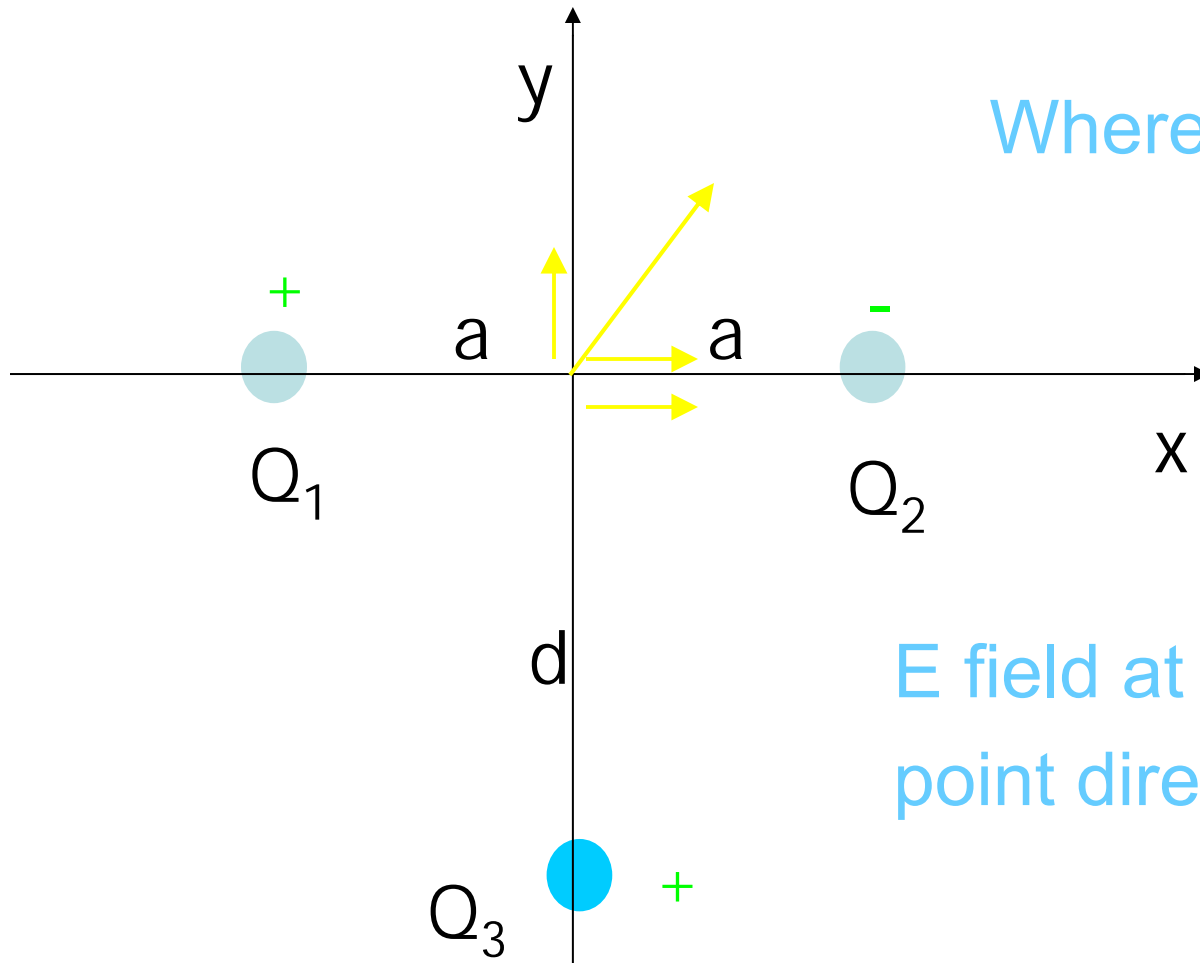


Where does F point at 0?

E field at origin does not point directly away from Q_1

Set #3, Problem #4

True or false: External work to bring charges together is negative

True

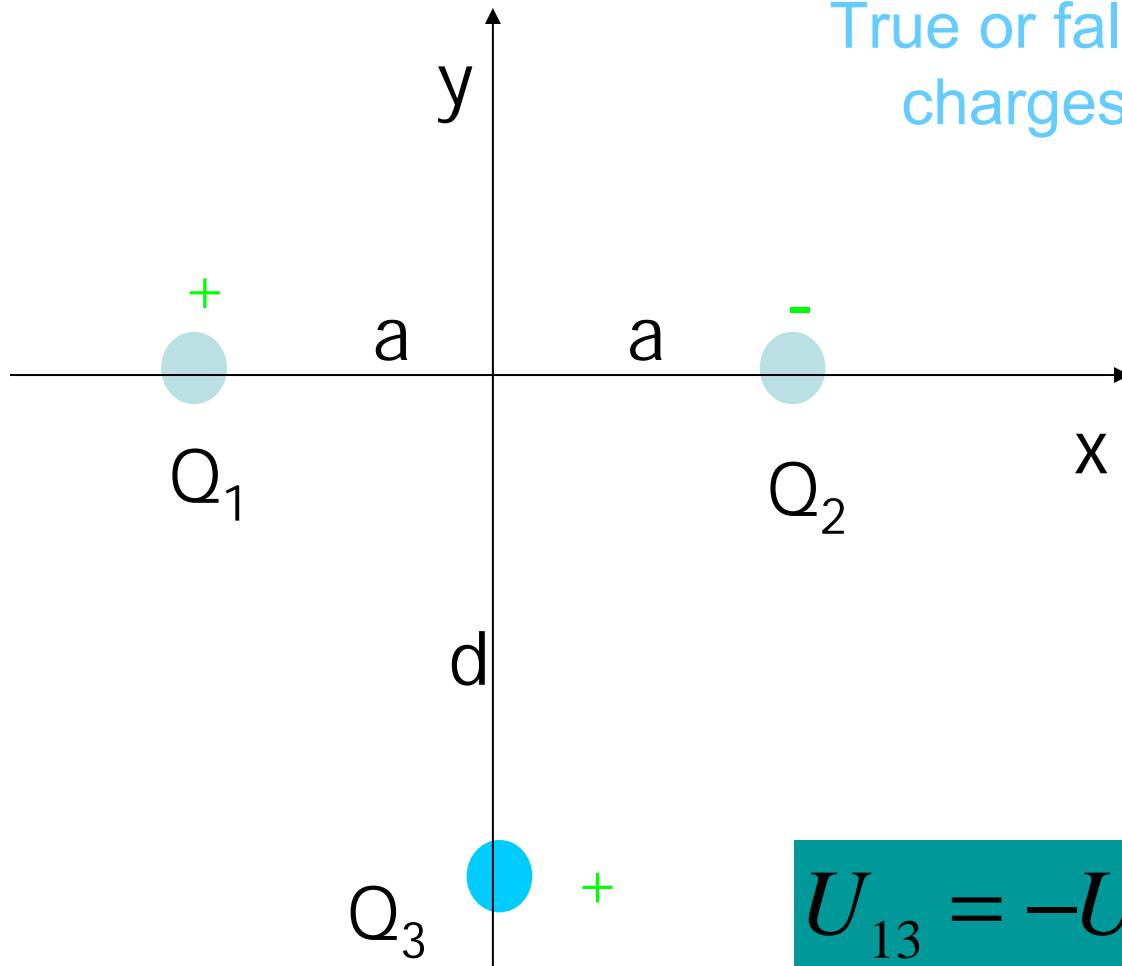

$$W = \Delta U = k \frac{qq'}{r}$$

$$U = U_{12} + U_{13} + U_{23}$$

$$U_{13} = -U_{23}$$

$$U_{12} = k \frac{Q(-Q)}{2a}$$

Capacitance (23)

- Parallel-plate capacitor charged to potential V by battery
- Disconnect battery to have isolated system
- If decrease distance, d , between the plates what happens to C ?

LARGER

- What happens to V ?

Isolated system q stays same so V decreases if C increases

$$C = \frac{\epsilon_0 A}{d}$$

$$q = CV$$

$$V = \frac{q}{C}$$

Capacitance (24)



- What happens if put material between the plates?
- Will the capacitance of the plates increase or decrease?

$$C = \frac{q}{V}$$

V decreases so C increases


Capacitance (25)

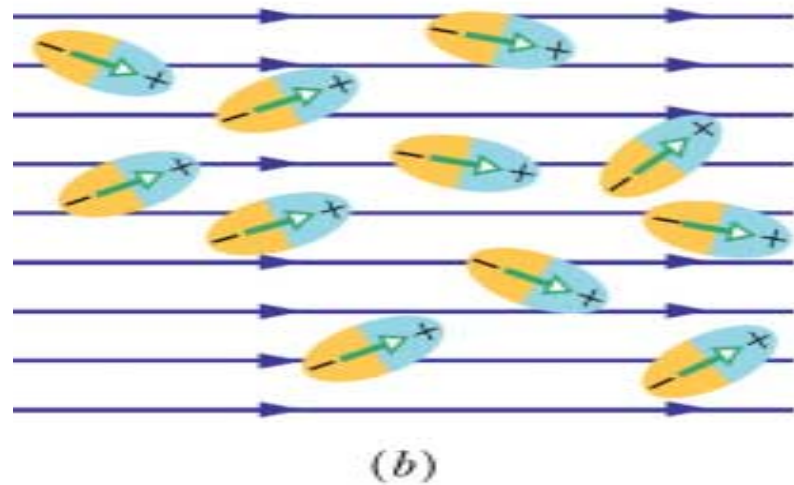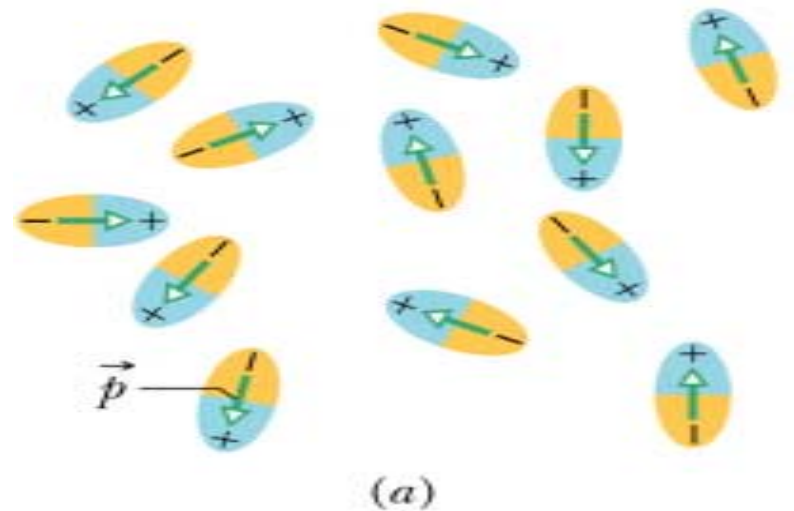- Why does C increase if add material?
- Material made up of molecules which are dipoles
- Molecules align with E field from capacitor




Capacitance (26)

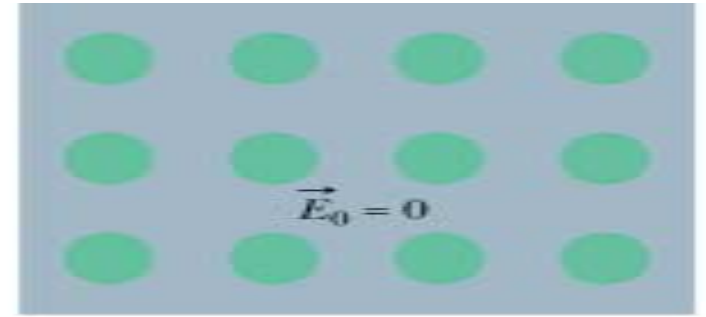
- Dipoles set up E field which opposes capacitors E field
- Total E field is weakened by adding material
- Material is called a **dielectric**



(a)

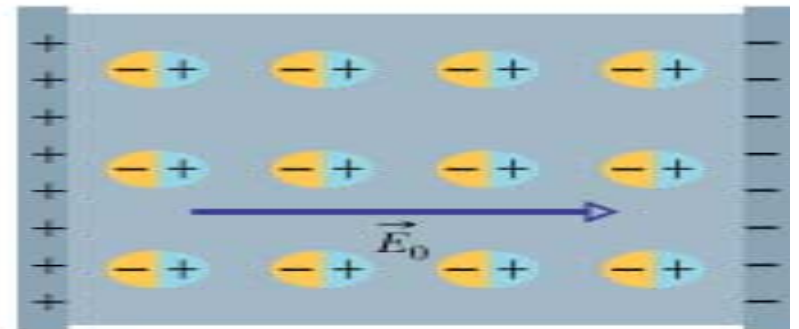

(b)

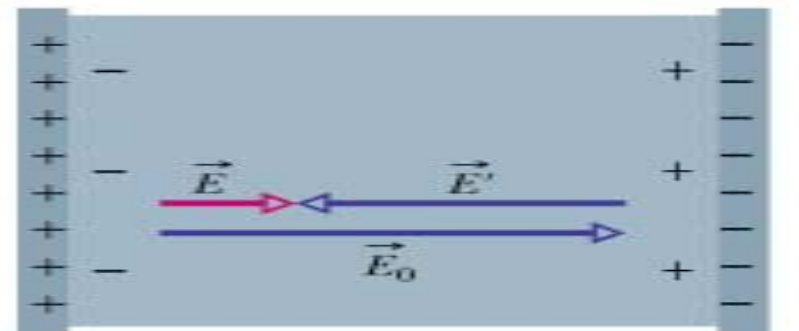

(c)



Capacitance (27)

$$V = Ed$$

- E field is weaker so V decreases

$$C = \frac{q}{V}$$

- q is constant so C
INCREASES

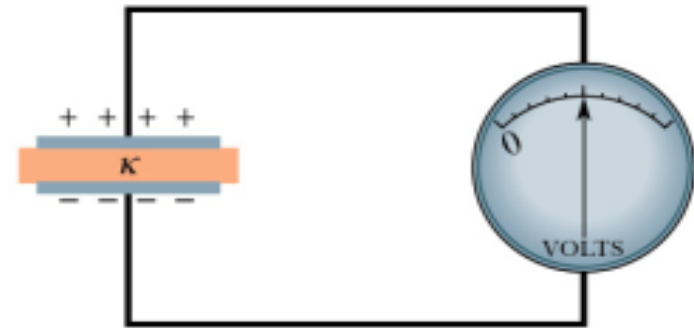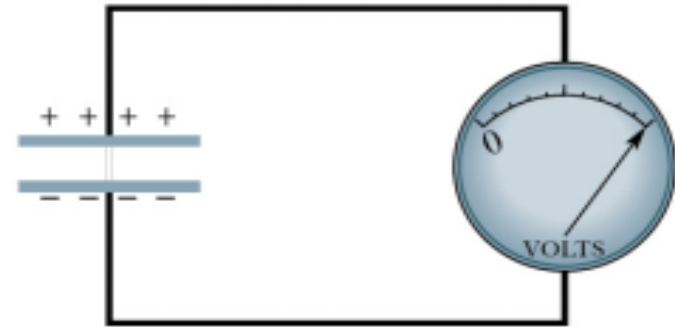

$q = \text{a constant}$

(b)

Capacitance (28)

- Place a dielectric in capacitor its capacitance increases by numerical factor
 - Called dielectric constant, κ

$$C_{dielectric} = \kappa C_{air}$$

- Modify all electrostatic equations by replacing ϵ_0 with $\kappa\epsilon_0$

$$E = \frac{1}{4\pi\kappa\epsilon_0} \frac{q}{r^2}$$

$$\epsilon_0 \oint \kappa \vec{E} \cdot d\vec{A} = q$$

Capacitance (29)

- If system connected to battery, V is a constant
- C increases with dielectric so q must increase

$$q = CV$$

- If system isolated, q is a constant
- C increases with dielectric so V must decrease



$V = \text{a constant}$

(a)



$q = \text{a constant}$


(b)

Capacitance (30)

- What if we have more than one capacitor in a circuit?
 - Replace combination with **equivalent capacitor C_{eq}**
- 2 basic combinations
 - Parallel
 - Series

Capacitance (31)

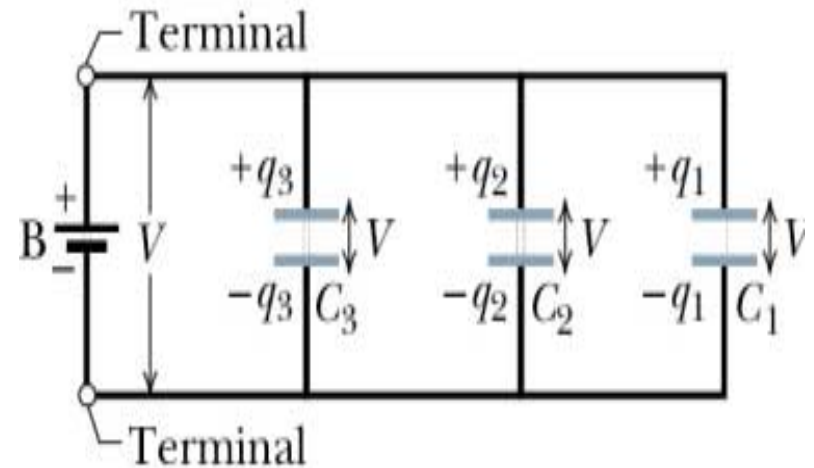
- Capacitors in parallel
- Capacitors are directly wired together at each plate and V applied across the group of plates



(a)

- V is same across all capacitors

$$V_1 = V_2 = V_3 = V$$

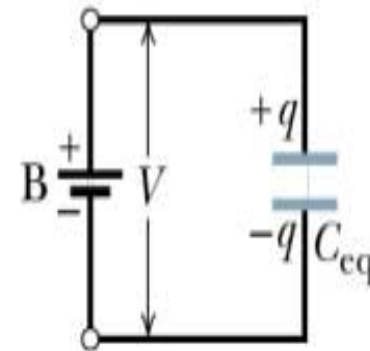

(b)


Capacitance (32)

- Capacitors in parallel
- Total q stored on capacitors is sum of the charges of all capacitors


$$q = q_1 + q_2 + q_3$$

- C_{eq} has total charge q and same V as original capacitors

$$C_{eq} = \frac{q}{V}$$

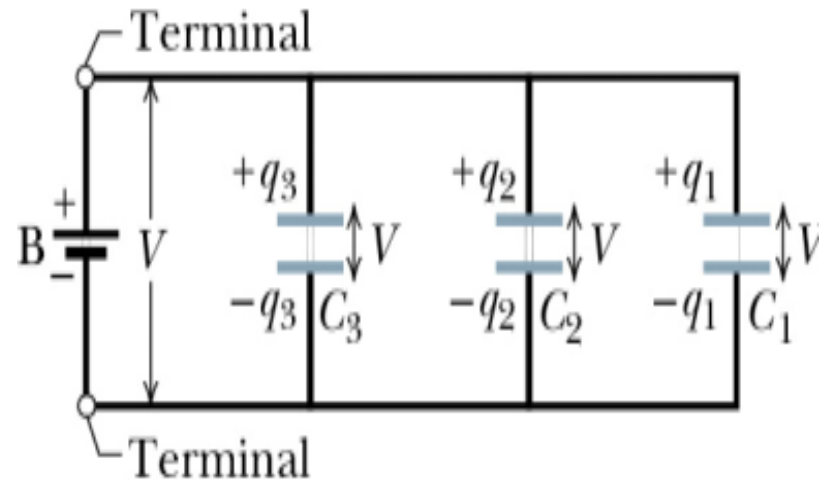

(a)

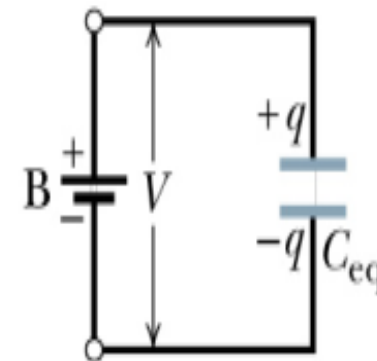

(b)

Capacitance (33)

- Capacitors in parallel

$$q = q_1 + q_2 + q_3$$

$$q_1 = C_1 V$$


$$q_2 = C_2 V$$

$$q_3 = C_3 V$$


$$q = (C_1 + C_2 + C_3)V$$

$$C_{eq} = C_1 + C_2 + C_3$$

$$C_{eq} = \sum_i^n C_i$$

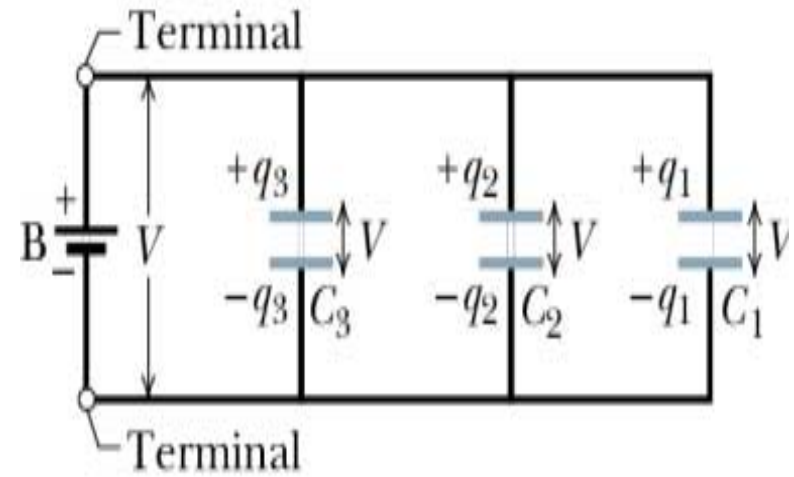

(a)

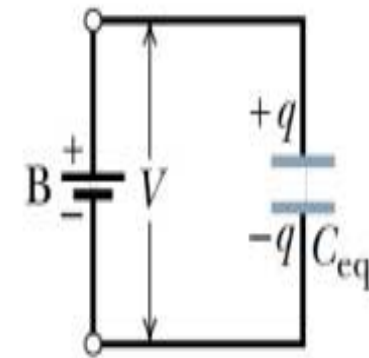


(b)

Capacitance (34)


- Capacitors in series
- Capacitors are wired one after the other and V is applied across the two ends of the series
- Capacitors have identical q

$$q_1 = q_2 = q_3 = q$$

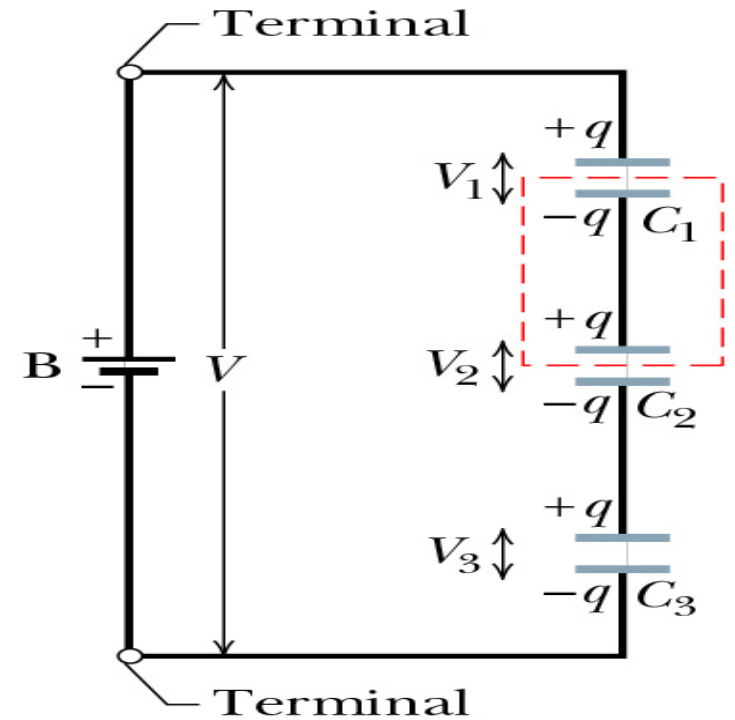- Battery produces q only on top and bottom plates, induced q on other plates



(a)

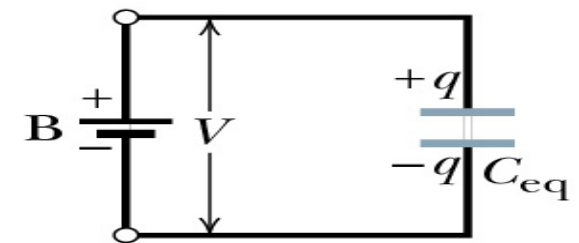

(b)


Capacitance (35)

- Capacitors in series
- Sum of V across all capacitors is equal to applied V


$$V = V_1 + V_2 + V_3$$

- C_{eq} has same q and total V as original capacitors

$$C_{eq} = \frac{q}{V}$$

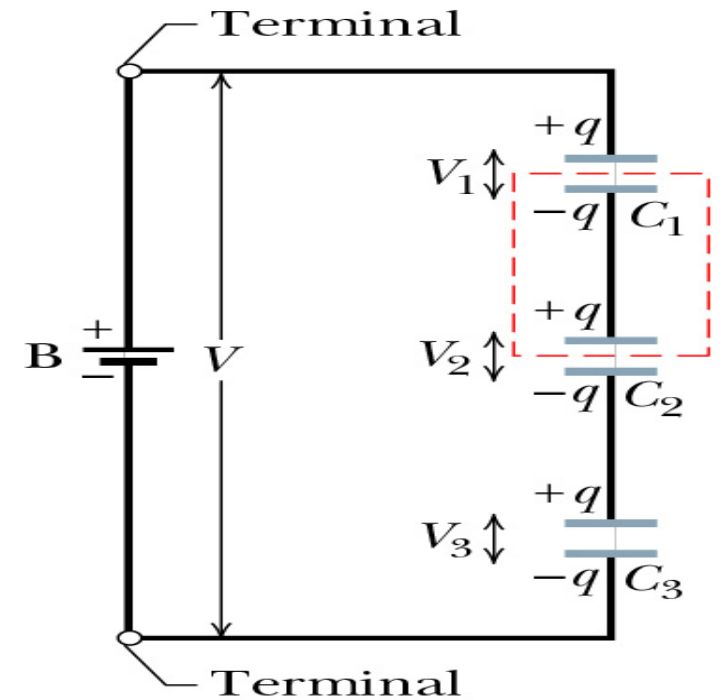

(a)

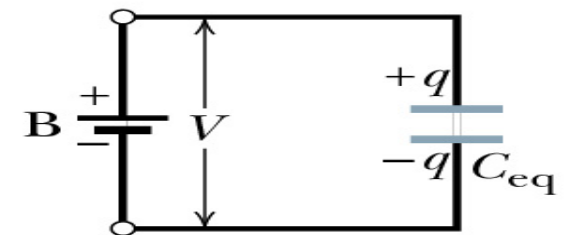

(b)

Capacitance (36)

- Capacitors in series

$$V = V_1 + V_2 + V_3$$


$$V_1 = \frac{q}{C_1}$$

$$V_2 = \frac{q}{C_2}$$


$$V_3 = \frac{q}{C_3}$$

$$V = q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$
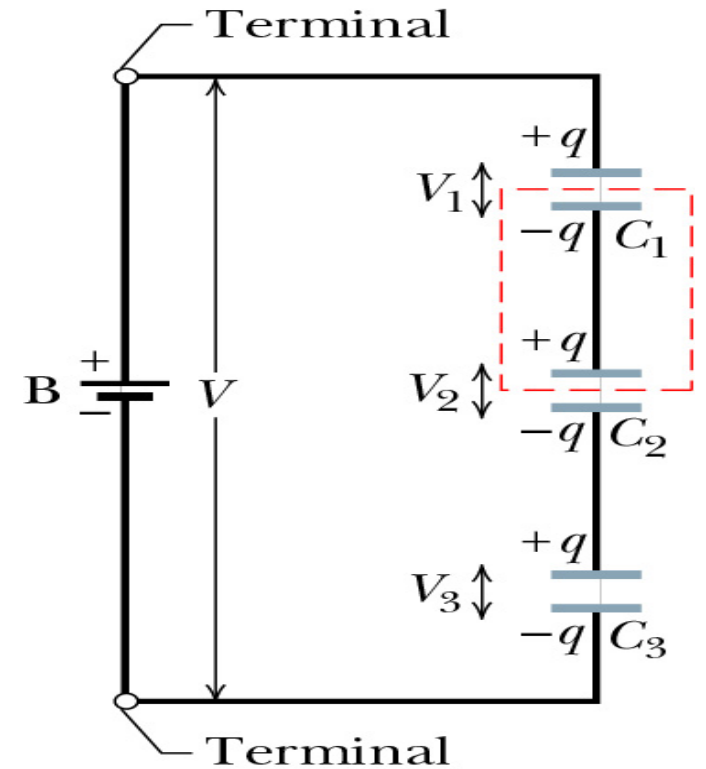
$$\frac{1}{C_{eq}} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$



(a)

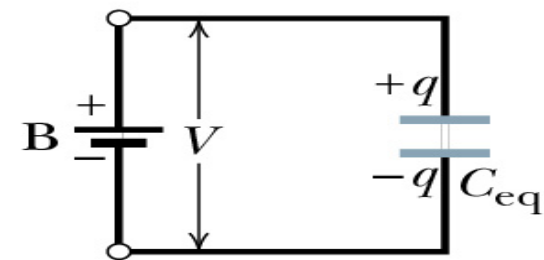


(b)

Capacitance (37)


- Capacitors in series
- Charge can only be shifted from one capacitor to another
- If alternate routes not in series

$$\frac{1}{C_{eq}} = \sum_i^n \frac{1}{C_i}$$

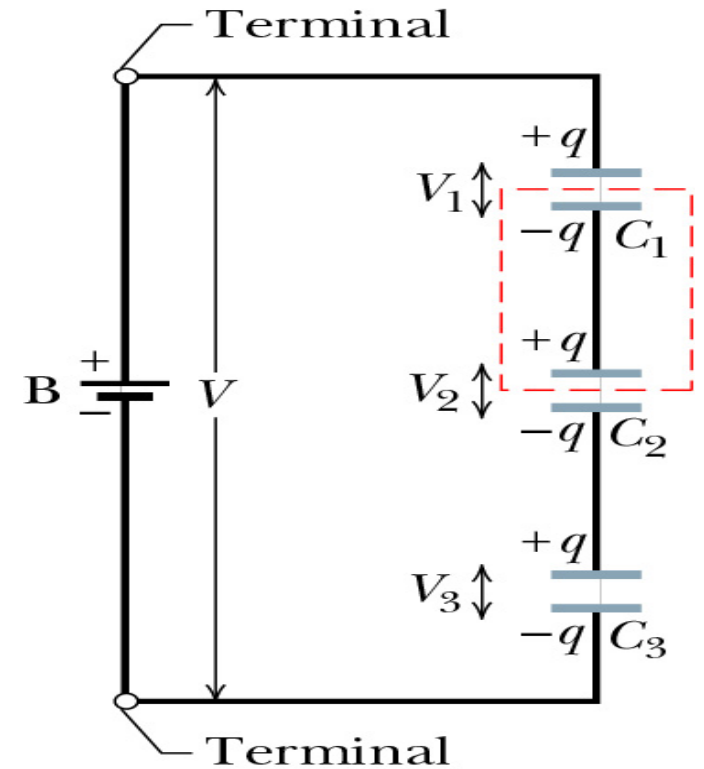- C_{eq} is always less than smallest capacitance



(a)

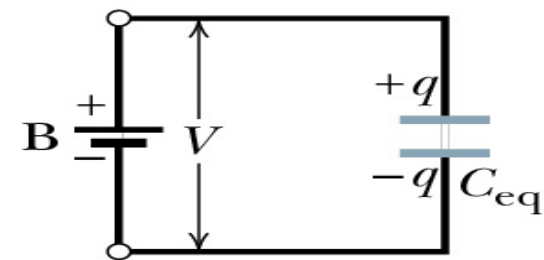

(b)

Capacitance (38)

- Capacitors in parallel
 - V across each is equal
 - Total q is sum
- Capacitors in series
 - q is equal on each
 - Total V is sum

$$C_{eq} = \sum_i^n C_i$$

$$\frac{1}{C_{eq}} = \sum_i^n \frac{1}{C_i}$$

Capacitance (39)

- Checkpoint #3 – A battery with V stores charge q on 2 identical capacitors
- A) What is V across and q on either capacitor if they are in parallel?
- V is same for each and equal to V of battery
 - Total charge conserved so

$$q = q_1 + q_2 = 2q_1$$

$$q_{cap} = \frac{q}{2}$$

Capacitance (40)

- Checkpoint #3 – A battery with V stores charge q on 2 identical capacitors
- A) What is V across and q on either capacitor if they are in series?
 - q is same for each
 - V is sum of V across capacitors

$$V = V_1 + V_2 = 2V_1$$

$$V_{cap} = \frac{V}{2}$$