


# Lecture 15

Chapter 28

Circuits

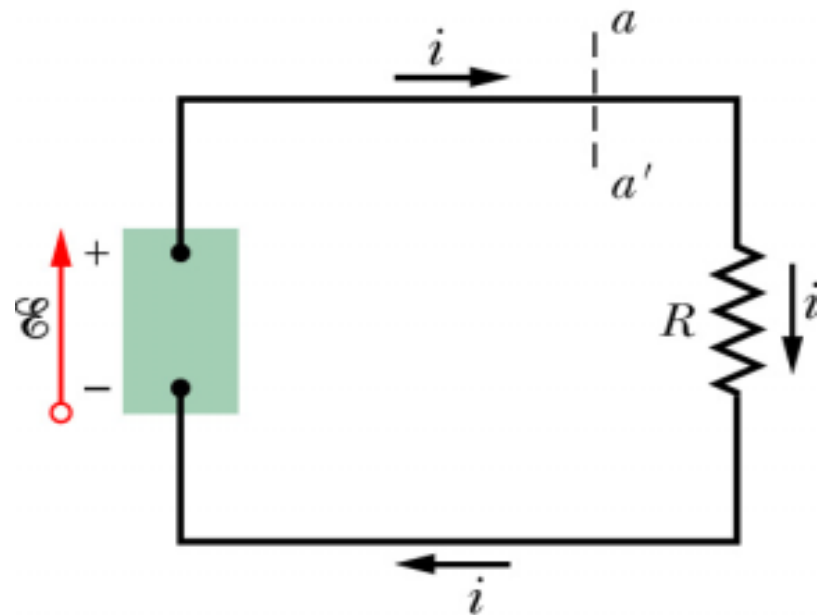
# Review

- **emf device** label terminal at higher  $V$  as + and lower  $V$  as –
- Draw emf,  $\mathcal{E}$ , arrow from – to + terminal
- + charge carriers move against  $E$  field in emf device from lower (-) to higher (+)  $V$


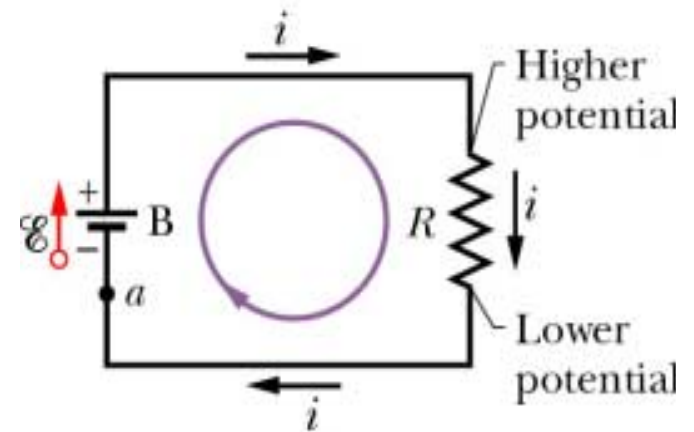
# Review

- **Kirchhoff's loop rule** – in traversing a circuit loop the sum of the changes in  $V$  is zero,  $\Delta V = 0$
- **Resistance rule** – Move through resistor in direction of current  $V = -iR$ , in opposite direction  $V = +iR$
- **Emf rule** – Move through emf device in direction of emf arrow  $V = +E$ , in opposite direction  $V = -E$




# Review

- Put **real** battery in circuit
- Using Kirchhoff's loop rule and starting at point a gives

$$\mathcal{E} - ir - iR = 0$$

$$\mathcal{E} = i(r + R)$$

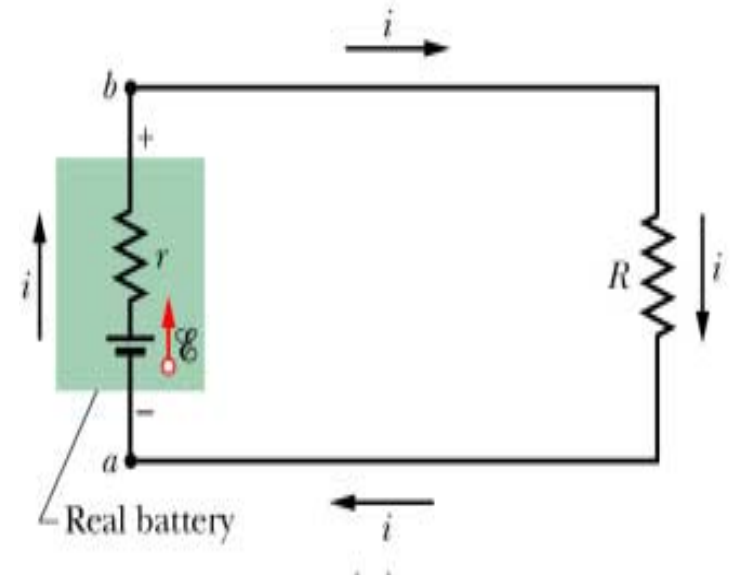- For ideal battery,  $r = 0$  and we get same as before



$$\mathcal{E} = iR$$

# Circuits (25)

- Arbitrarily label currents, using different subscript for each branch
- Using conservation of charge can write


$$i_{in} = i_{out}$$

- At point d

$$i_1 + i_3 = i_2$$

- At point b

$$i_1 + i_3 = i_2$$

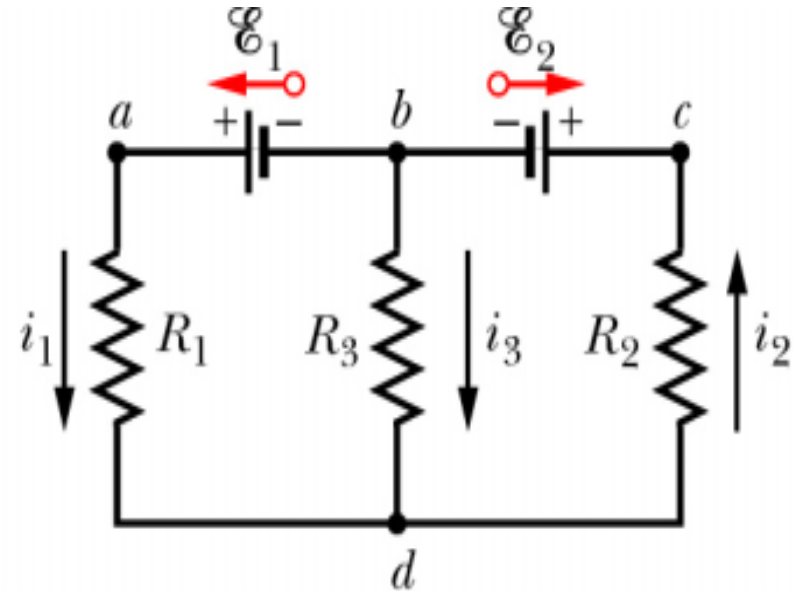

- At point a

$$i_1 = i_1$$

- At point c

$$i_2 = i_2$$

# Circuits (26)


- Kirchhoff's junction rule (or current law) –
  - From conservation of charge
  - Sum of currents entering a junction is equal to sum of currents leaving that junction
- Kirchhoff's loop rule (or voltage law) –
  - From conservation of energy
  - Sum of changes in potential going around a complete circuit loop equals zero

# Circuits (27)

- Resistors in series
- Have identical currents,  $i$ , through them
- Use Kirchhoff's loop rule

$$\mathcal{E} - iR_1 - iR_2 - iR_3 = 0$$
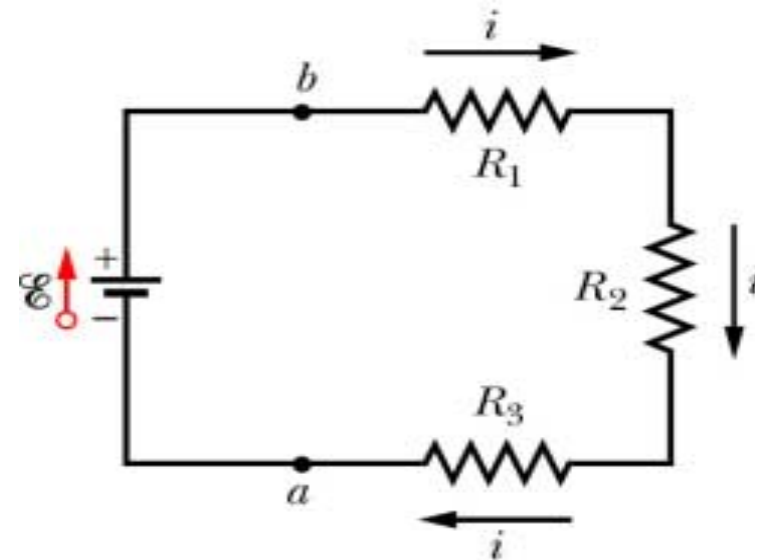
$$i = \frac{\mathcal{E}}{R_1 + R_2 + R_3}$$




# Circuits (28)


- Resistors in series
- Replace 3 resistors with equivalent resistor  $R_{eq}$

$$i = \frac{E}{R_1 + R_2 + R_3}$$

$$R_{eq} = R_1 + R_2 + R_3$$

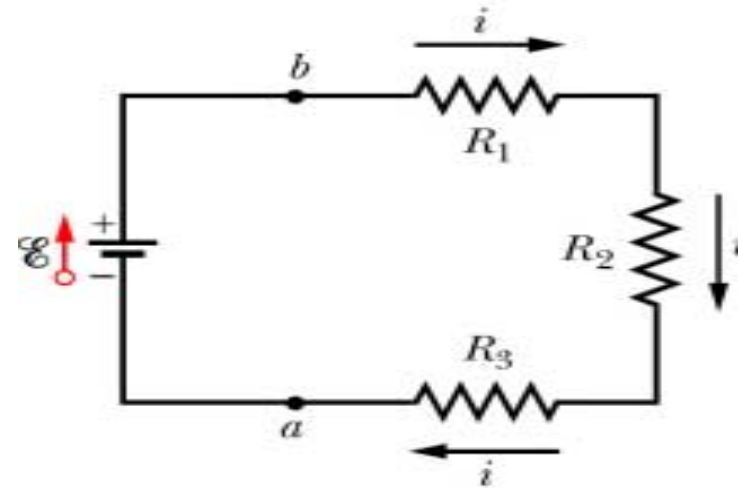

(a)

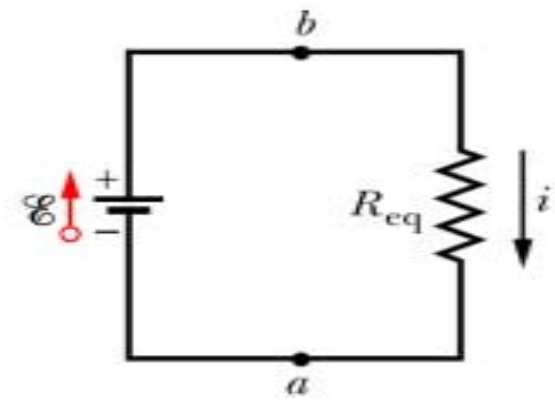





# Circuits (29)

- Resistors in series –
- Resistors have identical currents,  $i$
- Sum of  $V$  s across resistors = applied  $V$
- $R_{eq}$  is sum of all resistors

$$R_{eq} = \sum_{j=1}^n R_j$$

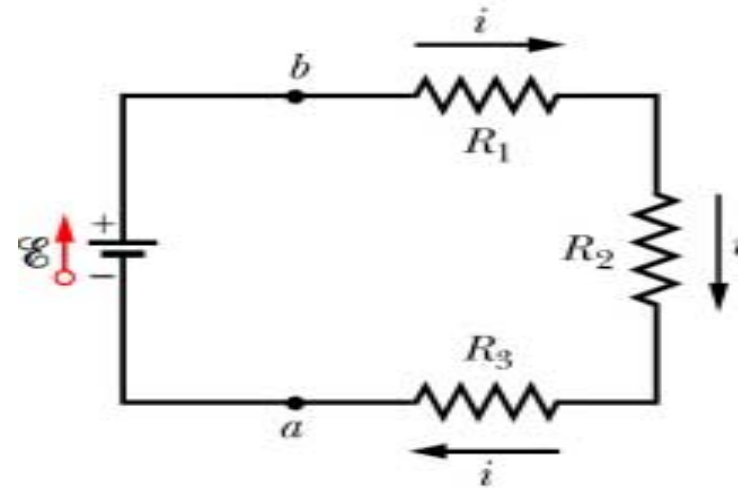

(a)

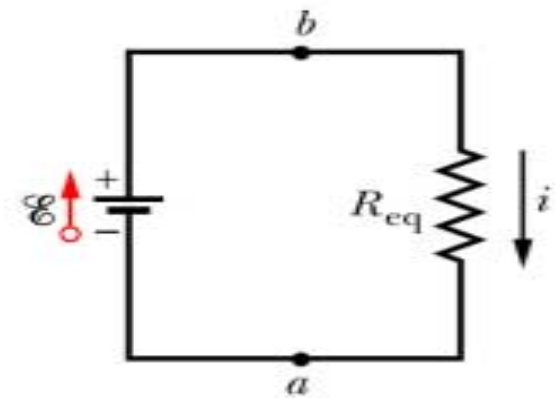


...

# Circuits (30)

- Checkpoint #2 – If  $R_1 > R_2 > R_3$ , rank greatest first
- A) current through resistors  
 $i$  is same for all, tie
- B)  $V$  across them


$$V = iR$$

$R_1, R_2, R_3$

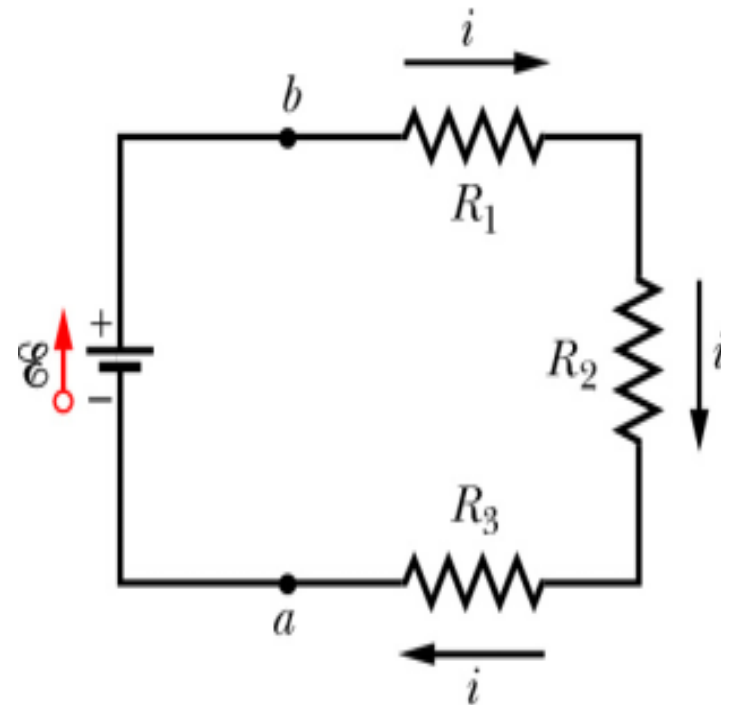
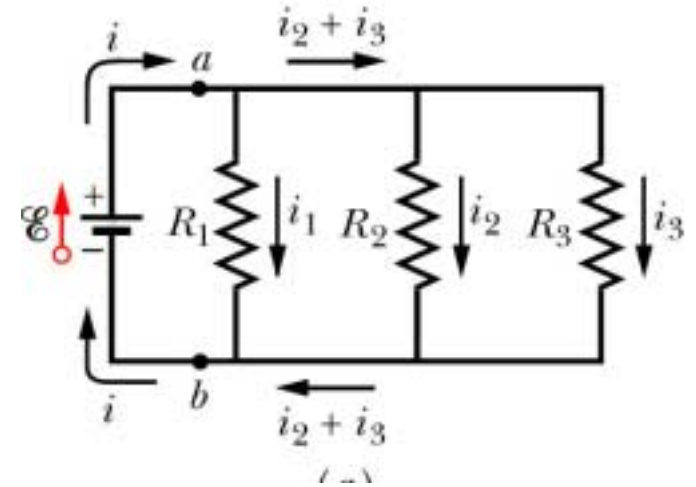
# Circuits (31)

- Resistors in parallel
- Have same  $V$  across them
- Arbitrarily choose direction for currents in each branch
- Write down current relation for each resistor



$$i_1 = \frac{V}{R_1}$$

$$i_2 = \frac{V}{R_2}$$

$$i_3 = \frac{V}{R_3}$$


# Circuits (32)

- Resistors in parallel
- Apply Kirchhoff's junction rule at point a

$$i = i_1 + i_2 + i_3$$



- Substitute current values
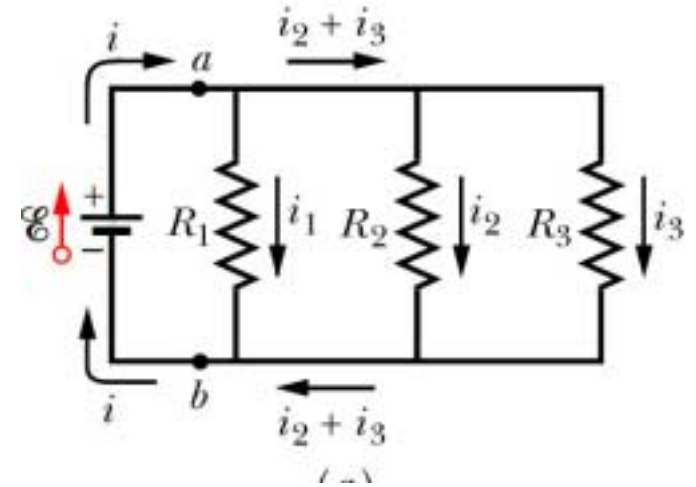
$$i = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$


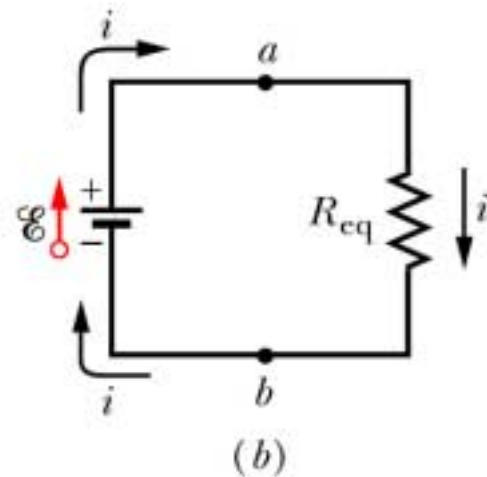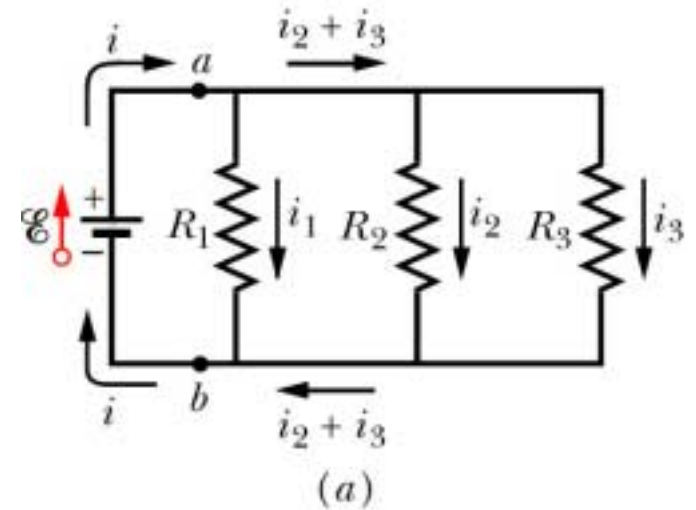
# Circuits (33)

- Resistors in parallel
- Replace 3 resistors with equivalent resistor,  $R_{eq}$



$$\frac{1}{R_{eq}} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

# Circuits (34)

- Resistors
- Series

$$R_{eq} = \sum_{j=1}^n R_j$$

- Parallel

$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$$

- Capacitors
- Series

$$\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j}$$

- Parallel

$$C_{eq} = \sum_{j=1}^n C_j$$

# Circuits (35)

- Checkpoint #4 – Battery with potential  $V$  supplies current  $i$  to 2 identical resistors
- What is  $V$  across and  $i$  through either of the resistors if they are connected in
- A) Series – What is constant?

$i$  is same,  $V_1 = V/2$


$$V = iR$$

- B) Parallel – What is constant?

$V$  is same,  $i_1 = i/2$
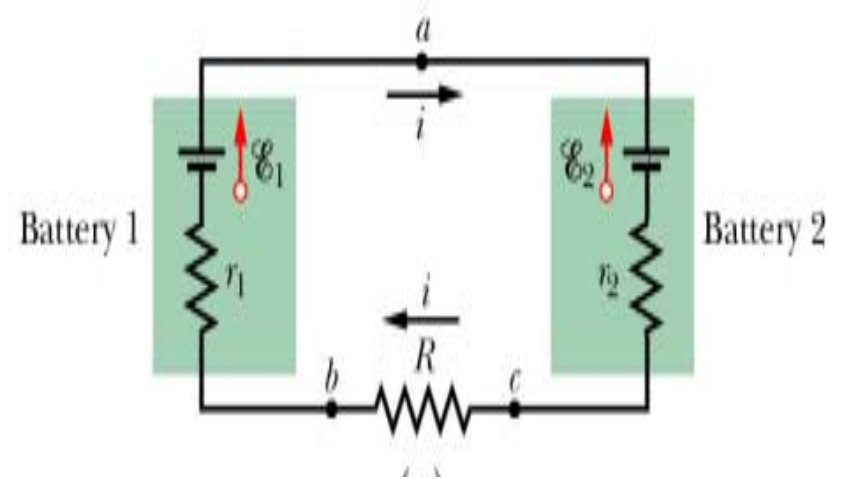
# Circuits (36)

- What is  $i$  of the circuit?
- Use Kirchhoff's loop rule



- Clockwise from point  $a$  gives

$$-\mathcal{E}_2 - ir_2 - iR - ir_1 + \mathcal{E}_1 = 0$$

- Counterclockwise from point  $a$  gives

$$-\mathcal{E}_1 + ir_1 + iR + ir_2 + \mathcal{E}_2 = 0$$



# Circuits (37)

- Solve for  $i$

$$-\mathcal{E}_1 + ir_1 + iR + ir_2 + \mathcal{E}_2 = 0$$

$$i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R + r_1 + r_2}$$


$$\mathcal{E}_1 = 4.4V$$

$$\mathcal{E}_2 = 2.1V$$

$$r_1 = 2.3\Omega$$

$$r_2 = 1.8\Omega$$

$$R = 5.5\Omega$$

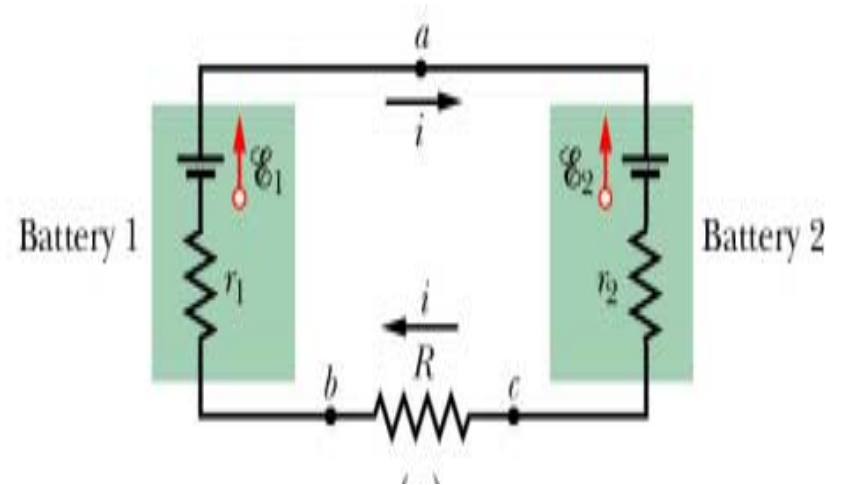

$$i = 0.2396A \approx 240mA$$


# Circuits (38)

- What is  $V$  across battery 1's terminals?
- Sum potential differences from point b to point a
  - Clockwise

$$V_b - ir_1 + \mathcal{E}_1 = V_a$$

- Counterclockwise
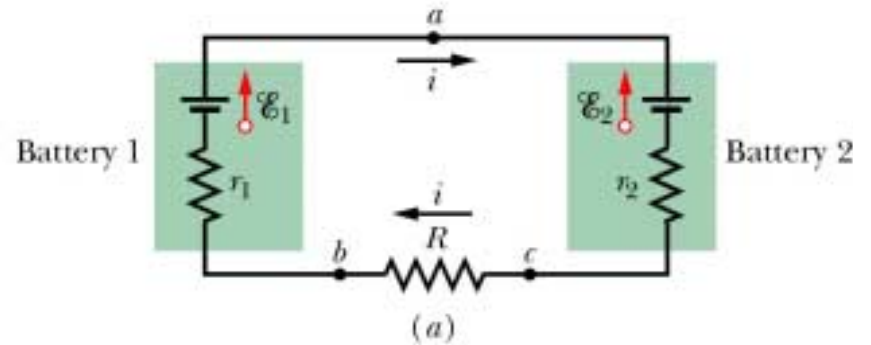
$$V_b + iR + ir_2 + \mathcal{E}_2 = V_a$$



$$V_a - V_b = \mathcal{E}_1 - ir_1$$

$$V_a - V_b = 3.84V$$

$$V_a - V_b = i(R + r_2) + \mathcal{E}_2$$

# Circuits (39)

- Checkpoint #3 – A real battery has  $\mathcal{E} = 12\text{V}$  and  $r = 2\Omega$ . Is the  $V$  across the terminals greater than, less than or equal to  $12\text{V}$  if the current in the battery is

- A) from – to + terminal

- LESS THAN

$$V_a + \mathcal{E} - ir = V_b$$

- B) from + to -

- GREATER THAN

$$V_a + \mathcal{E} + ir = V_b$$

- C)  $i = 0$

- EQUAL TO  $12\text{V}$

