

Lecture 16

Chapter 28
Circuits

Circuits (39)

- Checkpoint #3 – A real battery has $\mathcal{E} = 12\text{V}$ and $r = 2\Omega$. Is the V across the terminals greater than, less than or equal to 12V if the current in the battery is
- A) from $-$ to $+$ terminal – **LESS THAN**

$$V_a + \mathcal{E} - ir = V_b$$


$$V_b - V_a = \mathcal{E} - ir$$

- B) from $+$ to $-$ terminal - **GREATER THAN**

$$V_a + \mathcal{E} + ir = V_b$$

$$V_b - V_a = \mathcal{E} + ir$$

- C) $i = 0$ - **EQUAL TO 12V**

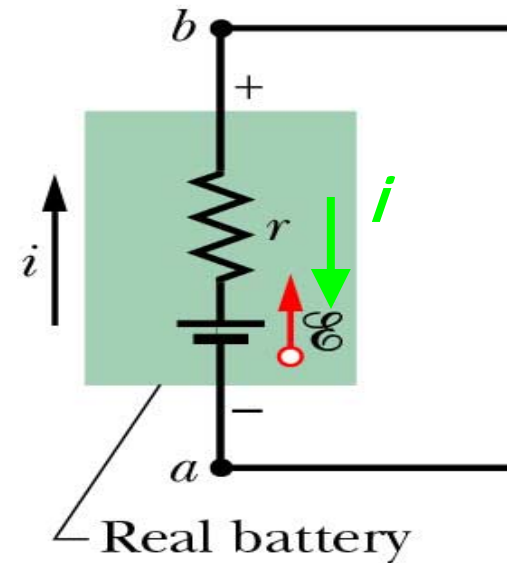


Circuits (40)

- Why is V greater when current is moving from $+$ to $-$ terminal?
- If start point a , go with emf arrow so $+\mathcal{E}$ but against current arrow so $+ir$ gives

$$V_a + \mathcal{E} + ir = V_b$$

$$V_b - V_a = \mathcal{E} + ir$$

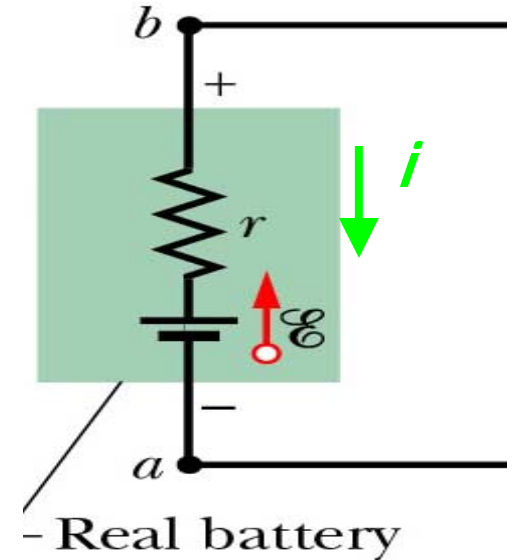

- If start point b , go with current arrow so $-ir$ but against emf arrow so $-\mathcal{E}$ gives

$$V_b - ir - \mathcal{E} = V_a$$


$$V_b - V_a = \mathcal{E} + ir$$

Circuits (41)

- What does it mean to have a V across the batteries terminals which is greater than its emf?


$$V_b - V_a = \mathcal{E} + ir$$

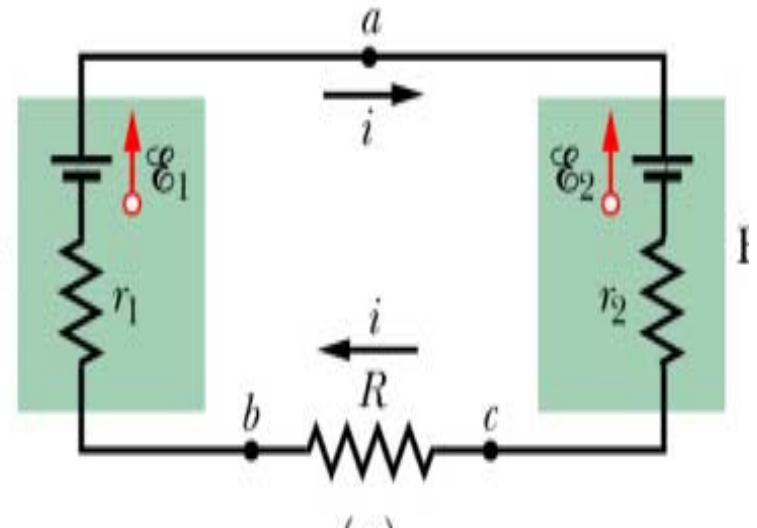- How could you get a current flowing against the emf arrow of a battery?
- Battery of greater V connected in opposite direction would be charging the smaller battery




Circuits (42)

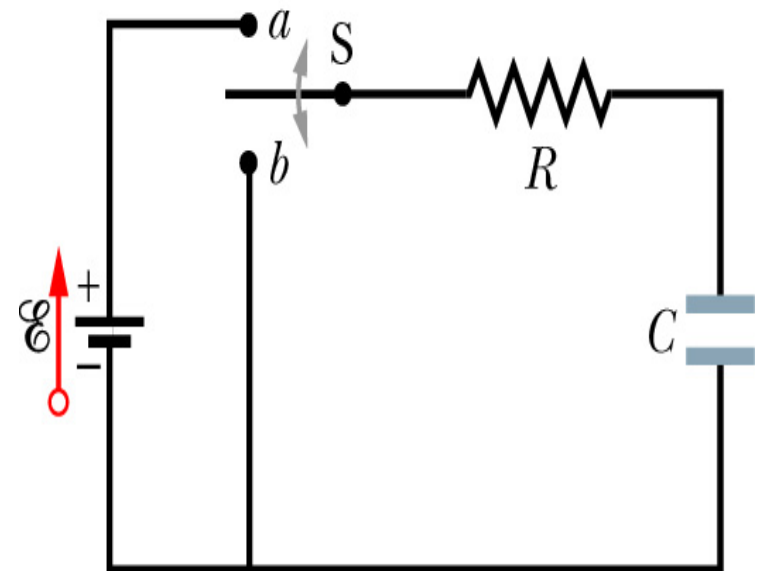- Circuits where current varies with time
- **RC series circuit** – a resistor and capacitor are in series with a battery and a switch
- At $t = 0$ switch is open and capacitor is uncharged so $q = 0$



Circuits (43)

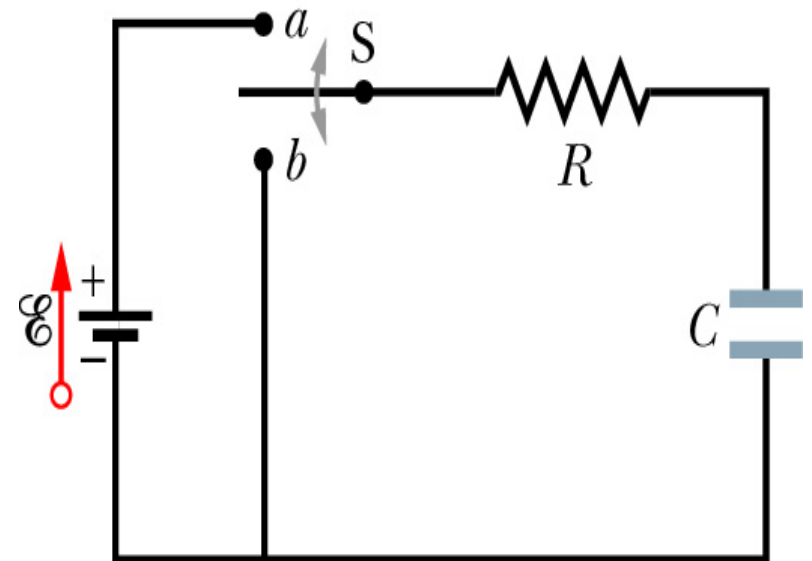
- Close the switch at point a
- Charge flows (current) from battery to capacitor, increasing q on plates and V across plates
- When V_C equal $V_{battery}$ flow of charge stops (current is zero) and charge on capacitor is



$$q = CV = C\mathcal{E}$$

Circuits (44)

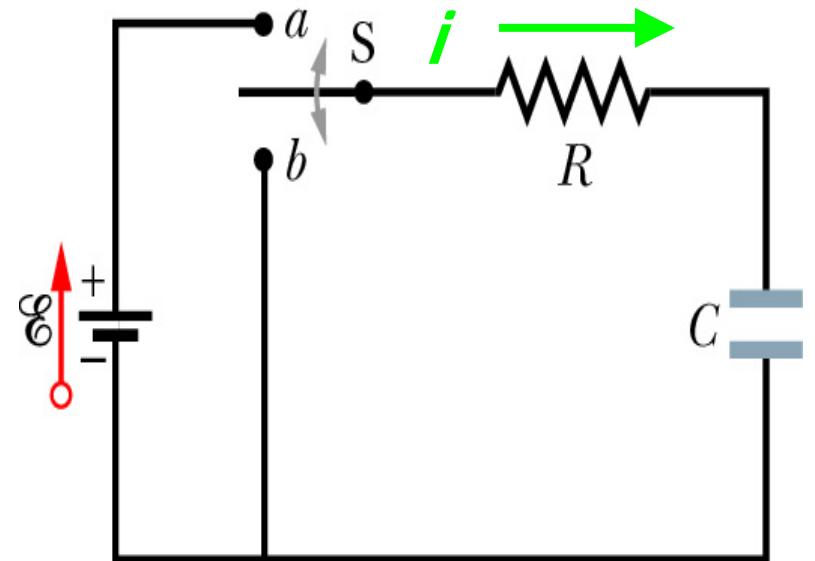- Want to know how q and V of capacitor and i of the circuit change with time when charging the capacitor
- Apply loop rule, traversing clockwise from battery



$$\mathcal{E} - iR - \frac{q}{C} = 0$$

Circuits (45)


$$\mathcal{E} - iR - \frac{q}{C} = 0$$

- Contains 2 of the variables we want i and q
- Remember

$$i = \frac{dq}{dt}$$

- Substituting gives

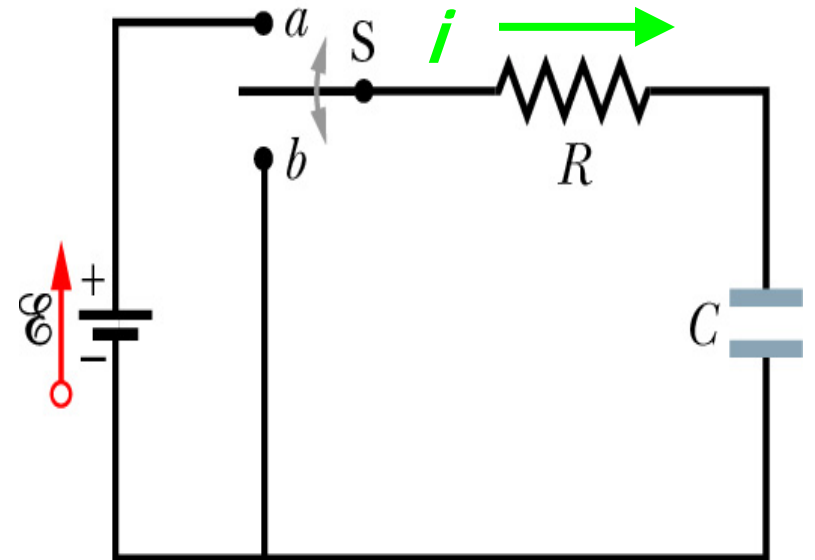
$$R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E}$$



Circuits (46)

$$R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E}$$

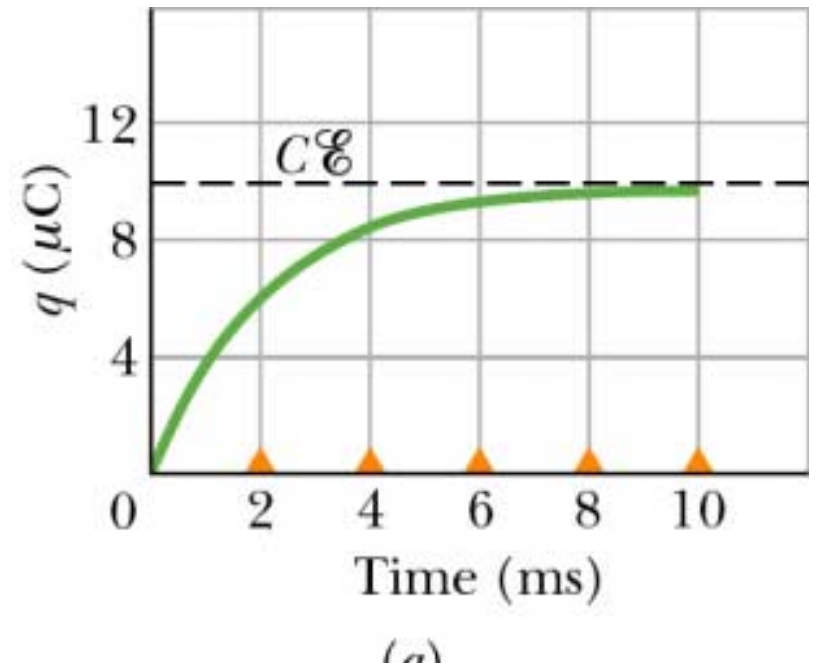- Need a function which satisfies initial condition $q = 0$ at $t = 0$ and final condition of $q = C\mathcal{E}$ at $t = \infty$
- For charging a capacitor




$$q = C\mathcal{E}\left(1 - e^{-t/RC}\right)$$

Circuits (47)

$$q = C\mathcal{E}\left(1 - e^{-t/RC}\right)$$

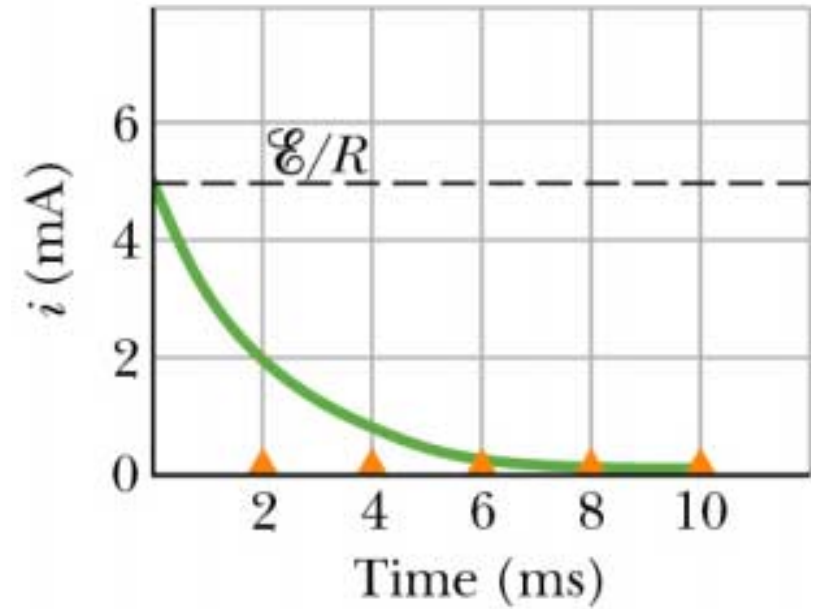- Want current as a function of time
- For charging a capacitor




$$i = \frac{dq}{dt} = \left(\frac{\mathcal{E}}{R}\right)e^{-t/RC}$$

Circuits (48)

$$q = C\mathcal{E}\left(1 - e^{-t/RC}\right)$$

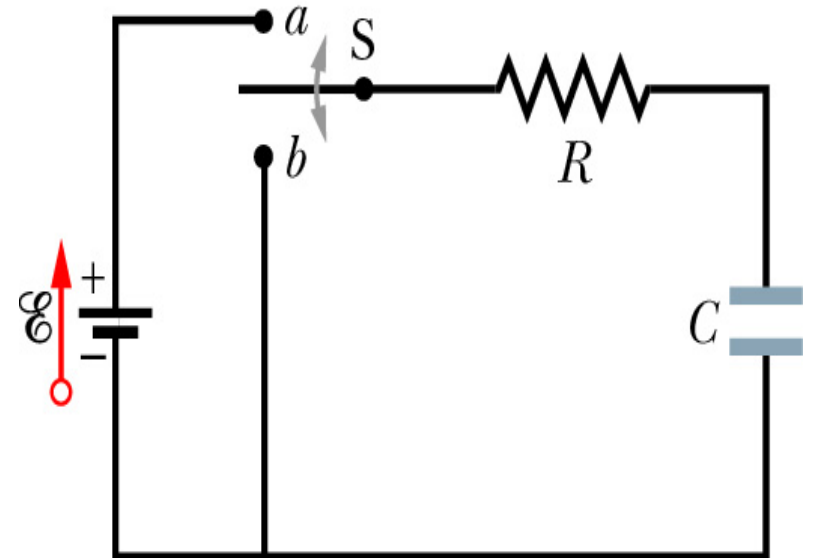
- Want V across the capacitor as function of time
- For charging a capacitor



$$V_c = \frac{q}{C} = \mathcal{E} \left(1 - e^{-t/RC}\right)$$

Circuits (49)

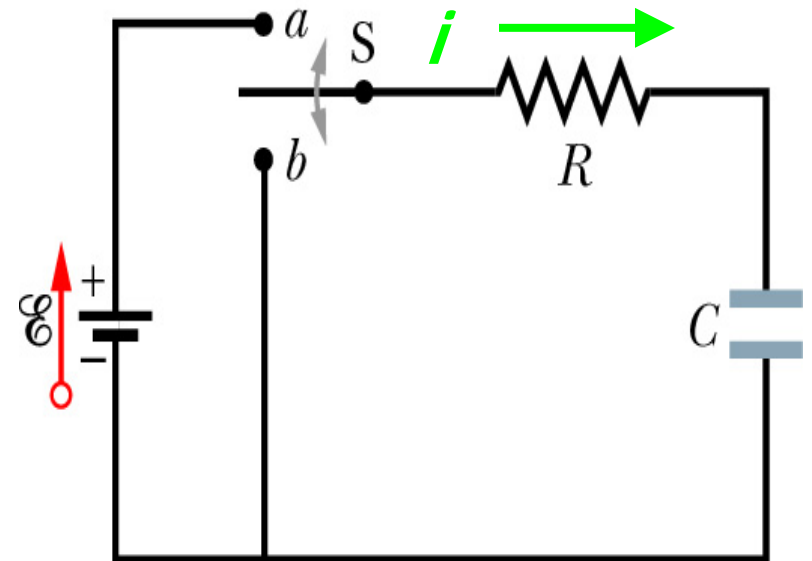- Want to know how q of capacitor and i of the circuit change with time when **discharging** the capacitor
- At new time $t = 0$, throw switch to point b and discharge capacitor through resistor R




Circuits (50)

- Apply the loop rule again but this time no battery

$$-iR - \frac{q}{C} = 0$$

- Substituting for i again gives differential equation

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$

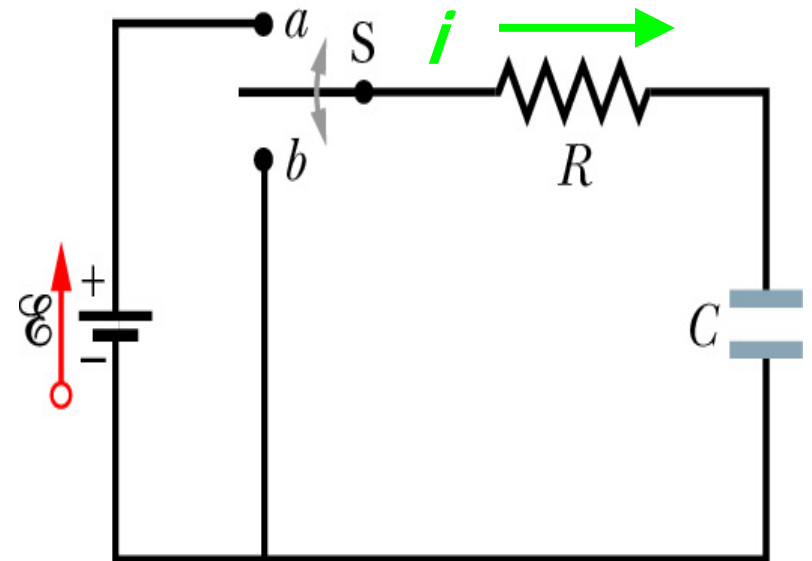


Circuits (51)

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$

- Solution must satisfy initial condition that $q_0 = CV_0$
- For discharging a capacitor

$$q = q_0 e^{-t/RC}$$

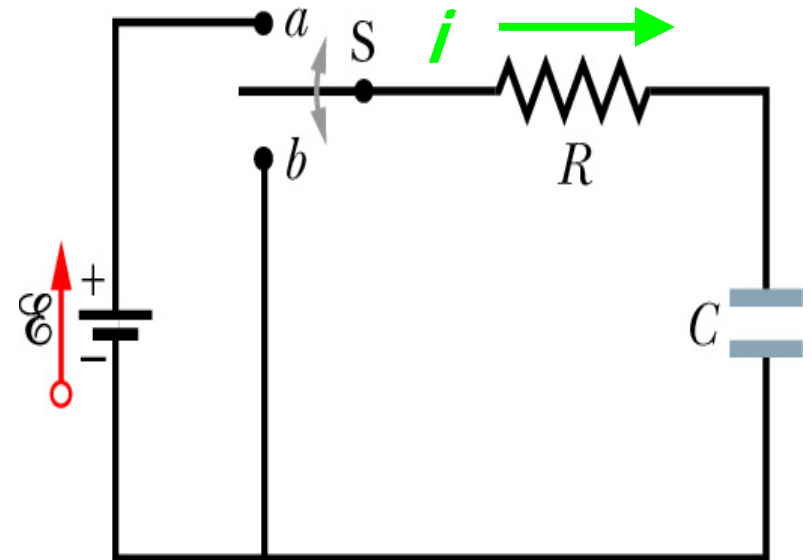


Circuits (52)

$$q = q_0 e^{-t/RC}$$

- Find i for **discharging capacitor** with initial condition at $i_0 = V_0/R = q_0/RC$ at $t = 0$
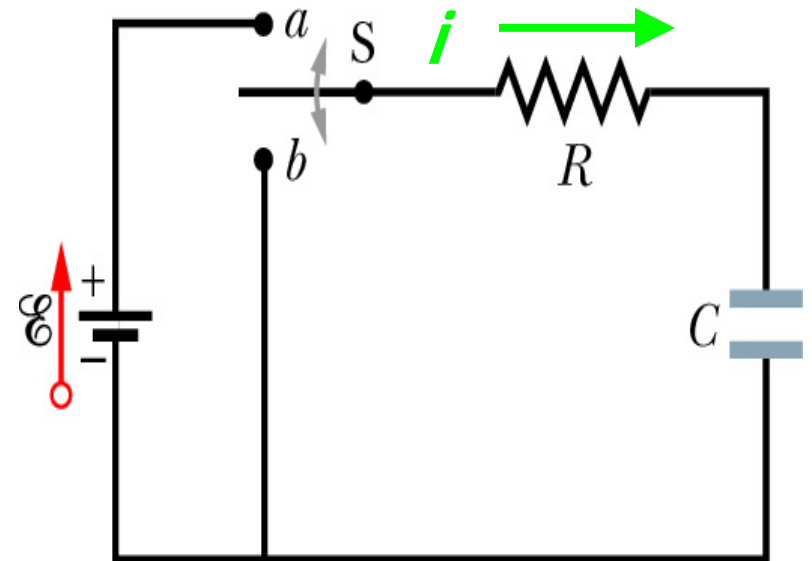
$$i = \frac{dq}{dt} = -\left(\frac{q_0}{RC}\right)e^{-t/RC}$$



Negative sign
means charge
is decreasing

Circuits (53)

- Charging capacitor

$$q = C\mathcal{E}\left(1 - e^{-t/RC}\right)$$

$$i = \left(\frac{\mathcal{E}}{R}\right)e^{-t/RC}$$

- Discharging capacitor

$$q = q_0 e^{-t/RC}$$



$$i = -\left(\frac{q_0}{RC}\right)e^{-t/RC}$$

- Define capacitive time constant –
greater τ , greater (dis)charging time

$$\tau = RC$$

Circuits (40)

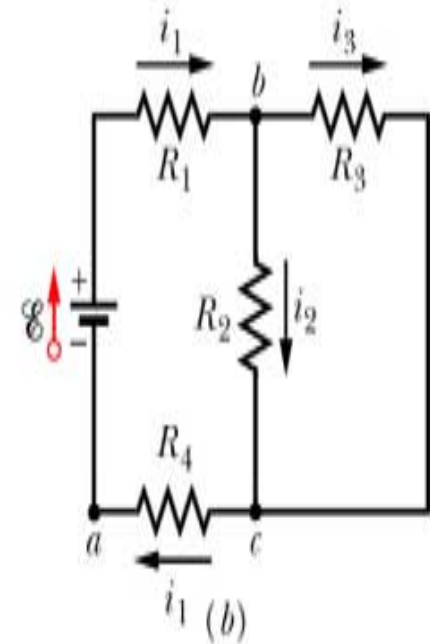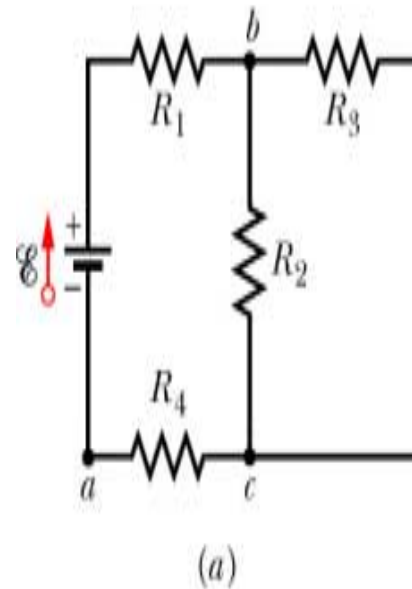- What is i through the battery?
- Label currents in loops
- i through R_1 or R_4 is same as for battery
- Can use loop rule



$$\mathcal{E} - i_1 R_1 - i_2 R_2 - i_1 R_4 = 0$$

Circuits (41)


$$\mathcal{E} - i_1 R_1 - i_2 R_2 - i_1 R_4 = 0$$

- Equation has 2 unknowns so need to apply loop rule again

OR

- Realize R_2 and R_3 are in parallel and find R_{eq}
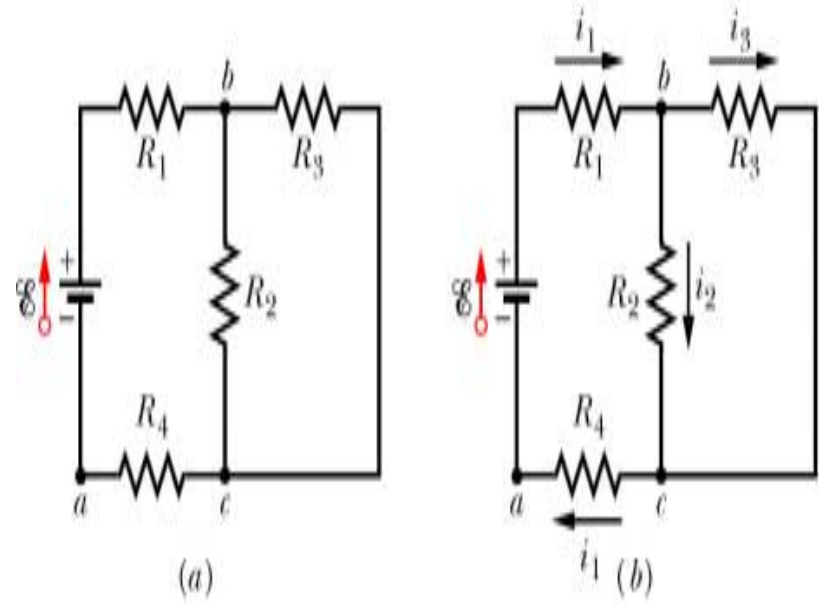
$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$$



$$R_{eq} = \frac{R_2 R_3}{R_2 + R_3}$$


Circuits (42)

- Now i through R_{eq} is equal to i_1
- Apply loop rule

$$E - i_1 R_1 - i_{23} R_{23} - i_1 R_4 = 0$$


- Now solve for i_1

$$i_1 = \frac{E}{R_1 + R_2 + R_3}$$

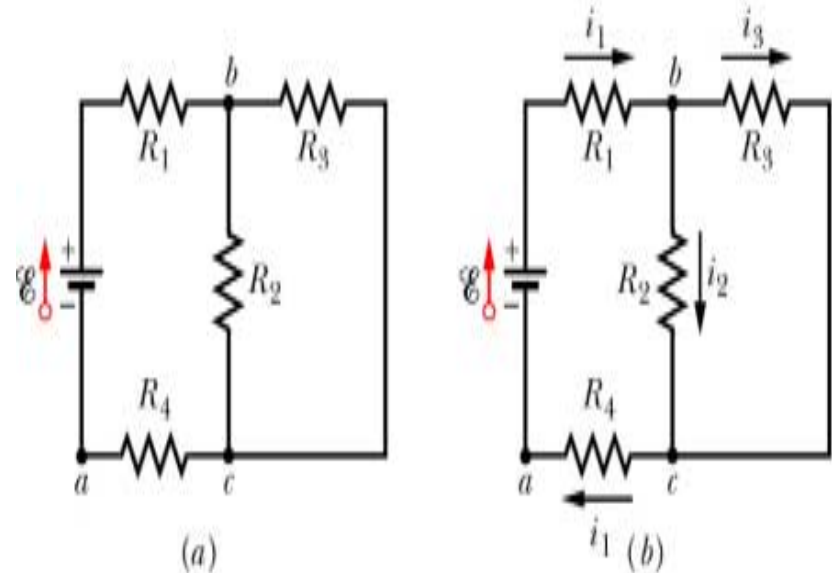

Circuits (43)

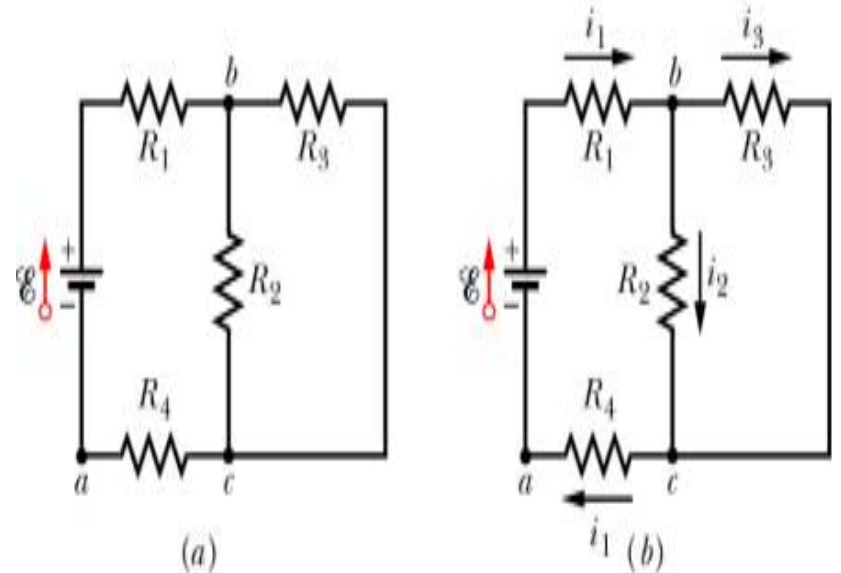- What is current i_2 through R_2 ?
- Work backwards from R_{eq} and realize V across R_{eq} is same for R_2 and R_3



$$V_{23} = i_1 R_{23}$$

$$V_{23} = V_2$$

$$i_2 = \frac{V_2}{R_2}$$

Circuits (44)

- What is current i_3 through R_3 ?
- Can use same method of R_{eq} and V_{23}

OR

- Use junction rule

$$i_1 = i_2 + i_3$$

$$i_3 = i_1 - i_2$$

