

Lecture 28

Chapter 33

EM Oscillations and AC

Review

$$\oint \vec{B} \cdot d\vec{s} = \mu_0 \epsilon_0 \frac{d\Phi_E}{dt} + \mu_0 i_{enc}$$

- Can represent change in electric flux with a fictitious current called the displacement current, i_d

$$i_d = \epsilon_0 \frac{d\Phi_E}{dt}$$

- Ampere-Maxwell's law becomes

$$\oint \vec{B} \cdot d\vec{s} = \mu_0 i_{d,enc} + \mu_0 i_{enc}$$

Review

Maxwell's 4 equations are

- Gauss' Law $\oint \vec{E} \cdot d\vec{A} = \frac{q_{enc}}{\epsilon_0}$

- Gauss' Law for magnetism $\oint \vec{B} \cdot d\vec{A} = 0$

- Faraday's Law $\oint \vec{E} \cdot d\vec{s} = -\frac{d\Phi_B}{dt}$

- Ampere-Maxwell Law $\oint \vec{B} \cdot d\vec{s} = \mu_0 \epsilon_0 \frac{d\Phi_E}{dt} + \mu_0 i_{enc}$

EM Oscillations (1)

- In this chapter study an RLC circuit
- Review RC and RL circuits
- Charge, current and potential difference grow and decay exponentially given by time constant, τ_C or τ_L
- Look at LC circuit

EM Oscillations (2)

- RC circuit - resistor & capacitor in series
 - Charging up a capacitor




$$q = CE(1 - e^{-t/\tau_c})$$

- Discharging capacitor

$$q = q_0 e^{-t/\tau_c}$$

- where

$$\tau_c = RC$$

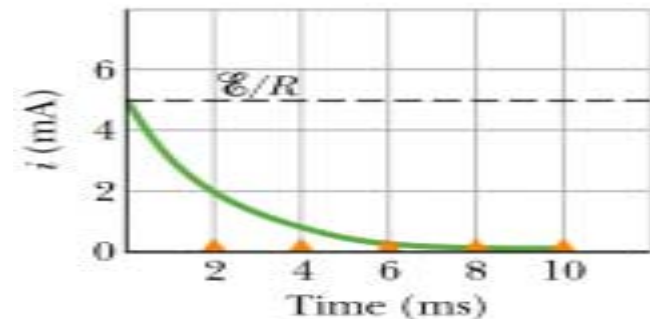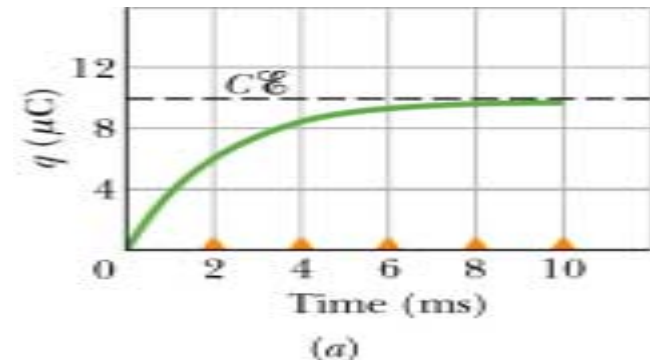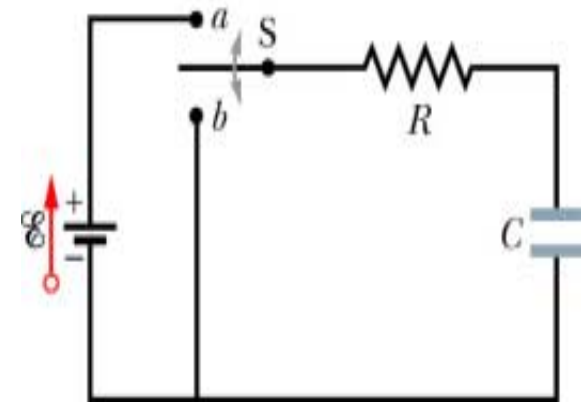

EM Oscillations (3)

- RL Circuit – resistor & inductor in series
 - Rise of current




$$i = \frac{E}{R} (1 - e^{-t/\tau_L})$$

- Decay of current

$$i = i_0 e^{-t/\tau_L}$$


- where

$$\tau_L = \frac{L}{R}$$

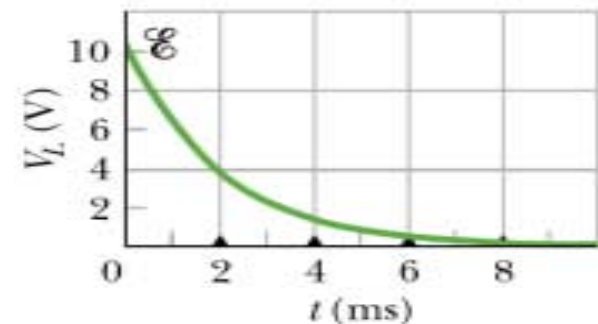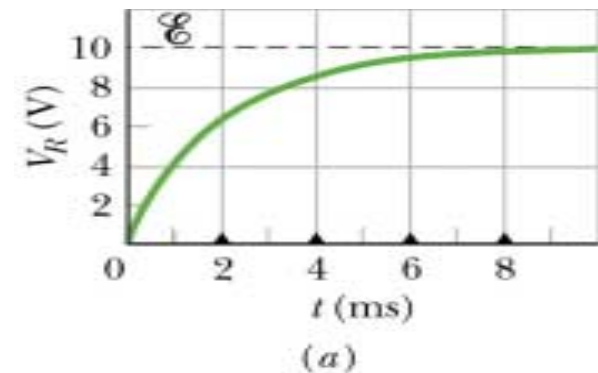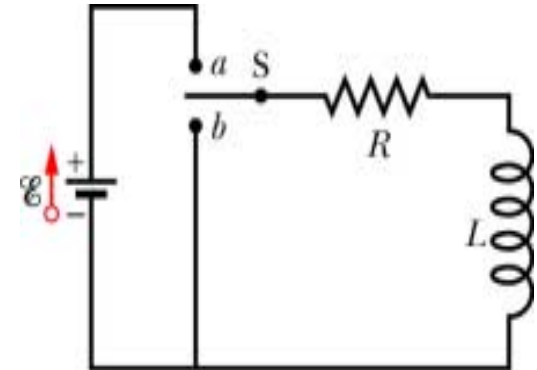

EM Oscillations (4)

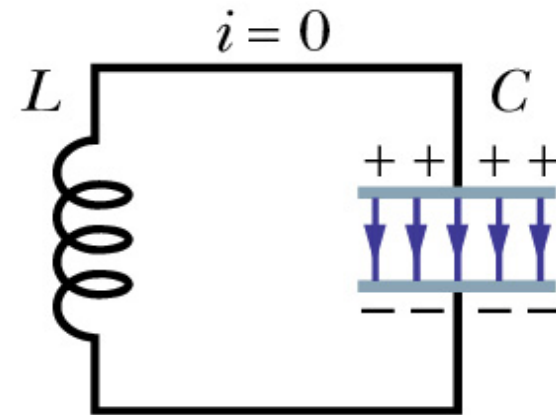
- LC Circuit – inductor & capacitor in series
- Find q , i and V vary sinusoidally with period T and angular frequency ω
- E field of capacitor and B field of inductor oscillate
- Called **Electromagnetic oscillations**
- Energy stored in E of capacitor and B of inductor



$$U_E = \frac{q^2}{2C}$$

$$U_B = \frac{Li^2}{2}$$

EM Oscillations (5)


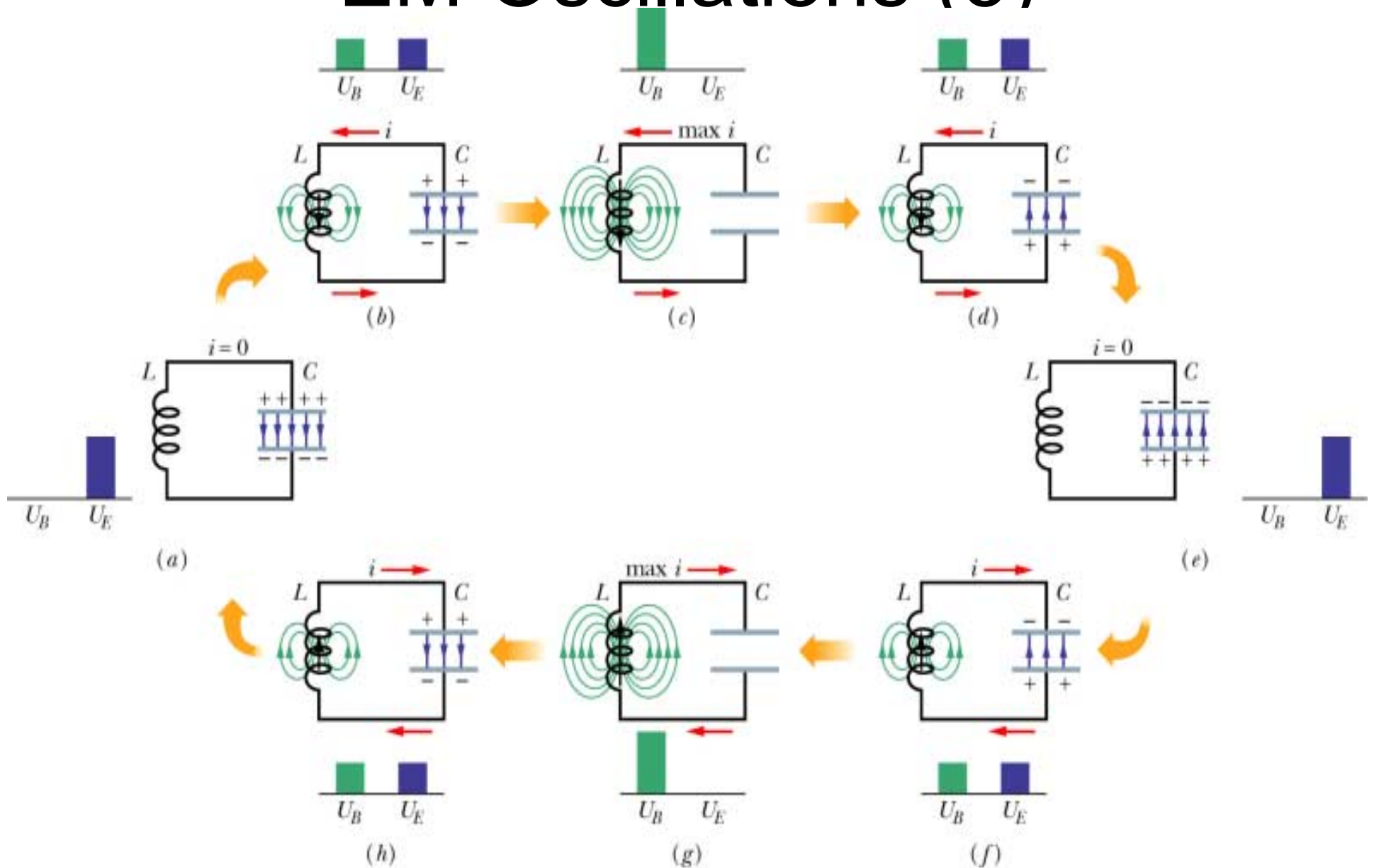


EM Oscillations (6)

- Cycle repeats at some frequency, f and thus angular frequency, ω

$$\omega = 2\pi f$$

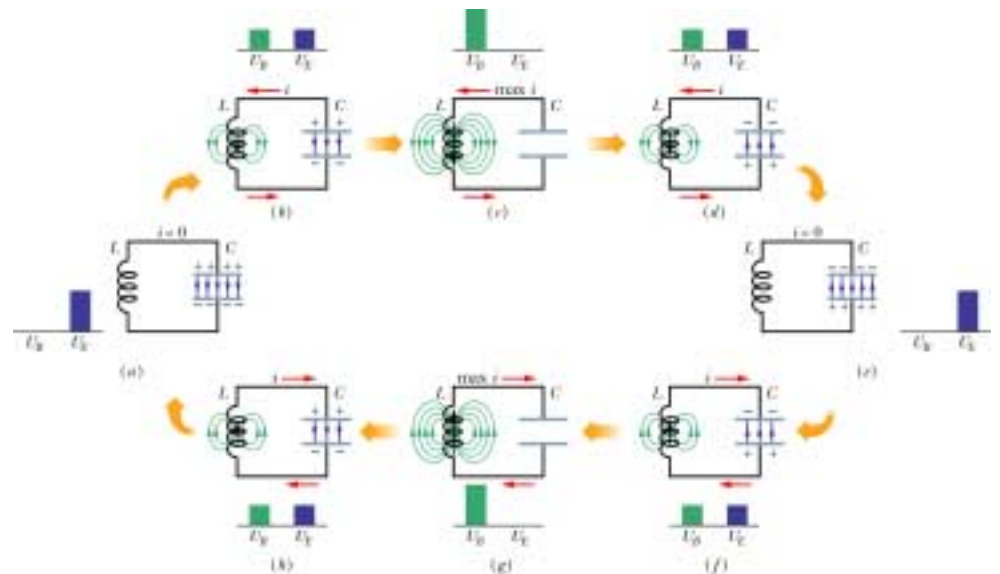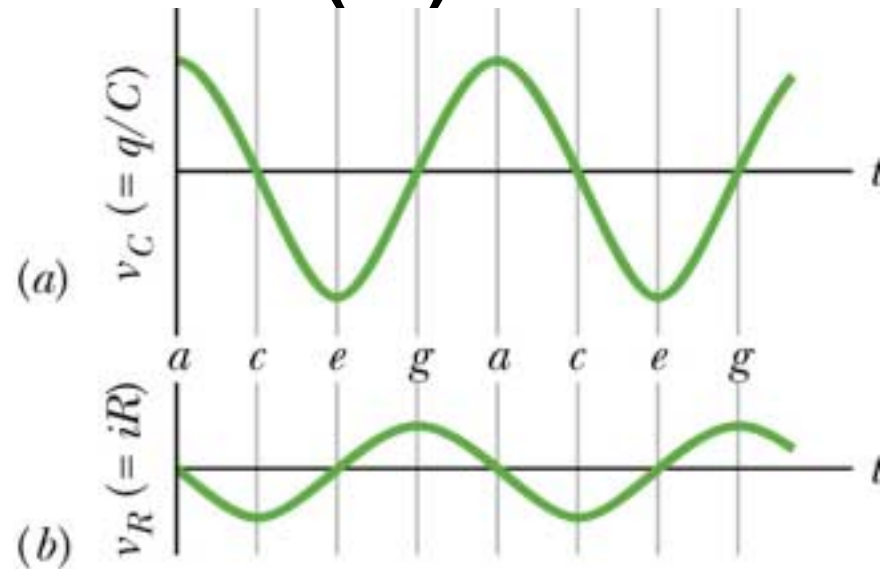- Ideal LC circuit, no R so oscillations continue indefinitely
- Real LC, oscillations die away as energy goes into heat in R



EM Oscillations (7)

- Checkpoint #1 – A charged capacitor & inductor are connected in series at time $t=0$. In terms of period, T , how much later will the following reach their maximums:

- q of capacitor

$T/2$

- V_C with original polarity


T

- Energy stored in E field

$T/2$

- The current

$T/4$

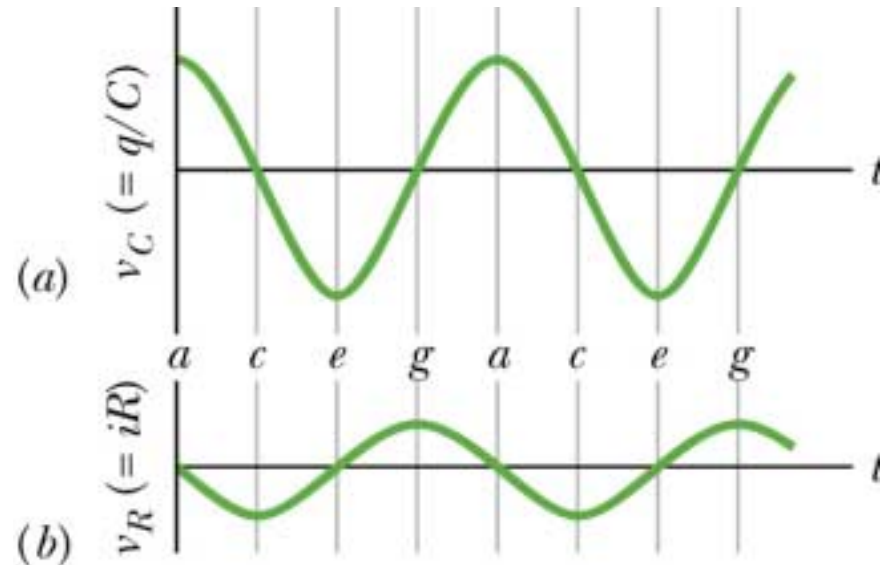



EM Oscillations (8)

- LC circuits analogous to block-spring system
- Total energy of block

$$U = \frac{1}{2}mv^2 + \frac{1}{2}kx^2$$

- Energy is conserved
- Differentiating gives

$$\frac{dU}{dt} = 0$$

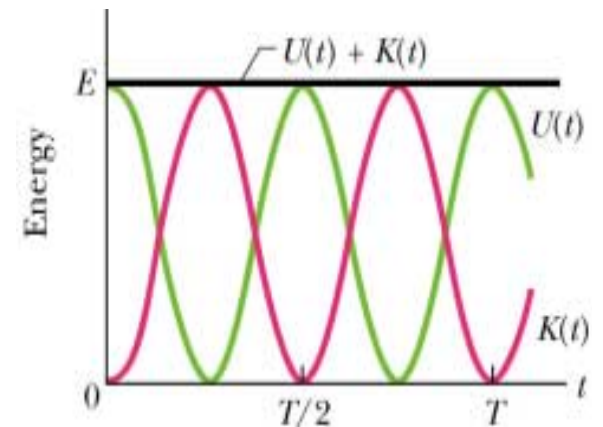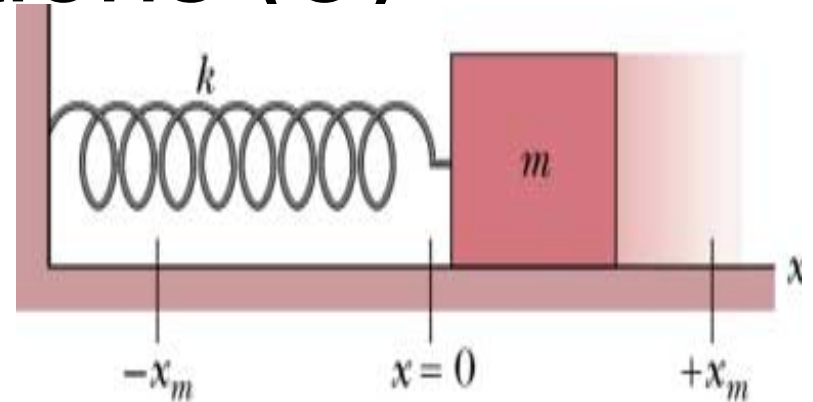

$$\frac{dU}{dt} = \frac{d}{dt} \left(\frac{1}{2}mv^2 + \frac{1}{2}kx^2 \right) = mv \frac{dv}{dt} + kx \frac{dx}{dt} = 0$$

EM Oscillations (9)

- Using

$$v = \frac{dx}{dt}$$

$$\frac{dv}{dt} = \frac{d^2 x}{dt^2}$$

- Substitute

$$mv \frac{dv}{dt} + kx \frac{dx}{dt} = mv \frac{d^2 x}{dt^2} + kxv = 0$$

- Gives

$$m \frac{d^2 x}{dt^2} + kx = 0$$

- Solution is

$$x = X \cos(\omega t + \phi)$$

- X is the amplitude
- ω is the angular frequency
- ϕ is the phase constant

$$\omega = \sqrt{\frac{k}{m}}$$

EM Oscillations (10)

- Total energy of LC circuit


$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}$$

- Total energy is constant

$$\frac{dU}{dt} = 0$$

- Differentiating gives
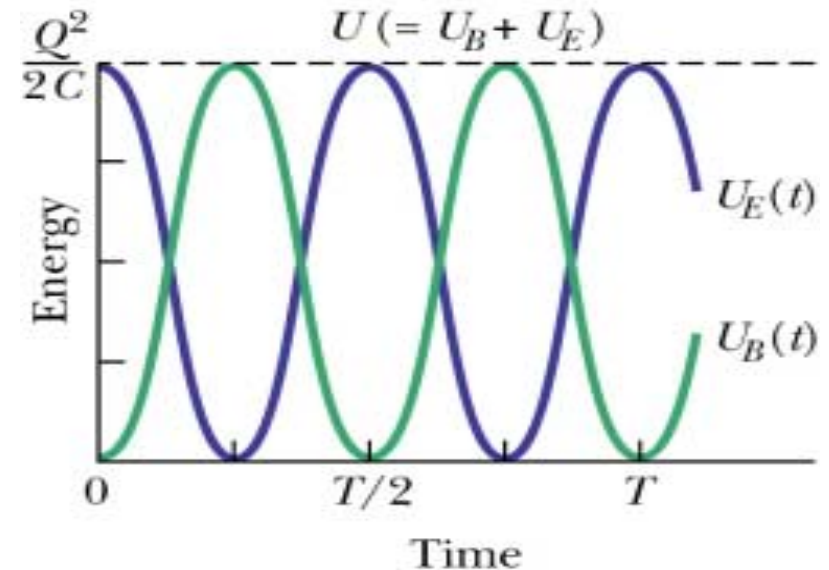
$$\frac{dU}{dt} = \frac{d}{dt} \left(\frac{Li^2}{2} + \frac{q^2}{2C} \right) = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = 0$$



EM Oscillations (11)

- Using

$$i = \frac{dq}{dt} \quad \frac{di}{dt} = \frac{d^2q}{dt^2}$$

- Substitute

$$Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = Li \frac{d^2q}{dt^2} + \frac{q}{C} i = 0$$

- Equation same form as
block and spring

$$L \frac{d^2q}{dt^2} + \frac{1}{C} q = 0$$

- Solution is

$$q = Q \cos(\omega t + \phi)$$

- Q is the amplitude
- ω is the angular frequency
- ϕ is the phase constant

EM Oscillations (12)

- Charge of LC circuit

$$q = Q \cos(\omega t + \phi)$$

- Find current by


$$i = \frac{dq}{dt}$$

$$i = \frac{d}{dt} [Q \cos(\omega t + \phi)] = -Q\omega \sin(\omega t + \phi)$$

- Amplitude I is

$$I = \omega Q$$

$$i = -I \sin(\omega t + \phi)$$

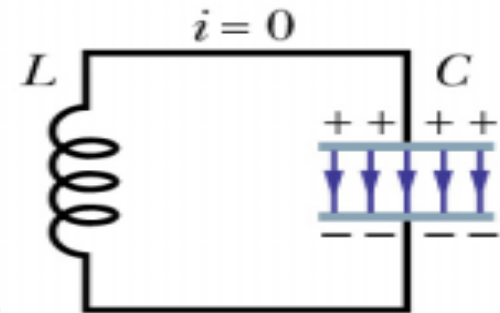

EM Oscillations (13)

- What is ω for an LC circuit?

$$q = Q \cos(\omega t + \phi)$$

$$\frac{d^2 q}{dt^2} = -\omega^2 Q \cos(\omega t + \phi)$$

- Substitute into

$$L \frac{d^2 q}{dt^2} + \frac{1}{C} q = 0$$

$$-L\omega^2 Q \cos(\omega t + \phi) + \frac{1}{C} Q \cos(\omega t + \phi) = 0$$

- Find ω for LC circuit is

$$\omega = \sqrt{\frac{1}{LC}}$$

EM Oscillations (14)

- The phase constant, ϕ , is determined by conditions at any certain time, t


$$q = Q \cos(\omega t + \phi)$$

$$i = -I \sin(\omega t + \phi)$$

- If $\phi = 0$ at $t = 0$ then

$$q = Q$$

$$i = 0$$

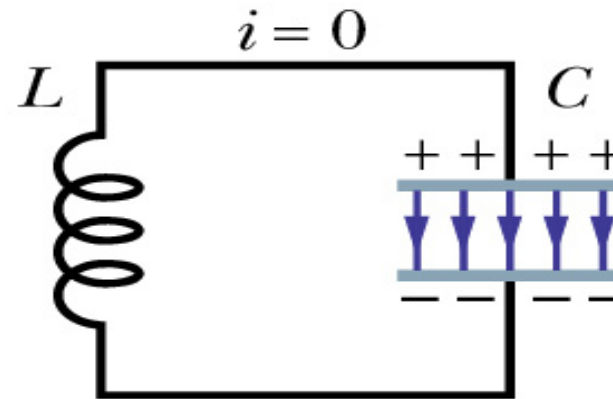

EM Oscillations (15)

- The energy stored in an LC circuit at any time, t

$$U = U_B + U_E$$

- Substitute $q = Q \cos(\omega t + \phi)$ $i = -I \sin(\omega t + \phi)$

$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2(\omega t + \phi)$$

$$U_B = \frac{Li^2}{2} = \frac{L}{2} \omega^2 Q^2 \sin^2(\omega t + \phi)$$

- Using

$$\omega = \sqrt{\frac{1}{LC}}$$


$$U_B = \frac{Q^2}{2C} \sin^2(\omega t + \phi)$$

EM Oscillations (16)

- For the case where $\phi = 0$

$$U_E = \frac{Q^2}{2C} \cos^2(\omega t + \phi)$$
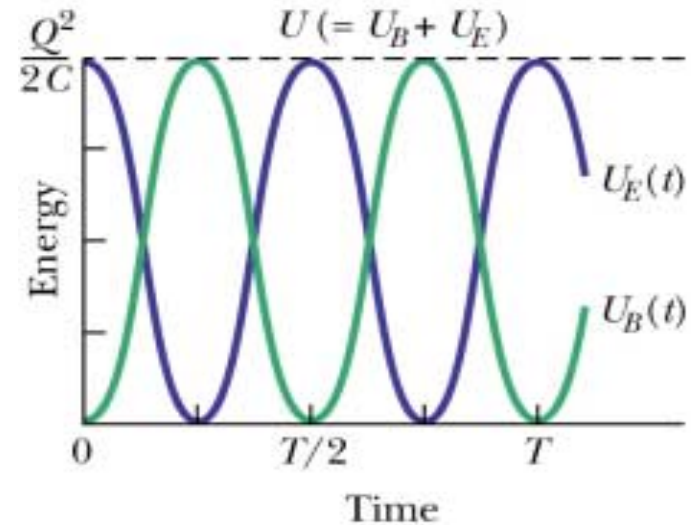
$$U_B = \frac{Q^2}{2C} \sin^2(\omega t + \phi)$$




- Maximum value for both

$$U_{E,\max} = U_{B,\max} = Q^2 / 2C$$

- At any instant, sum is $U = U_B + U_E = Q^2 / 2C$
- When $U_E = \max$, $U_B = 0$, and conversely, when $U_B = \max$, $U_E = 0$

EM Oscillations (17)

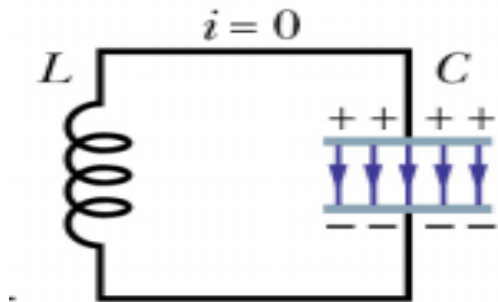- Checkpoint #2 – Capacitor in LC circuit has $V_{C,max} = 17V$ and $U_{E,max} = 160\mu J$. When capacitor has $V_C = 5V$ and $U_E = 10\mu J$, what are the a) emf across the inductor and b) the energy stored in the B field, U_B ?
- Can apply the loop rule
 - Net potential difference around the circuit must be zero



$$v_L(t) = v_C(t)$$



$$\text{A) } v_L = 5V$$

$$U_{E,max} = U_E(t) + U_B(t)$$

$$\text{B) } U_B = 160 - 10 = 150\mu J$$

EM Oscillations (18)

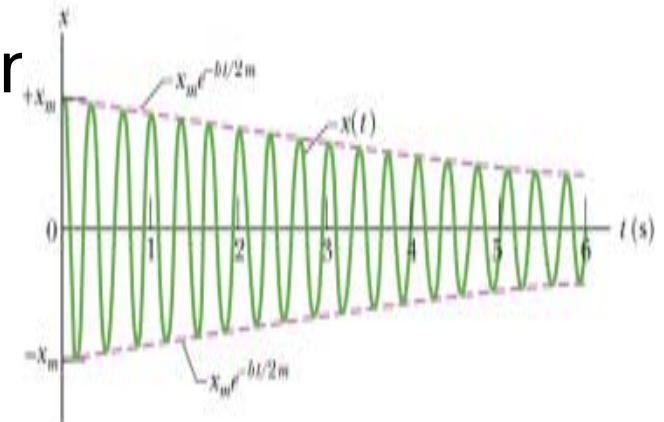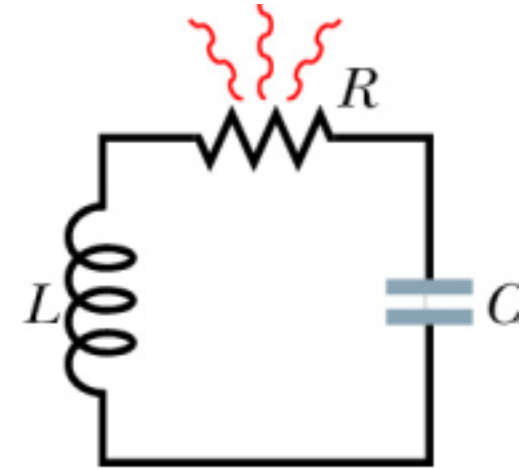- Consider a RLC circuit – resistor, inductor and capacitor in series
- Total electromagnetic energy, $U = U_E + U_B$, is no longer constant
- Energy decreases with time as it is transferred to thermal energy in the resistor
- Oscillations in q , i and V are **damped**
 - Same as damped block and spring




EM Oscillations (19)

- Resistor does not store electromagnetic energy so total energy at any time is

$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}$$

- Rate of transfer to thermal energy is (minus sign means U is decreasing)
- Differentiating gives
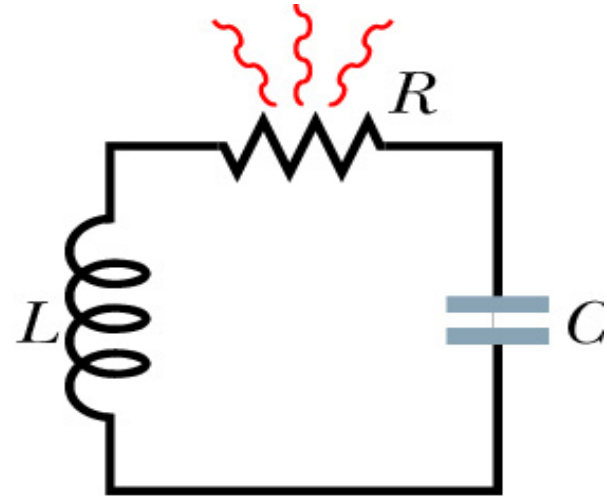
$$\frac{dU}{dt} = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = -i^2 R$$



$$\frac{dU}{dt} = -i^2 R$$

EM Oscillations (20)

$$\frac{dU}{dt} = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = -i^2 R$$

- Use relations $i = \frac{dq}{dt}$ $\frac{di}{dt} = \frac{d^2 q}{dt^2}$

- Differential equation for damped RLC circuit is

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0$$

- Solution

$$q = Q e^{-Rt/2L} \cos(\omega' t + \phi)$$

EM Oscillations (21)

$$q = Qe^{-Rt/2L} \cos(\omega't + \phi)$$

- Where $\omega' = \sqrt{\omega^2 - (R/2L)^2}$ $\omega = \sqrt{\frac{1}{LC}}$
- Charge in RLC circuit is sinusoidal but with an exponentially decaying amplitude $Qe^{-Rt/2L}$
- Damped angular frequency, ω' , is always less than ω of the undamped oscillations

EM Oscillations (22)

$$q = Qe^{-Rt/2L} \cos(\omega't + \phi)$$

- Find U_E as function of time

$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} e^{-Rt/L} \cos^2(\omega't + \phi)$$

- Total energy decreases as

$$U_{tot} = \frac{Q^2}{2C} e^{-Rt/L}$$