

Lecture 29



Chapter 33

EM Oscillations and AC

Review

- RL and RC circuits
 - Charge, current, and potential grow and decay exponentially
- LC circuit
 - Charge, current, and potential grow and decay sinusoidally – electromagnetic oscillations
 - Total electromagnetic energy is
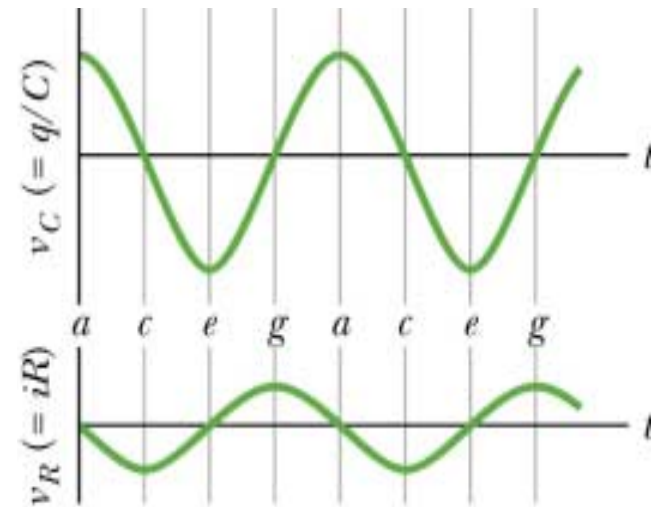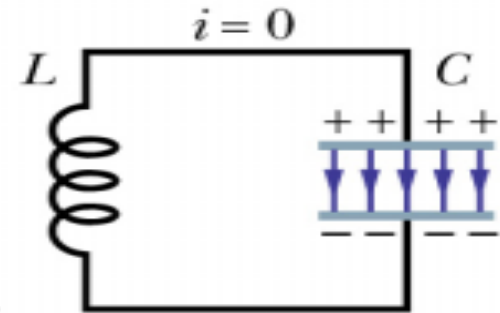
$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}$$



Review

- Ideal LC circuit

$$\frac{dU}{dt} = 0$$

- Total energy conserved
- Solved differential equation to find

$$q = Q \cos(\omega t + \phi)$$

$$i = -I \sin(\omega t + \phi)$$

$$\omega = \sqrt{\frac{1}{LC}}$$


- Substituting q and i into energy equations

$$U_E = \frac{Q^2}{2C} \cos^2(\omega t + \phi)$$

$$U_B = \frac{Q^2}{2C} \sin^2(\omega t + \phi)$$

$$U = U_B + U_E = Q^2 / 2C$$

Review

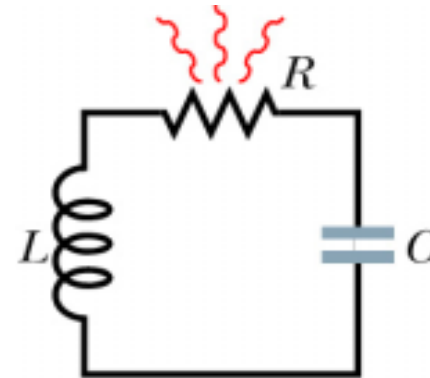

- RLC circuit
 - Energy is no longer conserved, becomes thermal energy in resistor
 - Oscillations are damped
 - Solved differential equation to find

$$\frac{dU}{dt} = -i^2 R$$

$$q = Q e^{-Rt/2L} \cos(\omega' t + \phi)$$

$$\omega = \sqrt{\frac{1}{LC}}$$

$$\omega' = \sqrt{\omega^2 - (R/2L)^2}$$

If R is very small

$$\omega' = \omega$$

- Energy decreases as

$$U_E = \frac{Q^2}{2C} e^{-Rt/L} \cos^2(\omega' t + \phi)$$


$$U_{tot} = \frac{Q^2}{2C} e^{-Rt/L}$$

EM Oscillations (23)

- LC and RLC circuits with no external emf
 - Free oscillations with **natural frequency, ω**

$$\omega = \sqrt{\frac{1}{LC}}$$

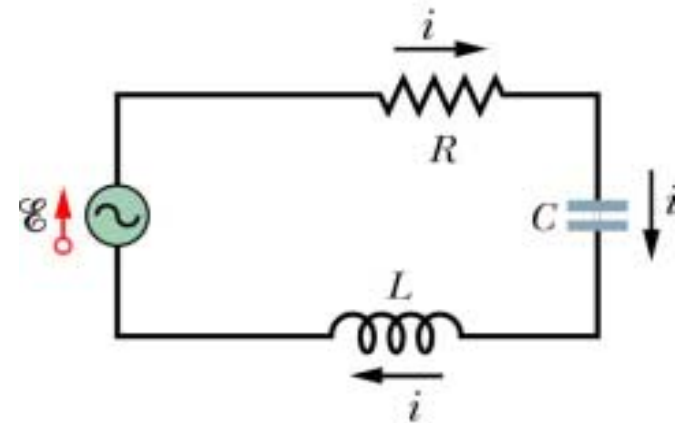
- Add external emf (e.g. ac to RLC circuit)
 - Oscillations said to be **or forced**
 - Oscillations occur at **driving frequency, ω_d**
 - When **$\omega_d = \omega$, called resonance**, current amplitude, I , is maximum



the

EM Oscillations (24)

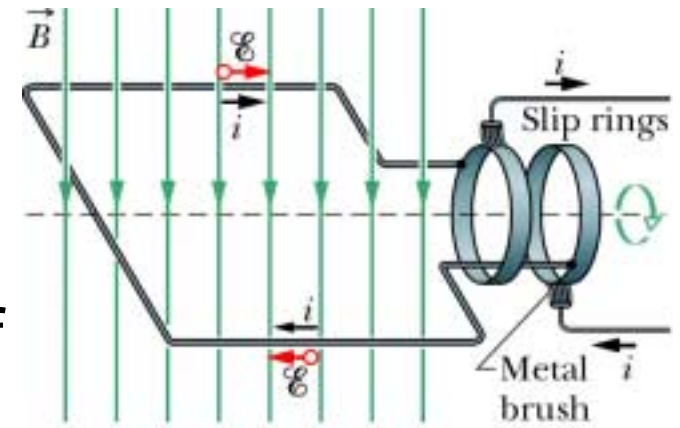
- **ac generator** – mechanically turn loop in B field, induces a current and therefore an emf
- Used Faraday's law to find emf



$$E = -N \frac{d\Phi_B}{dt} = NBA \omega \sin \omega t$$

$$E_{\max} = NBA \omega$$


$$E = E_{\max} \sin \omega t$$

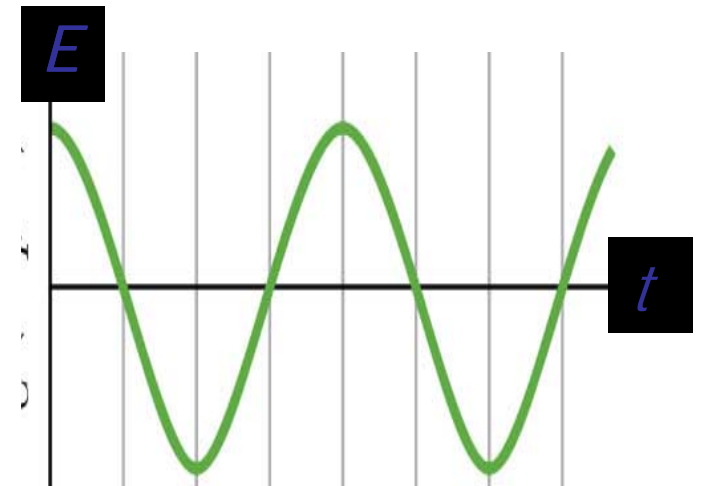

EM Oscillations (25)

$$E = E_m \sin \omega_d t$$

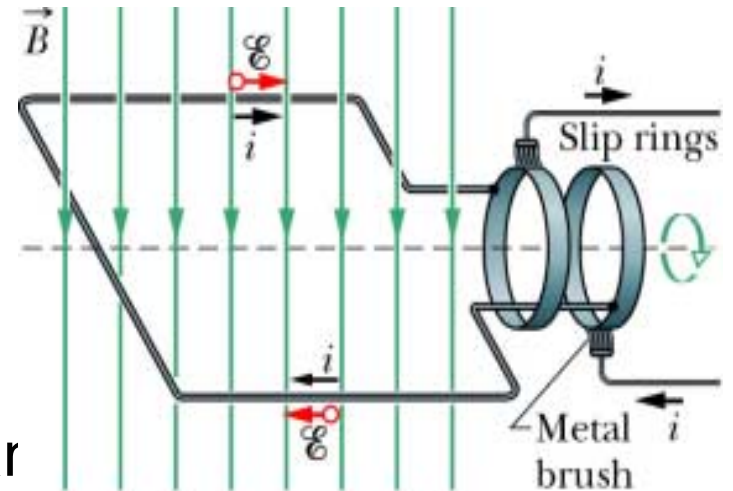- Driving angular frequency, ω_d is equal to angular speed that loop rotates in B field
 - The phase of the emf is $\omega_d t$
 - Amplitude is E_m where m star for maximum
- Current of ac generator where ϕ corresponds to phase difference between the current and emf



$$\omega_d = 2\pi f_d$$

$$i = I \sin(\omega_d t - \phi)$$

- I is amplitude
- Minus sign historical

EM Oscillations (26)

- Purely **resistive load**
- Apply loop rule


$$E - v_R = 0$$

- Using

$$E = E_m \sin \omega_d t$$

- Substitute

$$v_R = E_m \sin \omega_d t$$

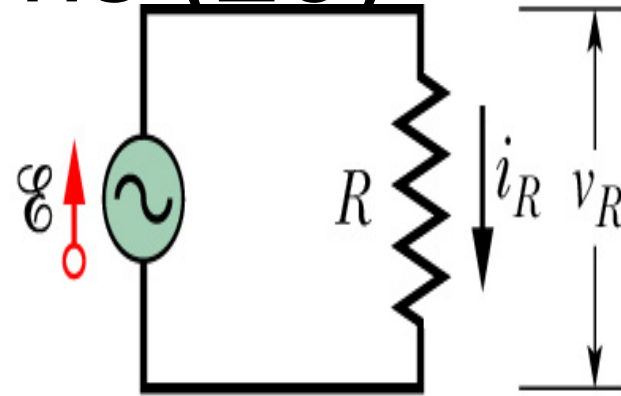

- Amplitude across resistor is same as across emf

$$E_m = V_R$$

- Rewrite v_R as

$$v_R = V_R \sin \omega_d t$$


EM Oscillations (27)

- Use definition of resistance to find i_R


$$R = \frac{V_R}{I_R}$$

$$v_R = V_R \sin \omega_d t$$
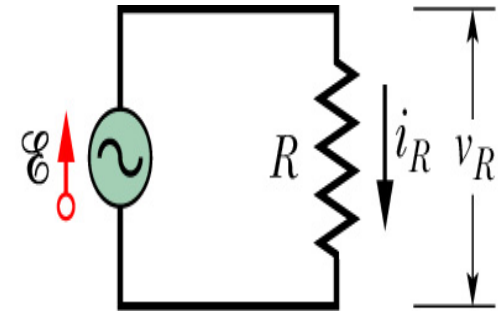
$$i_R = \frac{v_R}{R} = \frac{V_R}{R} \sin \omega_d t$$



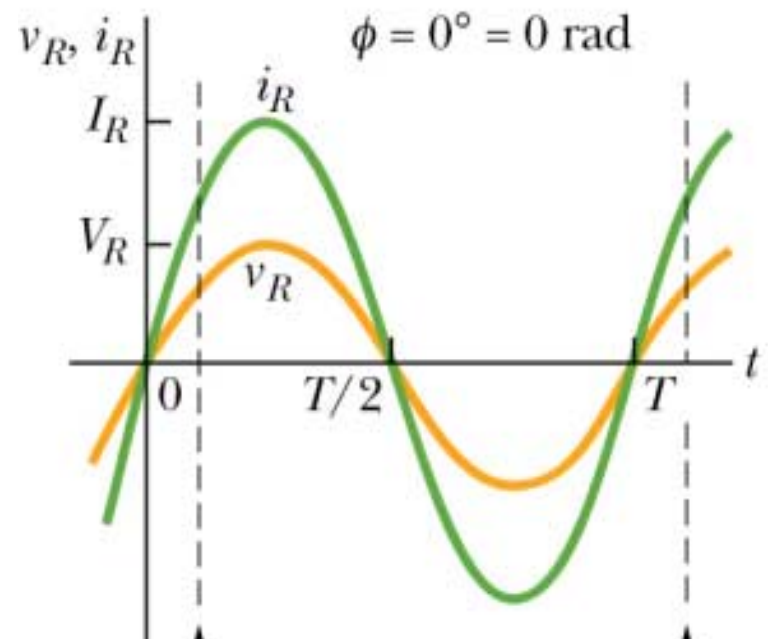- Voltage and current** are functions of $\sin(\omega_d t)$ with $\phi = 0$ so **are in phase**
- No damping of v_R and i_R , generator supplies energy




EM Oscillations (28)

- Compare i_R to i for emf

$$i_R = \frac{v_R}{R} = \frac{V_R}{R} \sin \omega_d t$$

$$i_{emf} = i_R = I_R \sin(\omega_d t - \phi)$$

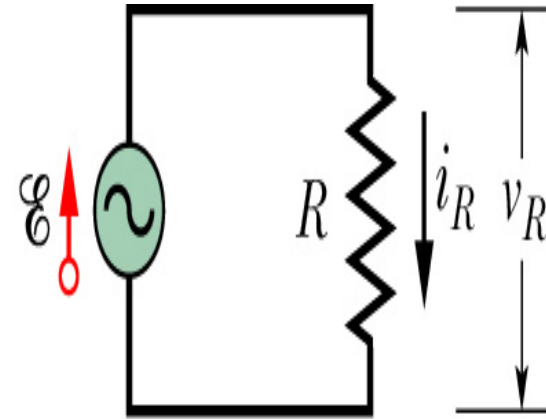- For purely resistive load the phase constant $\phi = 0$
- Voltage amplitude is related to current amplitude



$$I_R = \frac{V_R}{R}$$

$$V_R = I_R R$$

EM Oscillations (29)

- Purely **capacitive load**
- Apply loop rule


$$E - v_C = 0$$

- Using

$$E = E_m \sin \omega_d t$$

- Substitute

$$v_C = E_m \sin \omega_d t$$

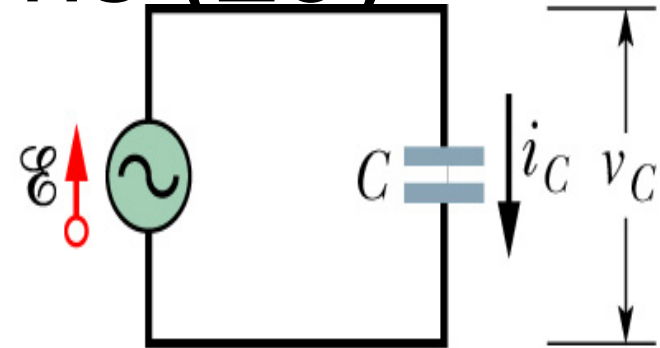

- Amplitude across capacitor is same as across emf

$$E_m = V_C$$

- Rewrite v_C as

$$v_C = V_C \sin \omega_d t$$

EM Oscillations (30)

- Use definition of capacitance

$$q_C = Cv_C$$

$$q_C = Cv_C = CV_C \sin \omega_d t$$


- Use definition of current and differentiate

$$i = \frac{dq}{dt}$$

$$i_C = \frac{dq_C}{dt} = \omega_d CV_C \cos \omega_d t$$

- Replace cosine term with a phase-shifted sine term

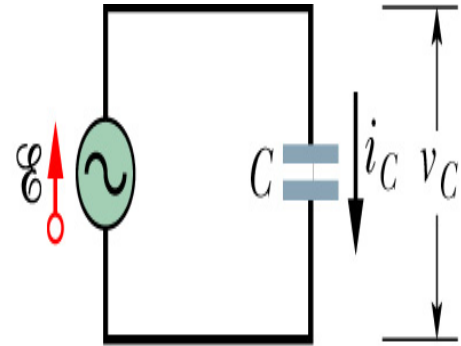
$$\cos \omega_d t = \sin(\omega_d t + 90^\circ)$$




EM Oscillations (31)

- Compare v_C and i_C of capacitor $v_C = V_C \sin \omega_d t$

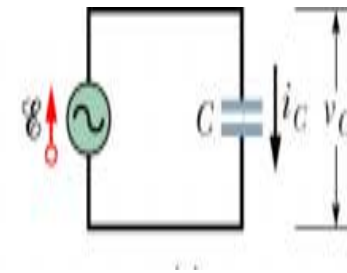
$$i_C = \omega_d C V_C \sin(\omega_d t + 90^\circ)$$



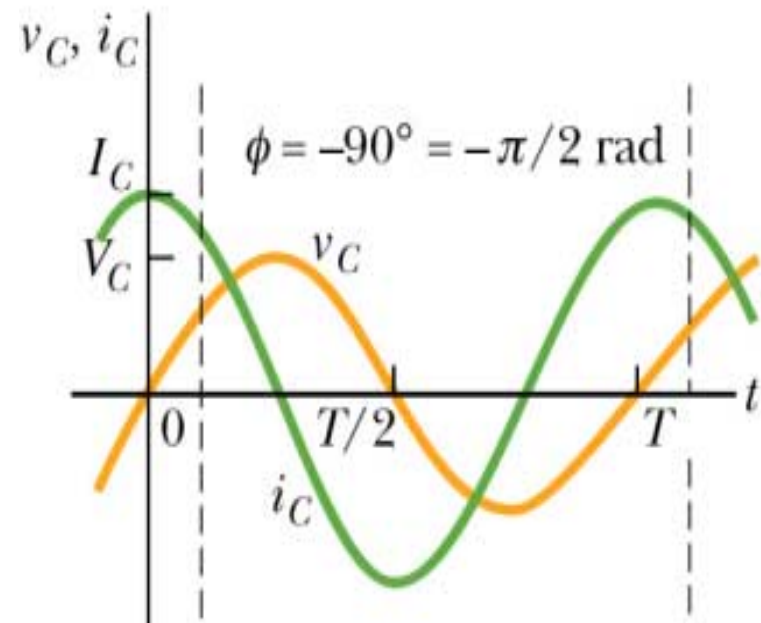- Voltage and current are out of phase by 90°
- Current leads voltage
 - Current reaches its max before voltage does by a quarter cycle or $T/4$



EM Oscillations (32)

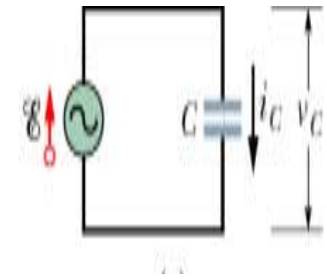

- Now compare currents

$$i_C = \omega_d C V_C \sin(\omega_d t + 90^\circ) \quad i_{emf} = i_C = I_C \sin(\omega_d t - \phi)$$

- For purely capacitive load phase $\phi = -90^\circ$
- V_C amplitude is related to I_C amplitude

$$I_C = \omega_d C V_C \quad V_C = I_C \frac{1}{\omega_d C} = I_C X_C$$

- X_C is the **capacitive reactance** and has SI unit of ohm, Ω just like resistance

$$V_C = I_C X_C$$

$$X_C = \frac{1}{\omega_d C}$$

EM Oscillations (33)

- Purely inductive load
- Apply loop rule


$$E - v_L = 0$$

- Using

$$E = E_m \sin \omega_d t$$

- Substitute

$$v_L = E_m \sin \omega_d t$$

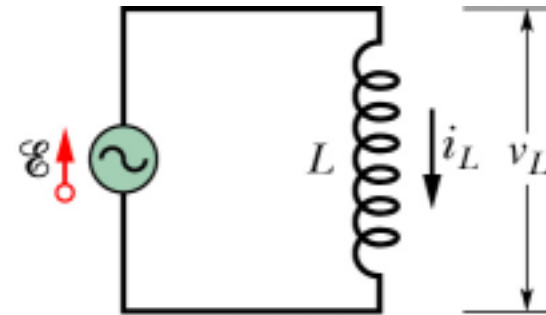

- Amplitude across inductor is same as across emf

$$E_m = V_L$$

- Rewrite v_L as

$$v_L = V_L \sin \omega_d t$$

EM Oscillations (34)


- Self-induced emf across an inductor is

$$E_L = v_L = L \frac{di}{dt}$$

- Relate

$$v_L = V_L \sin \omega_d t = L \frac{di}{dt}$$
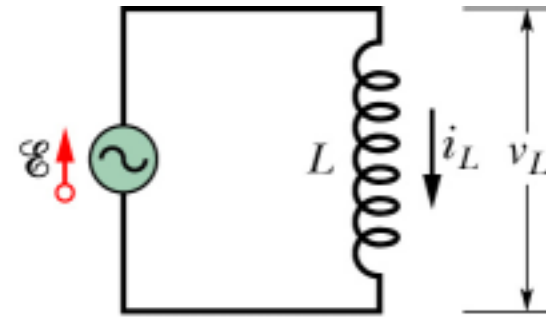
$$\frac{di}{dt} = \frac{V_L}{L} \sin \omega_d t$$




- Want current so integrate

$$i_L = \int di_L = \frac{V_L}{L} \int \sin \omega_d t dt = - \left(\frac{V_L}{\omega_d L} \right) \cos \omega_d t$$

EM Oscillations (35)

- Replace -cosine with a phase-shifted sine term

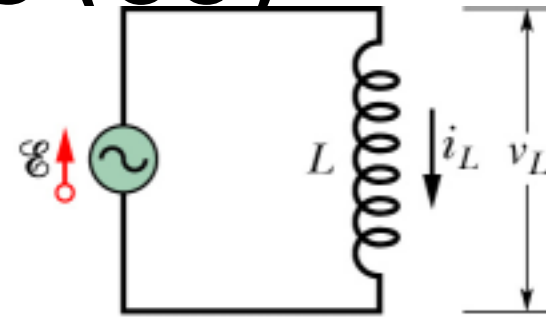
$$-\cos \omega_d t = \sin(\omega_d t - 90^\circ)$$




$$i_L = -\left(\frac{V_L}{\omega_d L}\right) \cos \omega_d t = \frac{V_L}{\omega_d L} \sin(\omega_d t - 90^\circ)$$

$$v_L = V_L \sin \omega_d t$$

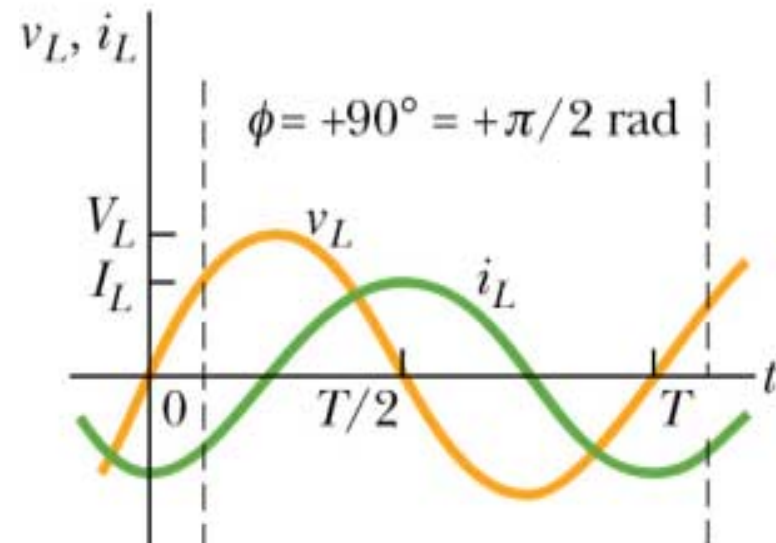- Compare i_L to v_L
- i_L and v_L are 90° out of phase
- Current lags voltage
 - i_L reaches max after v_L by a quarter cycle or $T/4$



EM Oscillations (36)

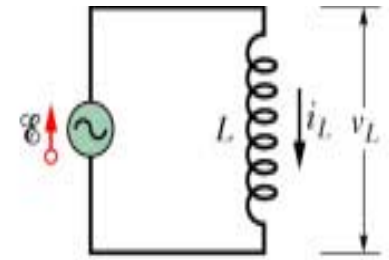

- Now compare currents

$$i_L = \frac{V_L}{\omega_d L} \sin(\omega_d t - 90^\circ)$$

$$i_{emf} = i_L = I_L \sin(\omega_d t - \phi)$$

- For purely inductive load phase $\phi = +90^\circ$
- V_L amplitude is related to I_L amplitude

$$I_L = \frac{V_L}{\omega_d L}$$

$$V_L = I_L \omega_d L = I_L X_L$$

- X_L is the inductive reactance and has SI unit of ohm, Ω just like resistance R

$$V_L = I_L X_L$$

$$X_L = \omega_d L$$

EM Oscillations (37)

Element	Reactance /	Phase of Current	Phase angle ϕ	Amplitude Relation
Resistor	Resistance R	In phase	0°	$V_R = I_R R$
Capacitor	$X_C = 1/\omega_d C$	Leads v_C (ICE)	-90°	$V_C = I_C X_C$
Inductor	$X_L = \omega_d L$	Lags v_L (ELI)	$+90^\circ$	$V_L = I_L X_L$

- **ELI the ICE man**

- Voltage or emf (E) before current (I) in an inductor (L)
- Current (I) before voltage or emf (E) in capacitor (C)

EM Oscillations (38)

- Checkpoints #3, 5, & 6 – If the driving frequency, ω_d , in a circuit is increased does the amplitude voltage and amplitude current increase, decrease or remain the same?
- For purely resistive circuit
- From loop rule $V_R = E_m$
- So amplitude voltage, V_L stays the same
- I_R also stays the same - only depends on R

$$I_R = \frac{V_R}{R}$$

I_R

EM Oscillations (39)

- Checkpoints #3, 5, & 6 – If the driving frequency, ω_d , in a circuit is increased does the amplitude voltage and amplitude current increase, decrease or remain the same?
- For purely capacitive circuit
- From loop rule $V_C = E_m$
- So amplitude voltage, V_C stays the same
- I_C depends on X_C which depends on ω_d by
- So I_C increases

$$I_C = \frac{V_C}{X_C} = \omega_d C V_C$$

EM Oscillations (40)

- Checkpoints #3, 5, & 6 – If the driving frequency, ω_d , in a circuit is increased does the amplitude voltage and amplitude current increase, decrease or remain the same?
- For purely inductive circuit
- From loop rule $V_L = E_m$
- So amplitude voltage, V_L stays the same
- I_L depends on X_L which depends on ω_d by
- So I_L decreases

$$I_L = \frac{V_L}{X_L} = \frac{V_L}{\omega_d L}$$