

Lecture 30

Chapter 33

EM Oscillations and AC

Review

- Characterized ideal LC circuit
 - Charge, current and voltage vary sinusoidally
- Added resistance to LC circuit
 - Oscillations become damped
 - Charge, current and voltage still vary sinusoidally but decay exponentially
- Added ac generator to circuits with just a
 - Resistor
 - Capacitor
 - Inductor

Review

| Element | Reactance / Resistance | Phase of Current | Phase angle ϕ | Amplitude Relation |
|-----------|------------------------------|----------------------|-----------------------|-----------------------|
| Resistor | R | In phase | 0° | $V_R = I_R R$ |
| Capacitor | $X_C = 1/\omega_d C$ | Leads v_C (ICE) | -90° | $V_C = I_C X_C$ |
| Inductor | $X_L = \omega_d L$ | Lags v_L (ELI) | $+90^\circ$ | $V_L = I_L X_L$ |

- **ELI the ICE man**


- Voltage or emf (E) before current (I) in an inductor (L)
- Current (I) before voltage or emf (E) in capacitor (C)

EM Oscillations (41)

- RLC circuit – resistor, capacitor and inductor in series

- Apply alternating emf

$$E = E_m \sin \omega_d t$$

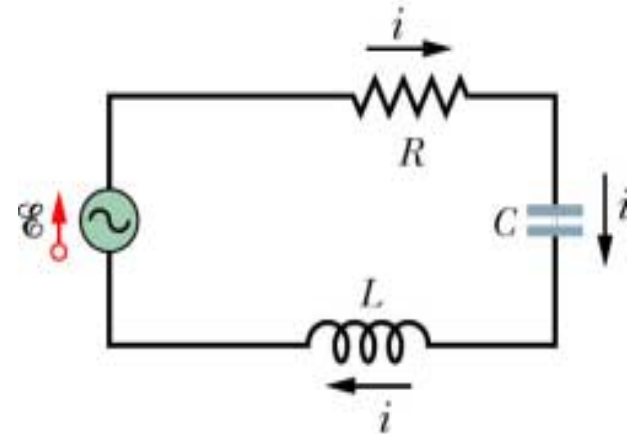

- Elements are in series so same current is driven through each

$$i = I \sin(\omega_d t - \phi)$$



- From the loop rule, at any time t , the sum of the voltages across the elements must

$$E = v_R + v_C + v_L$$

EM Oscillations (42)



- Want to find amplitude I and the phase constant ϕ
- Using phasors, represent the current at time t
 - Length is amplitude I
 - Projection on vertical axis is current i at time t
 - Angle of rotation is the phase at time t

$$\omega_d t - \phi$$

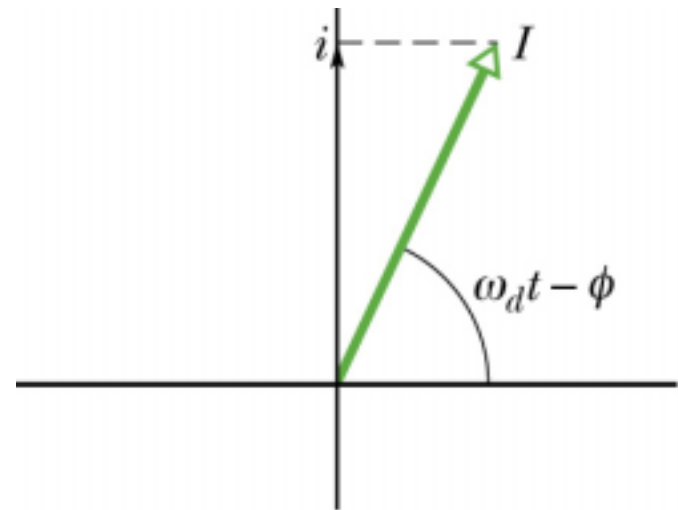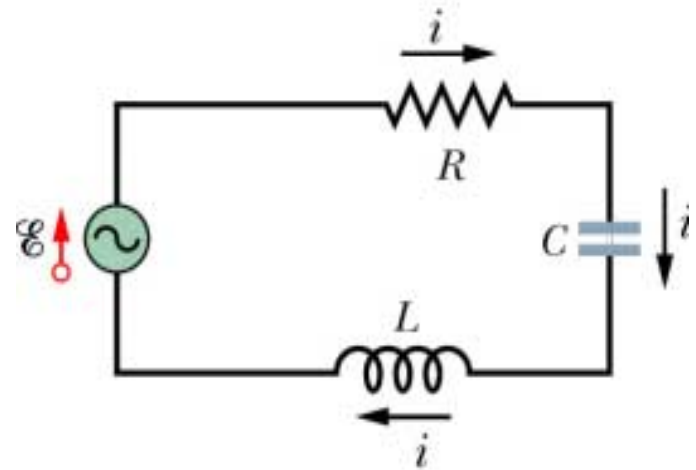

EM Oscillations (43)

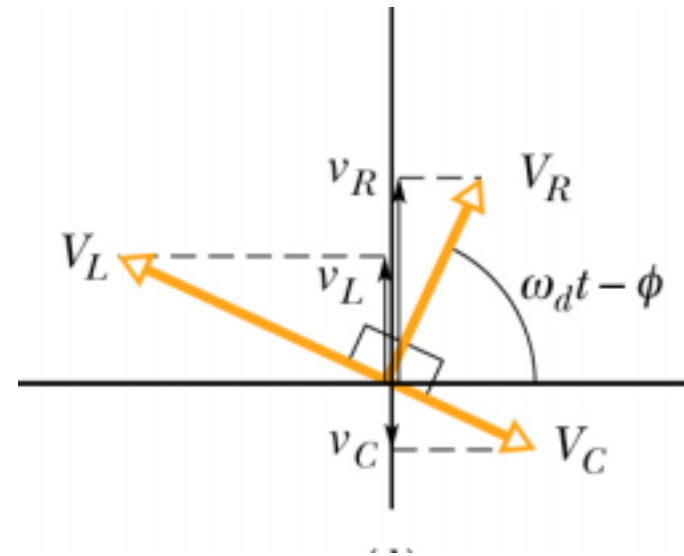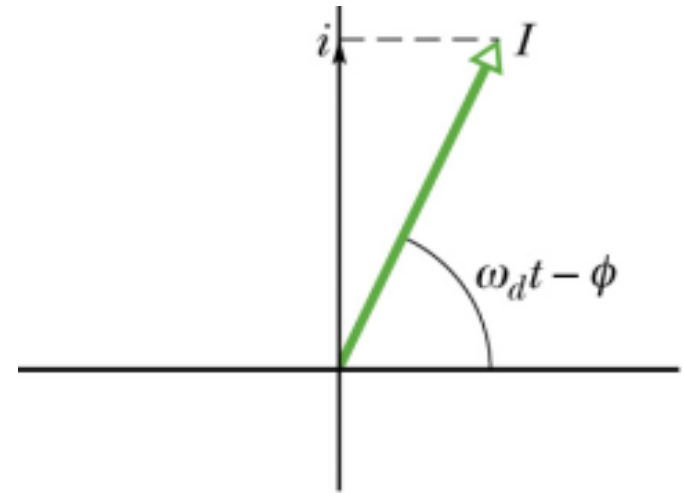- Draw phasors for voltages of R , C and L at same time t
- Orient V_R , V_L , & V_C phasors relative to current phasor
- Resistor – V_R and I are in phase
- Inductor – (ELI) V_L is ahead of I by 90°
- Capacitor – (ICE) I is ahead of V_C by 90°
- V_R , V_C , & v_L are projections





EM Oscillations (44)

- Draw phasor for applied emf

$$E = E_m \sin \omega_d t$$

- Length is amplitude E_m
- Projection is E at time t
- Angle is phase of emf $\omega_d t$
- From loop rule the projection $E =$ the algebraic sum of projections v_R , v_L & v_C

$$E = v_R + v_C + v_L$$

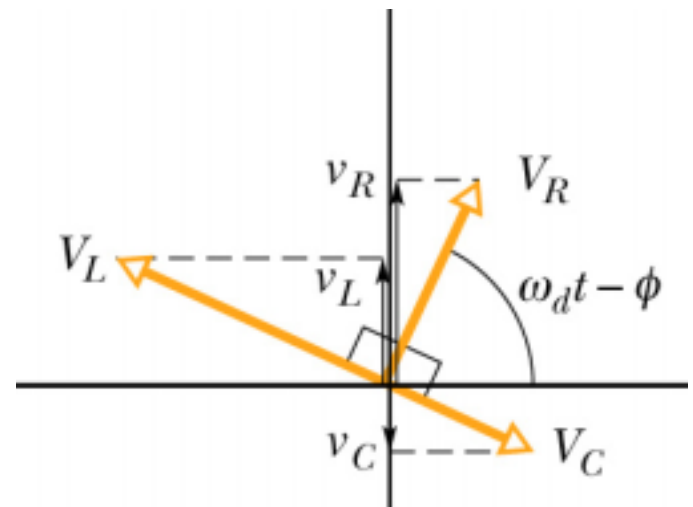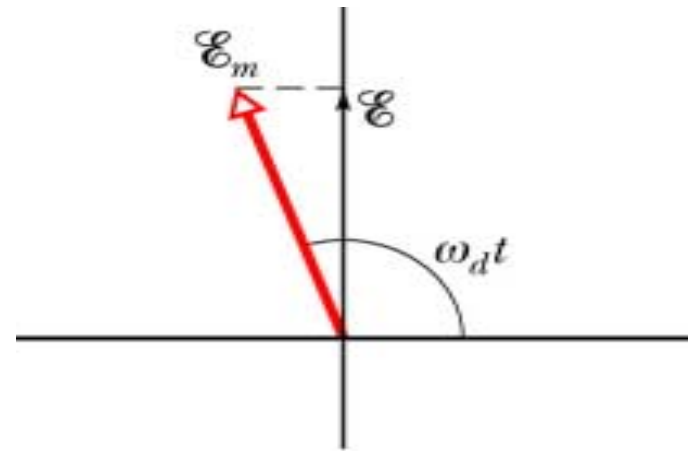

EM Oscillations (45)



$$E = v_R + v_C + v_L$$

- Phasors rotate together so equality always holds
- Phasor $E_m =$ vector sum of voltage phasors

$$\vec{E}_m = \vec{V}_R + \vec{V}_C + \vec{V}_L$$

- Combine V_L & V_C to form single phasor


$$V_L - V_C$$

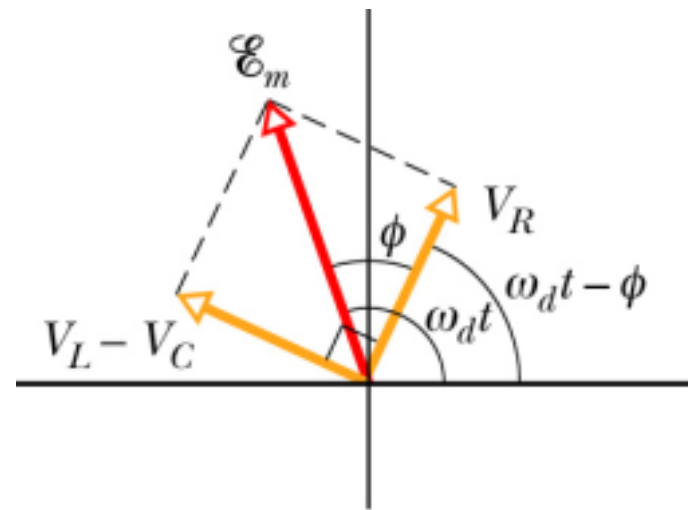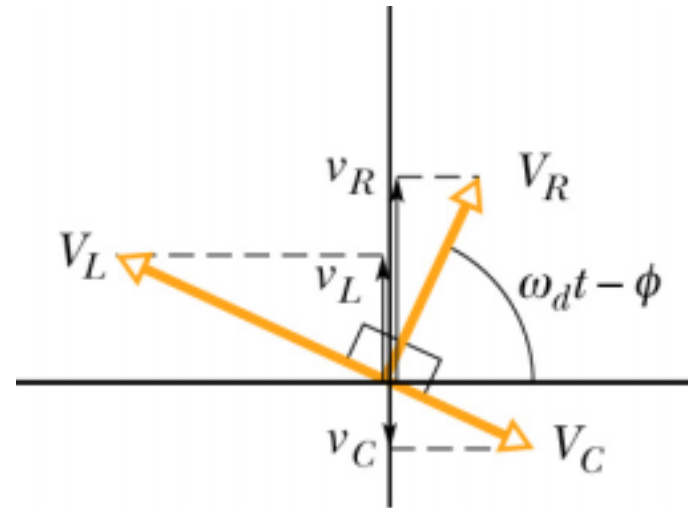

EM Oscillations (46)

- Using Pythagorean theorem

$$E_m^2 = V_R^2 + (V_L - V_C)^2$$

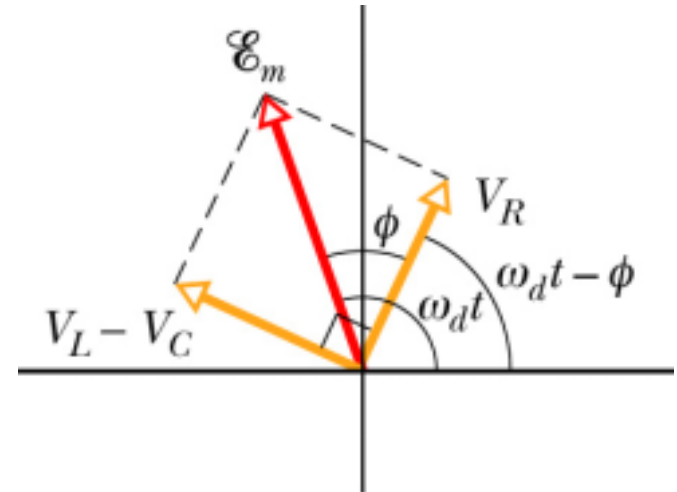

- From amplitude relations

result: $V_R = IR$ $V_L = IX_L$ $V_C = IX_C$

$$E_m^2 = (IR)^2 + (IX_L - IX_C)^2$$

- Rearrange to find amplitude I

$$I = \frac{E_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$

EM Oscillations (47)

$$I = \frac{E_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$

- Define **impedance, Z** to be

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


- Using reactances rewrite current as

$$X_L = \omega_d L$$

$$X_C = \frac{1}{\omega_d C}$$

$$I = \frac{E_m}{\sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2}}$$

$$I = \frac{E_m}{Z}$$

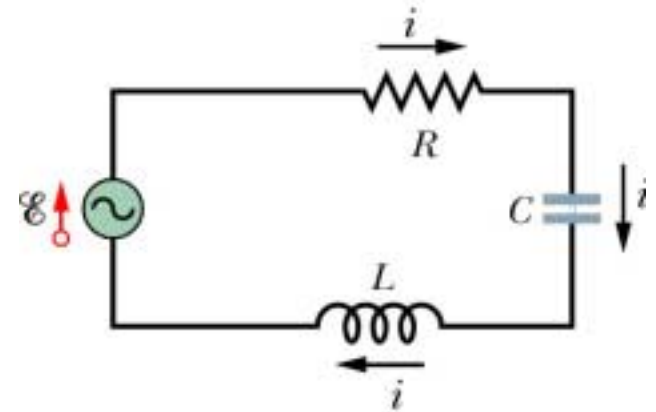

EM Oscillations (48)


- Using trig find the phase constant ϕ

$$\tan \phi = \frac{V_L - V_C}{V_R}$$

- Using amplitude relations

$$\tan \phi = \frac{IX_L - IX_C}{IR}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

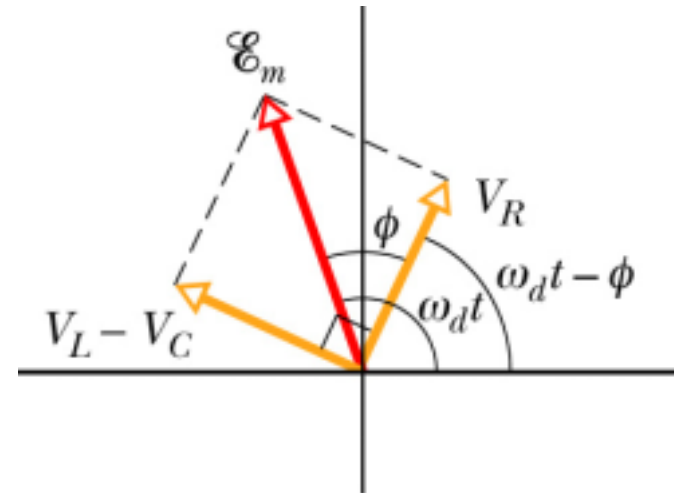



- Examine 3 cases:

- $X_L > X_C$
- $X_L < X_C$
- $X_L = X_C$

EM Oscillations (49)

$$\tan \phi = \frac{X_L - X_C}{R}$$

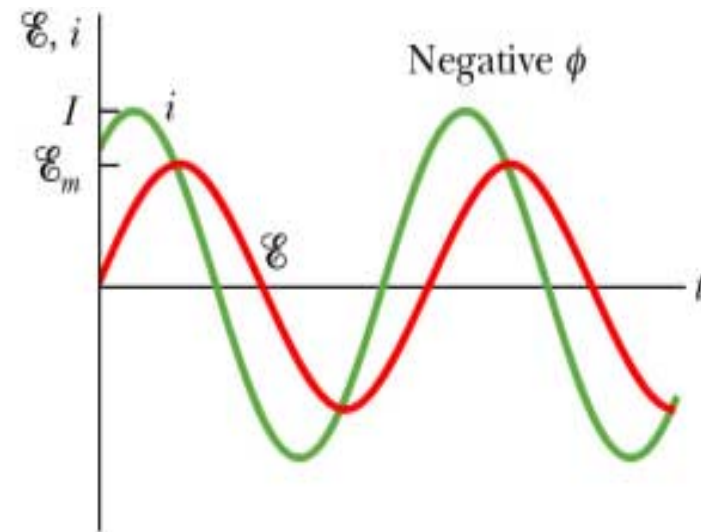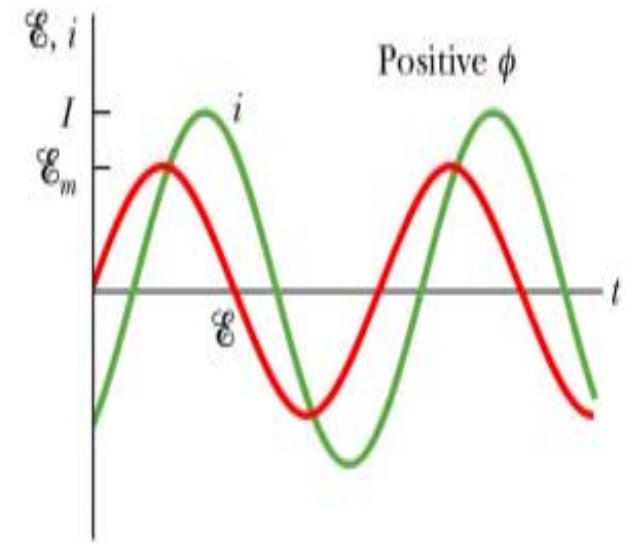- If $X_L > X_C$ the circuit is more inductive than capacitive
 - ϕ is positive
 - Emf is before current (ELI)
- If $X_L < X_C$ the circuit is more capacitive than inductive
 - ϕ is negative
 - Current is before emf (ICE)



EM Oscillations (50)


$$\tan \phi = \frac{X_L - X_C}{R}$$

- If $X_L = X_C$ the circuit is in **resonance** – emf and current are in phase
- Current amplitude I is max when impedance, Z is min

$$X_L - X_C = 0$$

$$Z = R$$
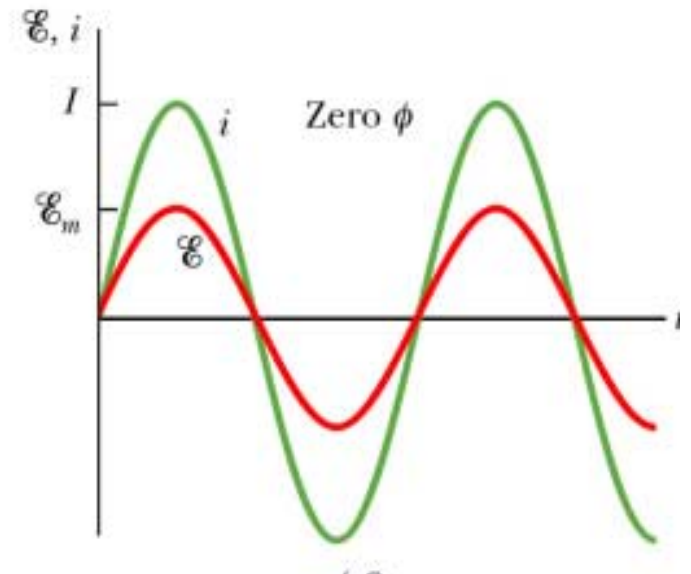
$$I = \frac{E_m}{Z} = \frac{E_m}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{E_m}{R}$$



EM Oscillations (51)

- When $X_L = X_C$ the driving frequency is

$$\omega_d L = \frac{1}{\omega_d C}$$

$$\omega_d = \frac{1}{\sqrt{LC}}$$

- This is the same as the natural frequency, ω


$$\omega_d = \omega = \frac{1}{\sqrt{LC}}$$

- For RLC circuit, resonance and the max current / occurs when $\omega_d = \omega$

EM Oscillations (52)

- For small driving frequency, $\omega_d < \omega$
 - X_L is small but X_C is large
 - Circuit capacitive
- For large driving frequency, $\omega_d > \omega$
 - X_C is small but X_L is large
 - Circuit inductive
- For $\omega_d = \omega$, circuit is in resonance
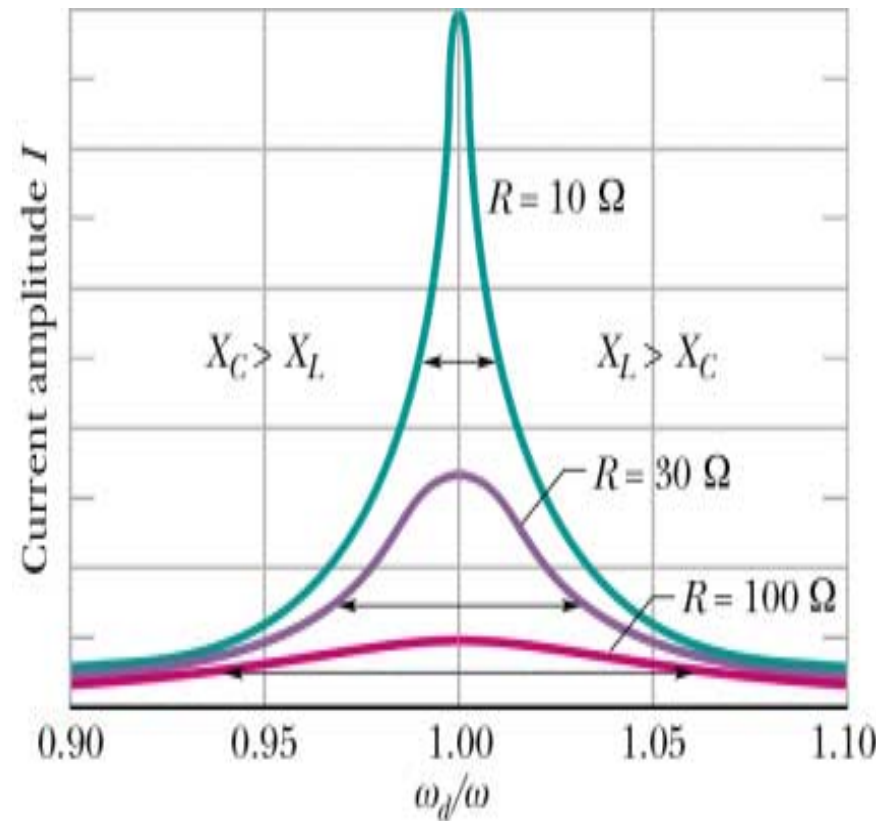
$$I = \frac{E_m}{\sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2}}$$



EM Oscillations (53)

- Instantaneous rate which energy is dissipated in resistor is



$$P = i^2 R$$

- But $i = I \sin(\omega_d t - \phi)$


$$P = I^2 R \sin^2(\omega_d t - \phi)$$

- Want average rate, P_{avg}
 - Average over complete cycle T

$$\sin^2 \theta = 1/2$$

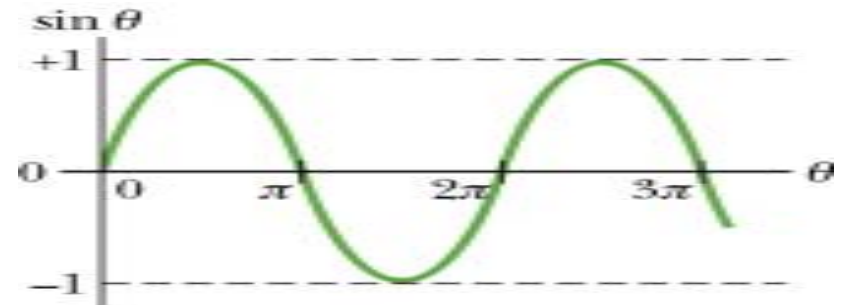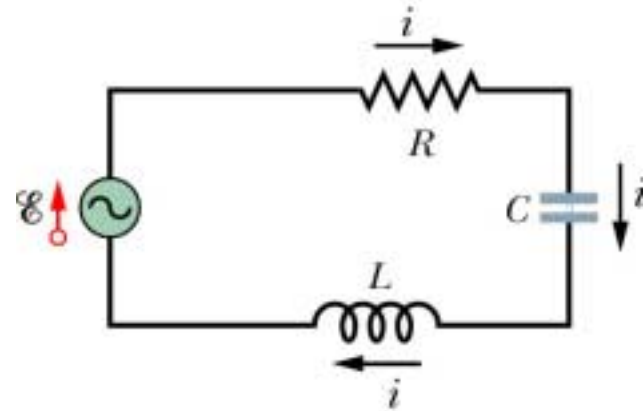

(a)

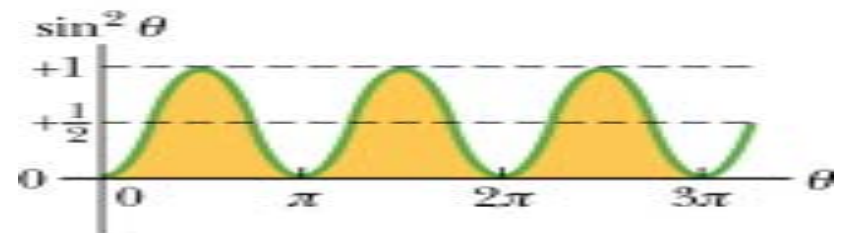

EM Oscillations (53)

- For alternating current circuits define **root-mean-square or rms** values for i , V and emf

$$I_{rms} = \frac{I}{\sqrt{2}}$$

$$V_{rms} = \frac{V}{\sqrt{2}}$$

$$E_{rms} = \frac{E}{\sqrt{2}}$$

- Ammeters, voltmeters - give rms values
- Write average power dissipated by resistor in an ac circuit is

$$P_{avg} = \frac{I^2 R}{2} = \left(\frac{I}{\sqrt{2}} \right)^2 R$$

$$P_{avg} = I_{rms}^2 R$$

EM Oscillations (54)

- Write average power in another form using

$$I_{rms} = \frac{E_{rms}}{Z}$$


$$P_{avg} = I_{rms}^2 R = \frac{E_{rms}}{Z} I_{rms} R = E_{rms} I_{rms} \frac{R}{Z}$$

- Using phasor and amplitude relations

$$\cos \phi = \frac{V_R}{E_m} = \frac{IR}{IZ} = \frac{R}{Z}$$

- Rewrite average power as

$$P_{avg} = E_{rms} I_{rms} \cos \phi$$

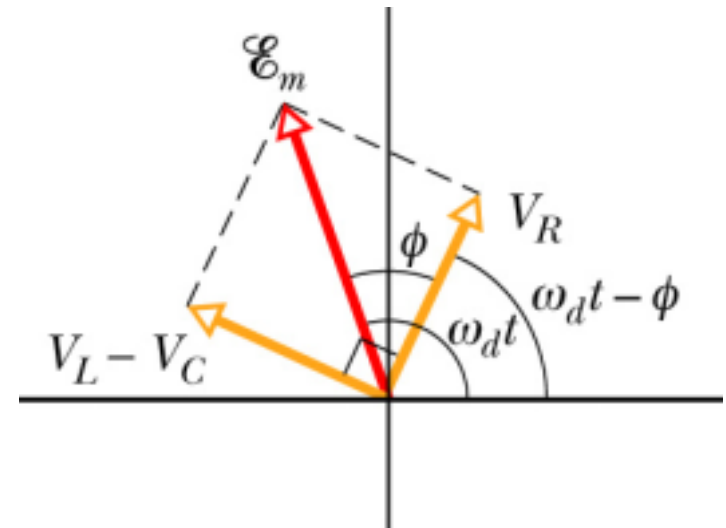

EM Oscillations (55)

- If ac circuit has only resistive load $R/Z = 1$

$$P_{avg} = E_{rms} I_{rms} = I_{rms} V_{rms}$$


- Trade-off between current and voltage
 - For general use want low voltage
 - Means high current but

$$P_{avg} = I_{rms}^2 R$$

- General energy transmission rule:
Transmit at the highest possible voltage
and the lowest possible current

EM Oscillations (56)

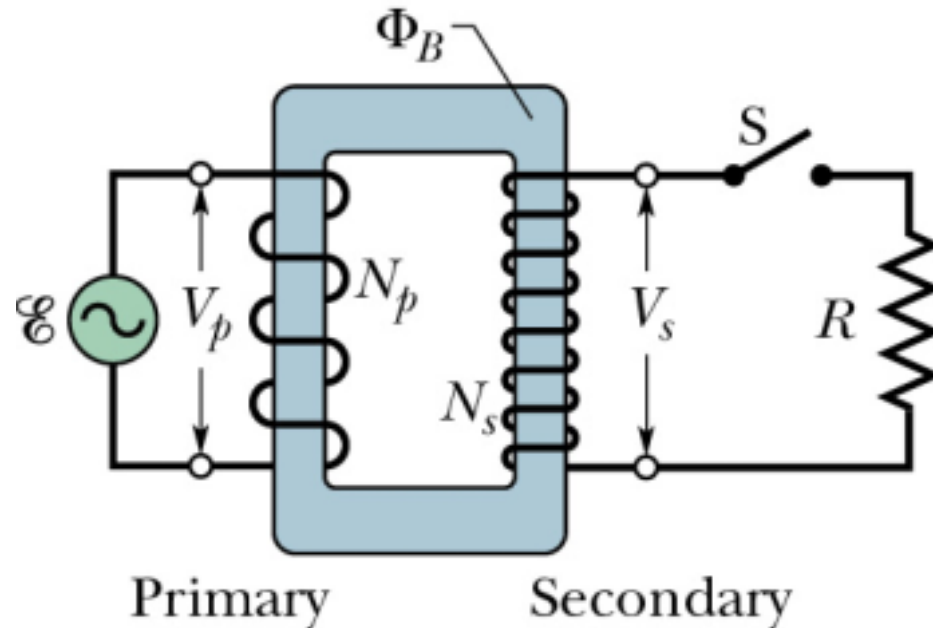- **Transformer** – device used to raise (for transmission) and lower (for use) the ac voltage in a circuit, keeping iV constant
 - Has 2 coils (primary and secondary) wound on same iron core with different #s of turns




EM Oscillations (57)

- Alternating primary current induces alternating magnetic flux in iron core
- Same core in both coils so induced flux also goes through the secondary coil
- Using Faraday's law

$$V_P = -N_P \frac{d\Phi_B}{dt}$$

$$V_S = -N_S \frac{d\Phi_B}{dt}$$

$$\frac{V_P}{N_P} = \frac{V_S}{N_S}$$

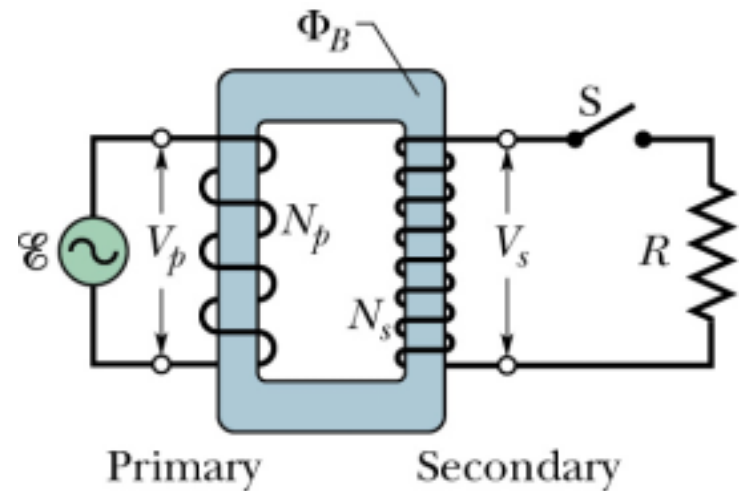


EM Oscillations (58)

- Transformation of voltage is
- If $N_S > N_P$ called a **step-up transformer**
- If $N_S < N_P$ called a **step-down transformer**
- Conservation of energy

$$V_S = V_P \frac{N_S}{N_P}$$

$$I_P V_P = I_S V_S$$
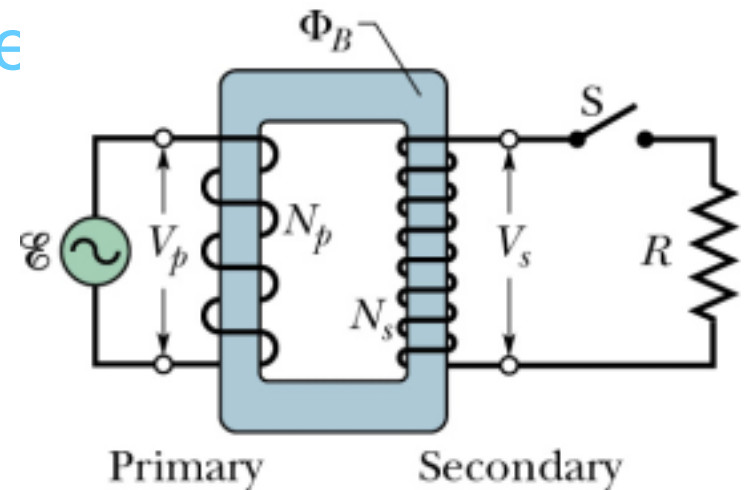
$$I_S = I_P \frac{V_P}{V_S} = I_P \frac{N_P}{N_S}$$



EM Oscillations (59)

- The current I_P appears in primary circuit due to R in secondary circuit.

$$I_P V_P = I_S V_S \quad I_S = V_S / R$$

$$I_P = \frac{V_S}{R} \frac{V_S}{V_P} = \frac{1}{R} \frac{V_S^2}{V_P^2} V_P = \frac{1}{R} \left(\frac{N_S}{N_P} \right)^2 V_P$$

- Has for of $I_P = V_P / R_{eq}$ where

$$R_{eq} = \left(\frac{N_P}{N_S} \right)^2 R$$

