

PHY232 (Pratt) Quiz #1

A light bulb dissipates **75 W** of power when a potential difference of **125 V** is placed across it.

1. The current flowing through the bulb is

- (a) 0.45 A
- (b) 0.60 A ← correct answer. $I = P/\Delta V = 75\text{W}/125\text{V}$
- (c) 0.75 A
- (d) 0.90 A
- (e) 1.05 A

2. The resistance of the bulb is

- (a) $2.1 \times 10^2 \Omega$ ← correct answer. $R = 125\text{V}/0.60\text{A}$
- (b) $3.2 \times 10^2 \Omega$
- (c) $4.3 \times 10^2 \Omega$
- (d) $5.4 \times 10^2 \Omega$
- (e) $6.5 \times 10^2 \Omega$

Could also use $P = (\Delta V)^2/R$. Thus $R = (\Delta V)^2/P = 2.1 \times 10^2 \Omega$