

October 1st


Circuits - Chapter 28

# How to Analyze Complex Circuits

- Kirchhoff's junction rule (or current law) –
  - From conservation of charge
  - Sum of currents entering a junction is equal to sum of currents leaving that junction
- Kirchhoff's loop rule (or voltage law) –
  - From conservation of energy
  - Sum of changes in potential going around a complete circuit loop equals zero
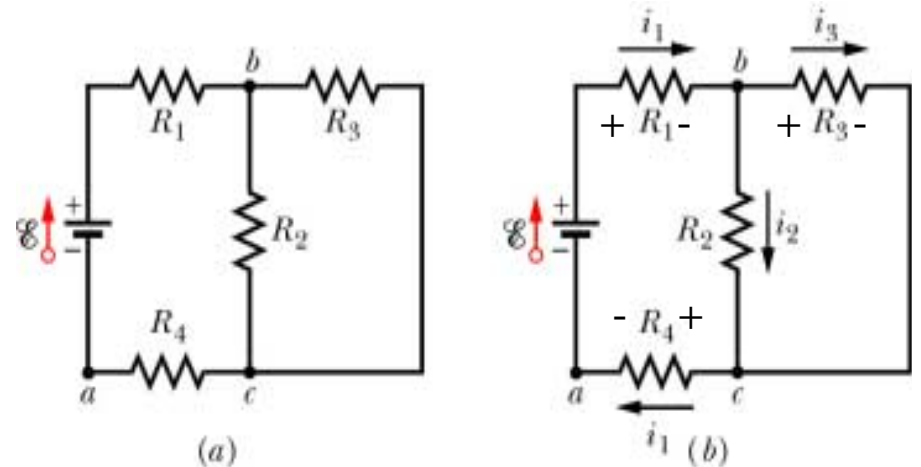
# Circuits (Figs. 28-9a, 28-9b)

- What is  $i$  through the battery?
- Label currents. New label for every branch. Pick any arbitrary direction.
- $i$  through  $R_1$  or  $R_4$  is same as for battery
- Can use loop rule




$$\mathcal{E} - i_1 R_1 - i_2 R_2 - i_1 R_4 = 0$$

# Circuits (Figs. 28-9a, 28-9b)

$$\text{—} i_1 R_1 - i_2 R_2 - i_1 R_4 = 0$$

- Equation has 2 unknowns so need to apply loop rule again
- Take the loop through  $R_2$  and  $R_3$

$$-i_3 R_3 + i_2 R_2 = 0$$

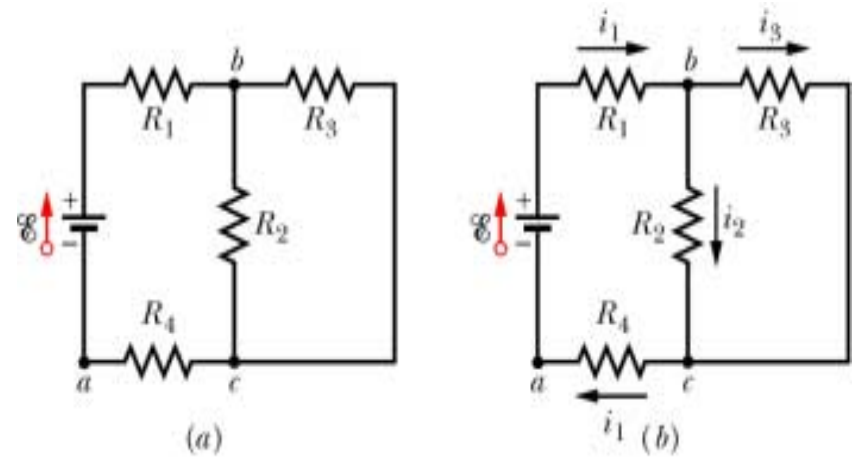

$$i_1 = i_2 + i_3$$

$$-(i_1 - i_2)R_3 + i_2 R_2 = 0$$

$$i_2 = -\frac{i_1 R_3}{(R_3 + R_2)}$$


# Circuits (Figs. 28-9a, 28-9b)

Now solve for  $i_1$ :

$$\text{—} i_1 R_1 - i_2 R_2 - i_1 R_4 = 0$$

$$\text{—} i_1 R_1 - \frac{i_1 R_3 R_2}{(R_2 + R_3)} - i_1 R_4 = 0$$

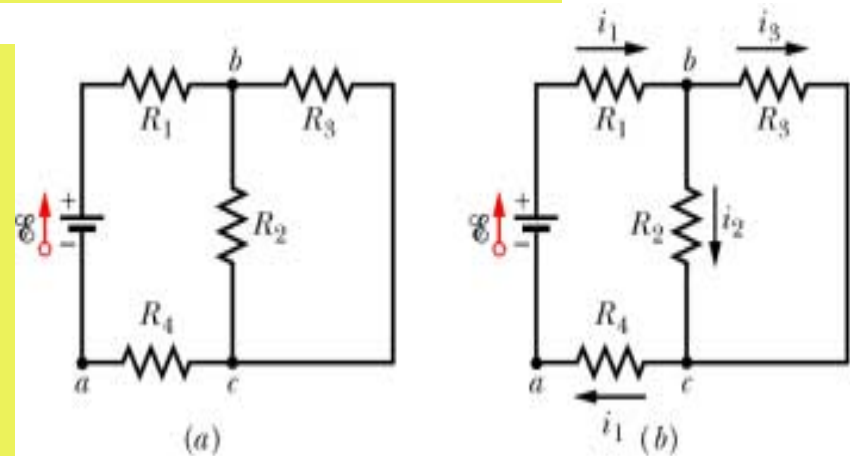
$$i_1 = \frac{E}{R_1 + \frac{R_2 R_3}{(R_2 + R_3)} + R_4}$$



# Circuits (Figs. 28-9a, 28-9b)

- What is current Voltage lost (V) in  $R_2$ ?
- Recall that  $V=iR$

$$V_2 = i_2 R_2$$

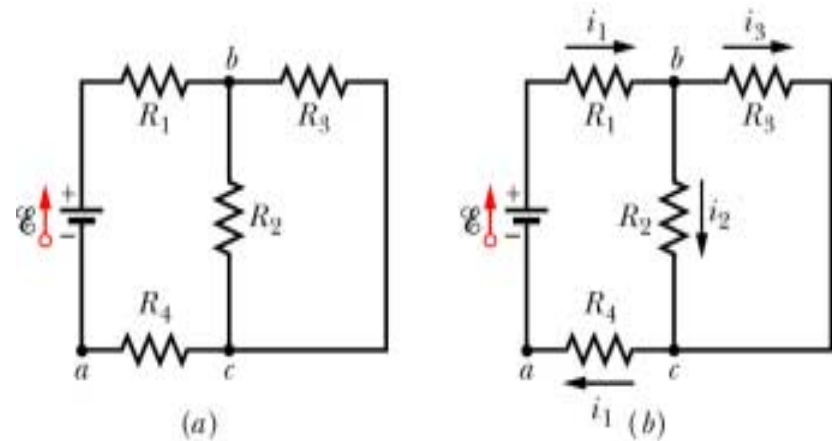


$$\text{point} - i_1 R_1 - i_2 R_2 - i_1 R_4 = 0$$

$$i_2 = \frac{i_1 R_1 + i_1 R_4 - \text{point}}{R_2}$$

$$i_1 = \frac{\text{point}}{R_1 + \frac{R_2 R_3}{(R_2 + R_3)} + R_4}$$

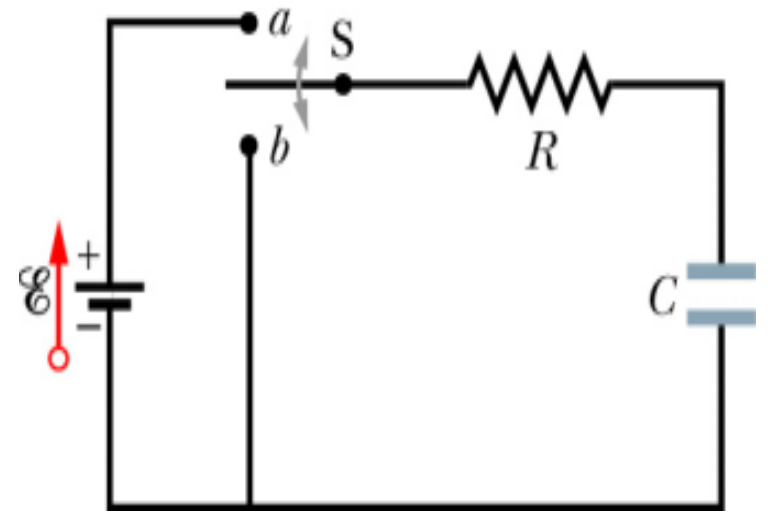
# Circuits (Fig. 28-13)

- Circuits where current varies with time
- **RC series circuit** – a resistor and capacitor are in series with a battery and a switch
- At  $t = 0$  switch is open and capacitor is uncharged so  $q = 0$


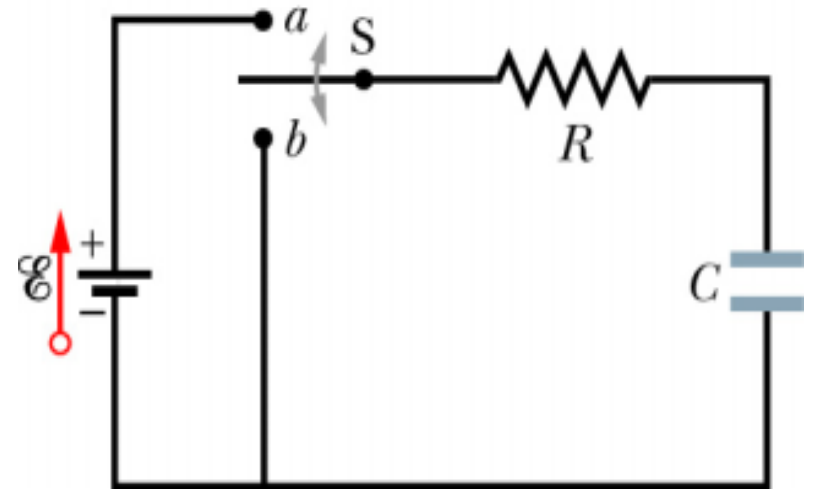
## Circuits (Fig. 28-13)

- Close the switch at point a
- Charge flows (current) from battery to capacitor, increasing  $q$  on plates and  $V$  across plates




- When  $V_C$  equal  $V_{battery}$  flow of charge stops (current is zero) and charge on capacitor is

$$q = CV = CE$$


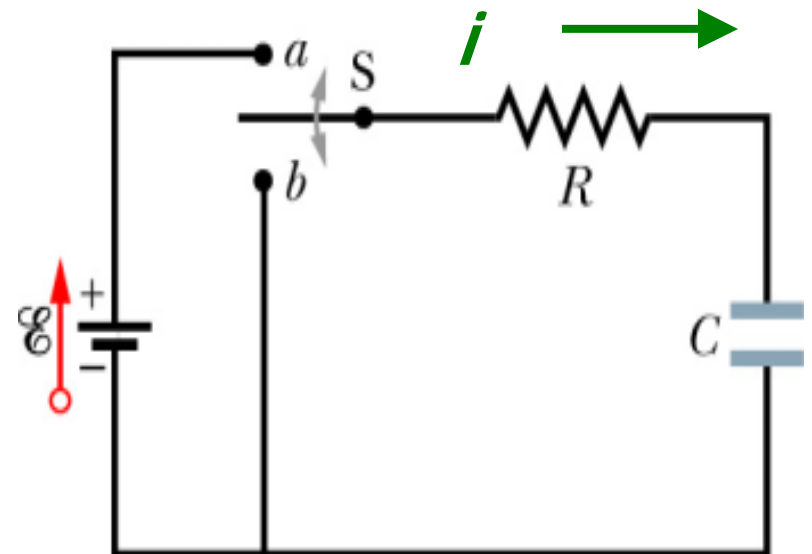
## Circuits (Fig. 28-13)

- Want to know how  $q$  and  $V$  of capacitor and  $i$  of the circuit change with time when charging the capacitor
- Apply loop rule, traversing clockwise from battery



$$\mathcal{E} - iR - \frac{q}{C} = 0$$

# Circuits (Fig. 28-13)


$$E - iR - \frac{q}{C} = 0$$

- Contains 2 of the variables we want  $i$  and  $q$
- Remember

$$i = \frac{dq}{dt}$$

- Substituting gives


$$R \frac{dq}{dt} + \frac{q}{C} = E$$

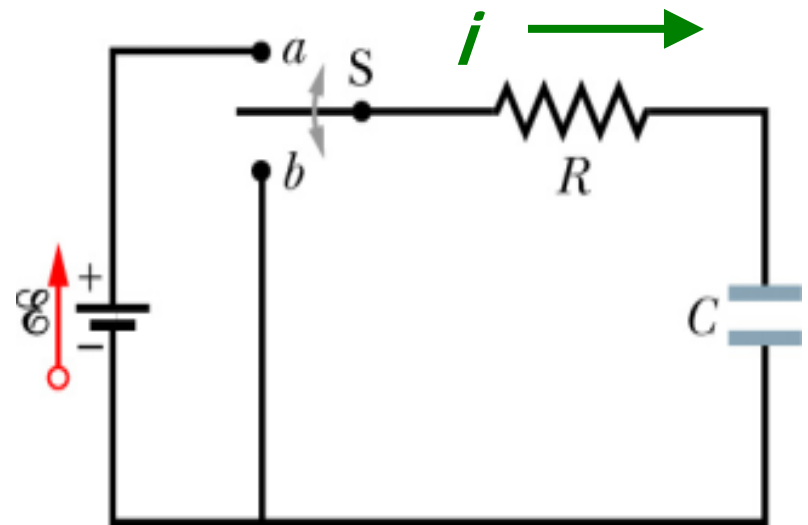
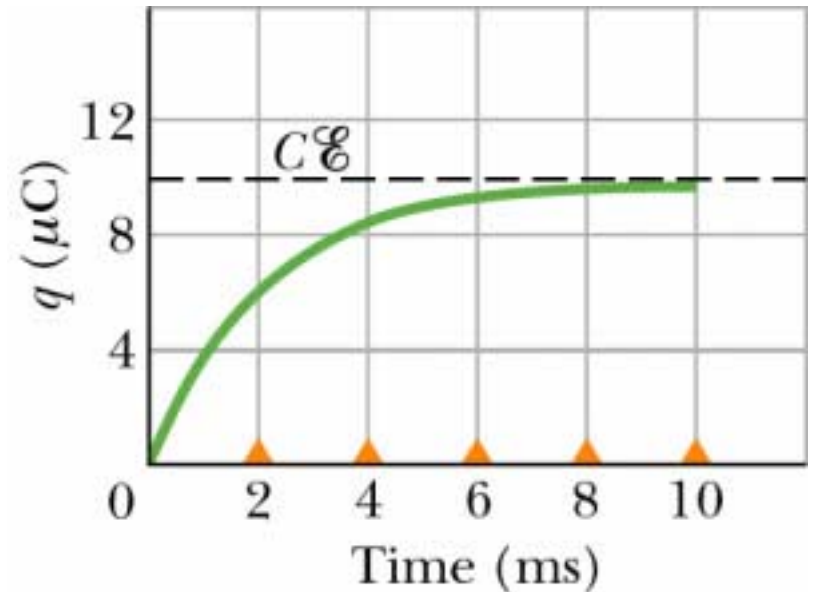
# Circuits (Fig. 28-14a)

$$R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E}$$

- Need a function which satisfies initial condition  $q = 0$  at  $t = 0$  and final condition of  $q = C\mathcal{E}$  at  $t = \infty$
- For **charging a capacitor**




$$q = C\mathcal{E} \left( 1 - e^{-t/RC} \right)$$
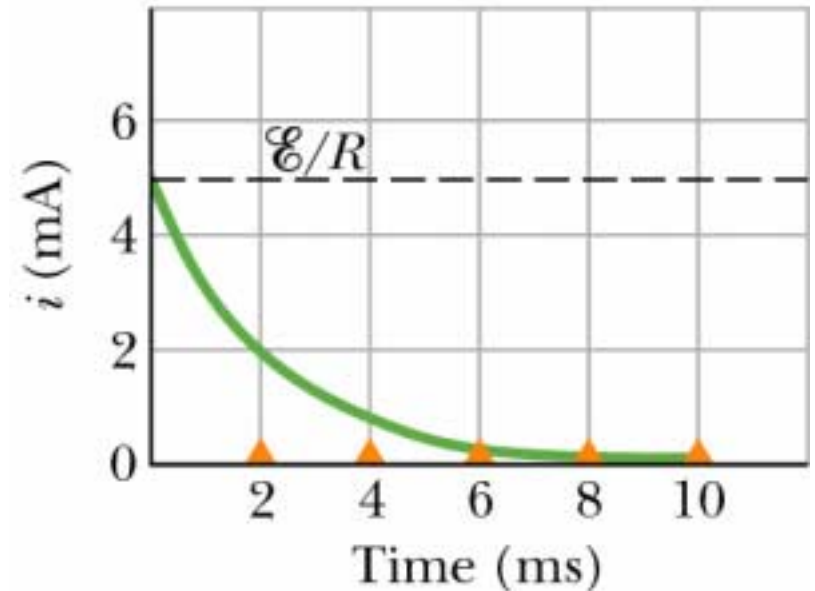
## Circuits (Fig. 28-14b)

$$q = CE \left( 1 - e^{-t/RC} \right)$$

- Want current as a function of time
- For **charging a capacitor**




$$i = \frac{dq}{dt} = \left( \frac{E}{R} \right) e^{-t/RC}$$
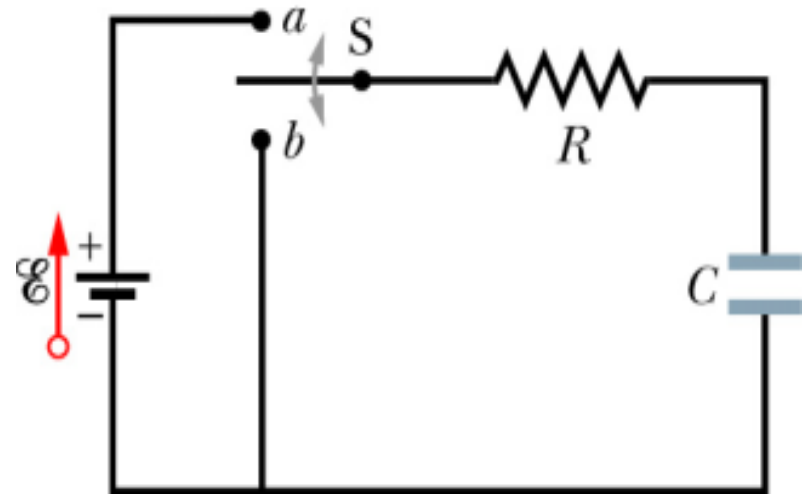
# Circuits (Fig. 28-13)

$$q = CE \left( 1 - e^{-t/RC} \right)$$


- Want  $V$  across the capacitor as function of time
- For **charging a capacitor**



$$V_c = \frac{q}{C} = E \left( 1 - e^{-t/RC} \right)$$
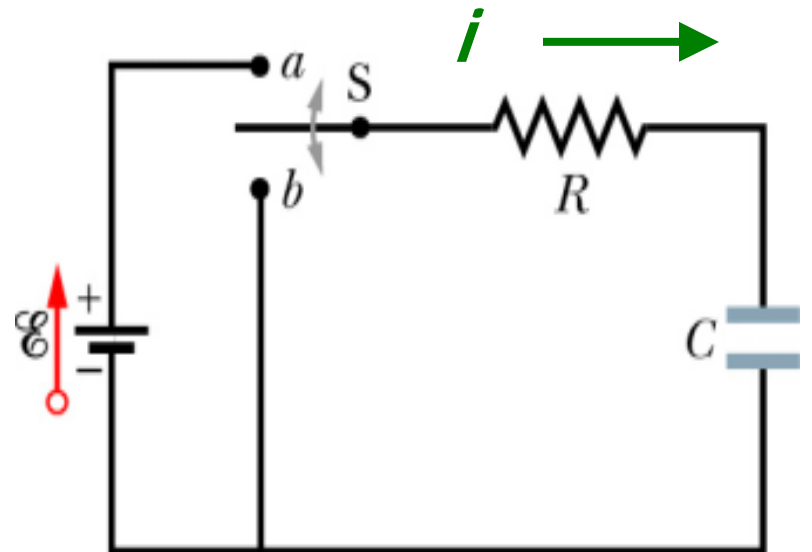
# Circuits (Fig. 28-13)

- Want to know how  $q$  of capacitor and  $i$  of the circuit change with time when **discharging** the capacitor
- At new time  $t = 0$ , throw switch to point  $b$  and discharge capacitor through resistor  $R$




## Circuits (Fig. 28-13)

- Apply the loop rule again but this time no battery

$$-iR - \frac{q}{C} = 0$$

- Substituting for  $i$  again gives differential equation

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$

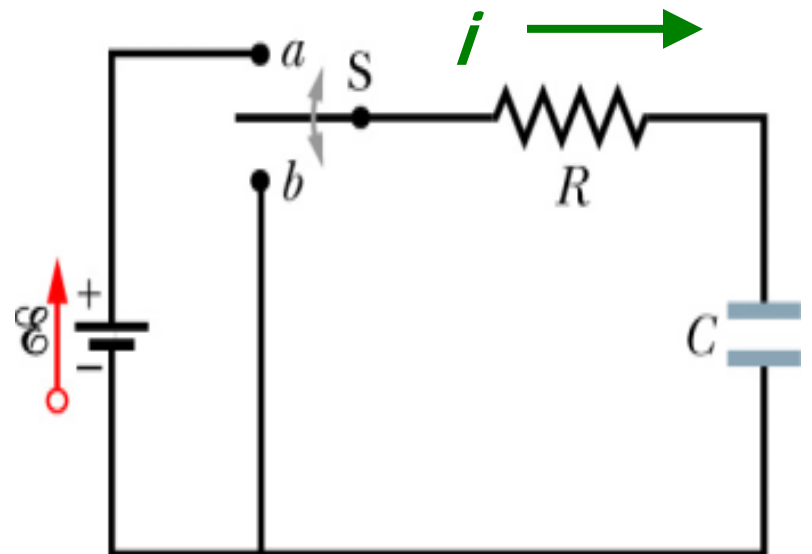


## Circuits (Fig. 28-13)

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$

- Solution must satisfy initial condition that  $q_0 = CV_0$
- For **discharging a capacitor**

$$q = q_0 e^{-t/RC}$$

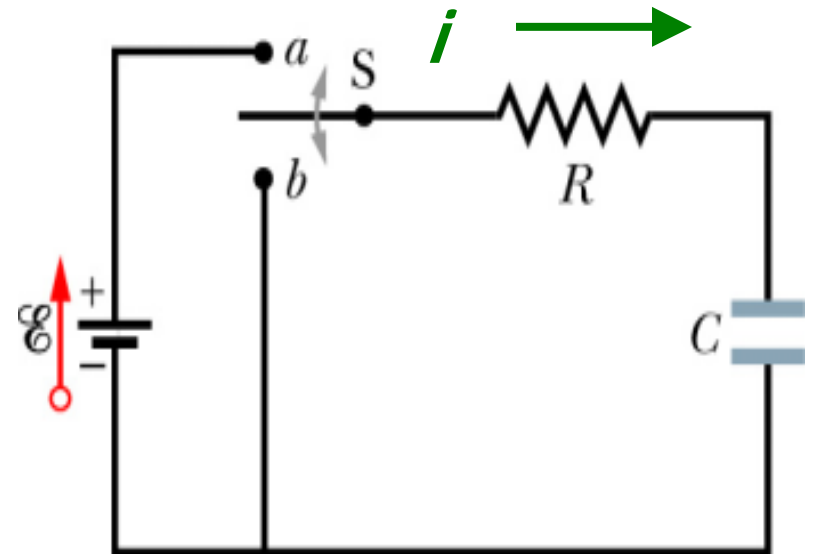



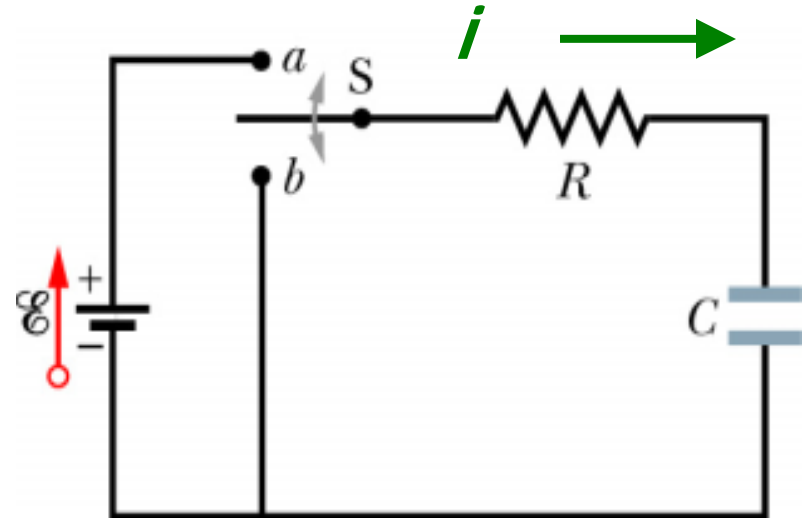
## Circuits (Fig. 28-13)

$$q = q_0 e^{-t/RC}$$

- Find  $i$  for **discharging capacitor** with initial condition at  $i_0 = V_0/R = q_0/RC$  at  $t = 0$



$$i = \frac{dq}{dt} = -\left(\frac{q_0}{RC}\right)e^{-t/RC}$$

Negative sign means charge is decreasing

# Circuits

- Charging capacitor

$$q = CE(1 - e^{-t/RC})$$

$$i = \left( \frac{E}{R} \right) e^{-t/RC}$$

- Discharging capacitor

$$q = q_0 e^{-t/RC}$$

$$i = -\left( \frac{q_0}{RC} \right) e^{-t/RC}$$

- Define **capacitive time constant** –  
greater  $\tau$ , greater (dis)charging time

$$\tau = RC$$