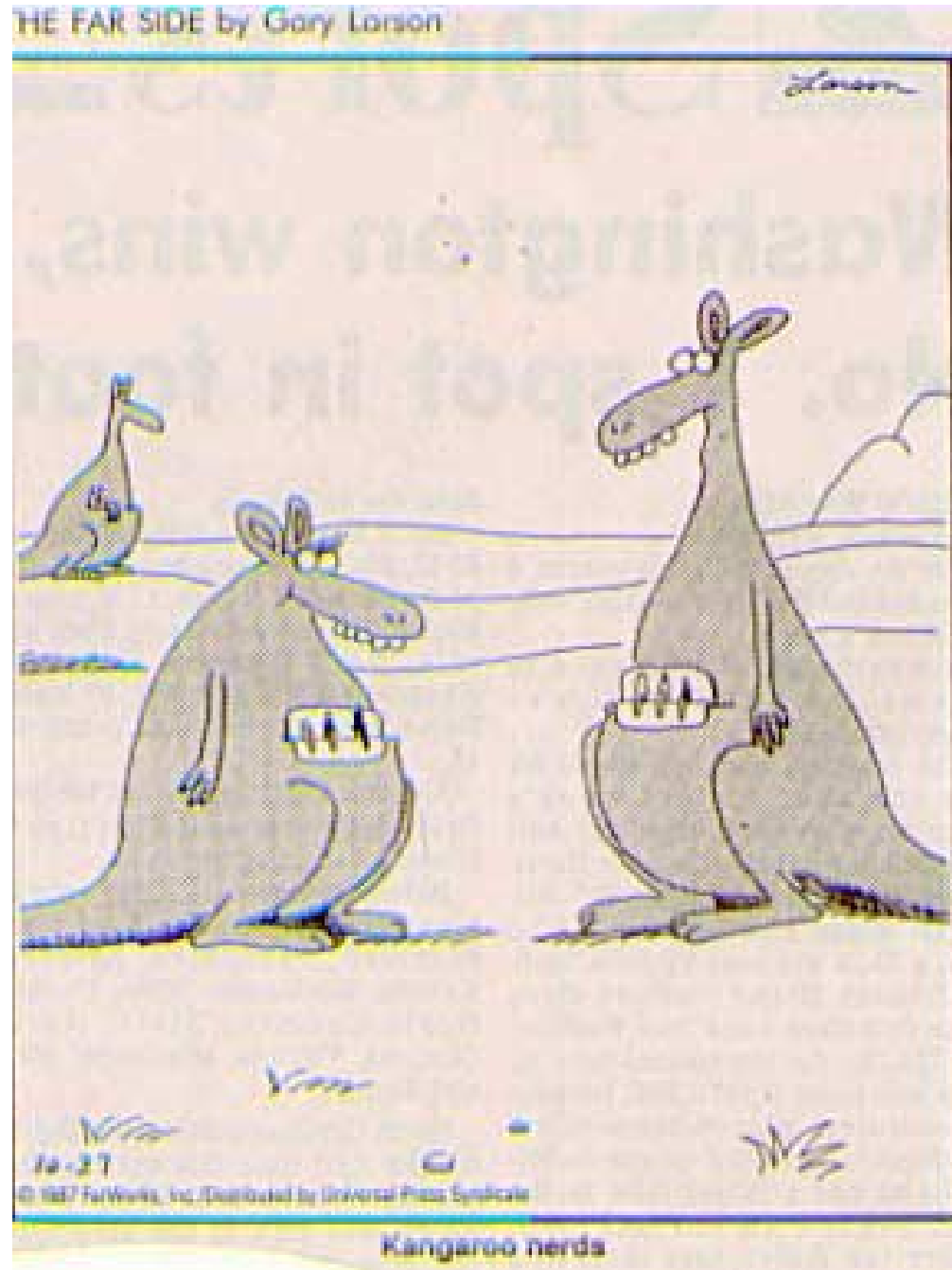


October  
22th

Induction and  
Inductance  
Chapter 31



# Midterm-2



- **Wednesday October 29 at 6pm**
  - Sec 1 – N100 BCC (Business College)
  - Sec 2 – 158 NR (Natural Resources)
- Allowed one sheet of notes (both sides) and calculator
- Covers Chapters 27-31 and homework sets #5-8
- Send an email to your professor if you have a class conflict and need a make-up exam

# Review - Self Inductance

- Self-induced emf,  $\mathcal{E}_L$  appears in any coil in which the current is changing

$$\mathcal{E}_L = -L \frac{di}{dt}$$

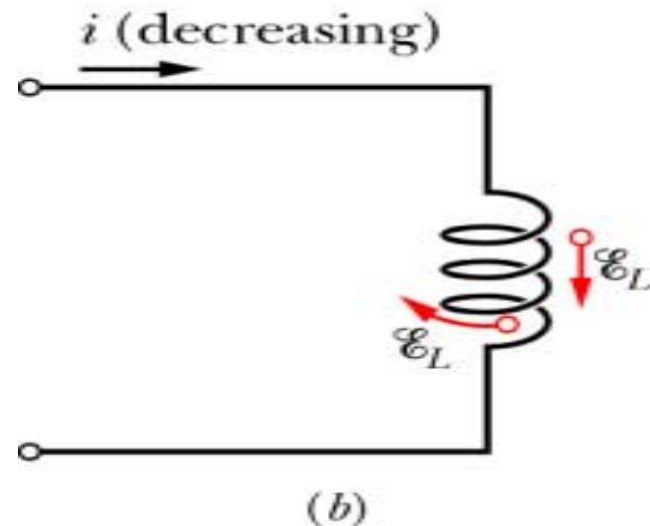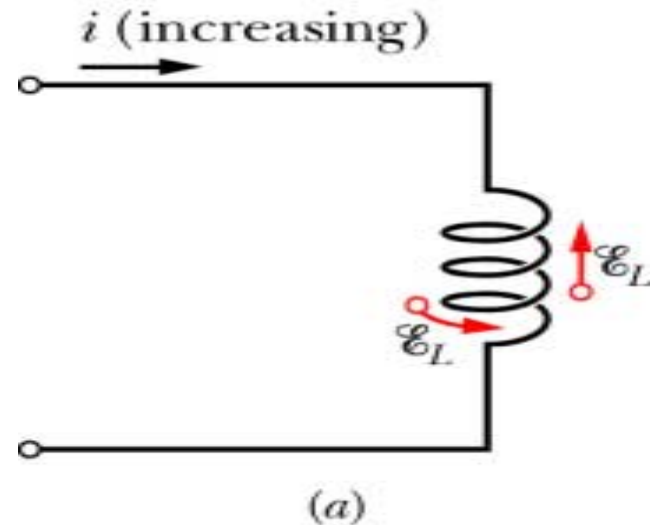- Direction of  $\mathcal{E}_L$  follows Lenz's law and opposes the change in current




# Review - Mutual Inductance

- What is induced emf in coil 1 from a changing current in coil 2?

$$\mathcal{E}_1 = -M_{12} \frac{di_2}{dt}$$

where

$$M_{12} = \frac{N_1 \Phi_{12}}{i_2}$$

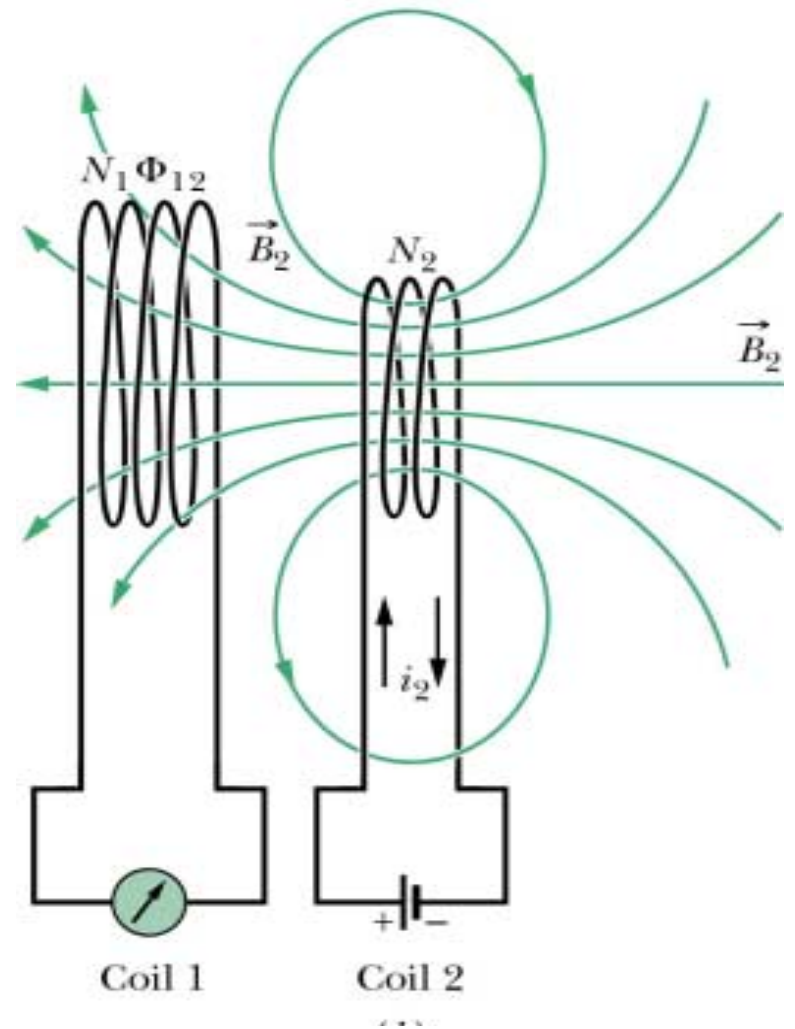


# Review RC circuit

- **RC circuit** is a resistor and capacitor in series
  - Charging up a capacitor (switch at a)

$$q = CE(1 - e^{-t/\tau_c})$$

- Discharging capacitor (switch at b)

$$q = q_0 e^{-t/\tau_c}$$

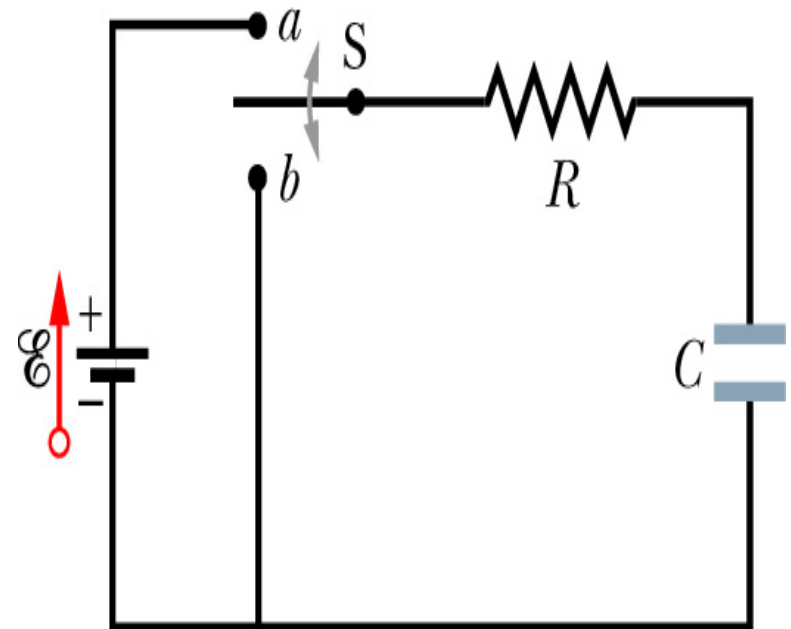

where

$$\tau_c = RC$$


# Inductance

- **RL circuit** is a resistor and inductor in series
- Close switch to point a
  - **Initially**  $i$  is increasing through inductor so  $\mathcal{E}_L$  opposes rise and  $i$  through  $R$  will be


$$i < \mathcal{E}/R$$

- **Long time later**,  $i$  is constant so  $\mathcal{E}_L=0$  and  $i$  in circuit is

$$i = \mathcal{E}/R$$

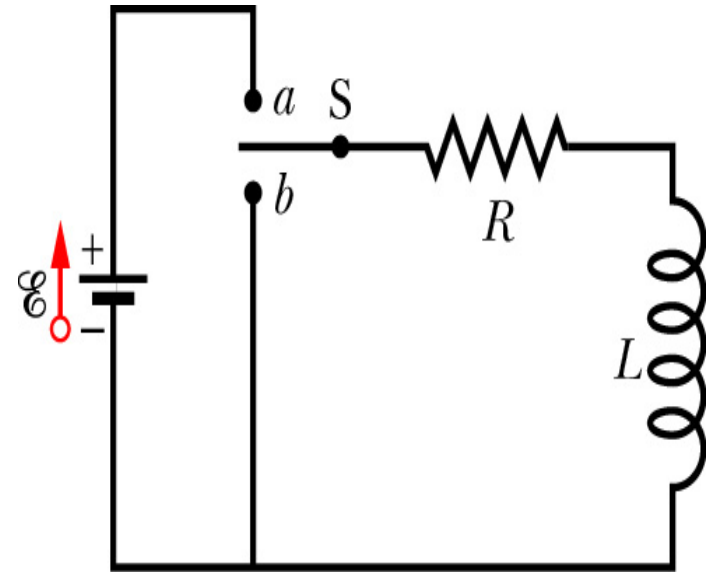



$$\mathcal{E}_L = -L \frac{di}{dt}$$

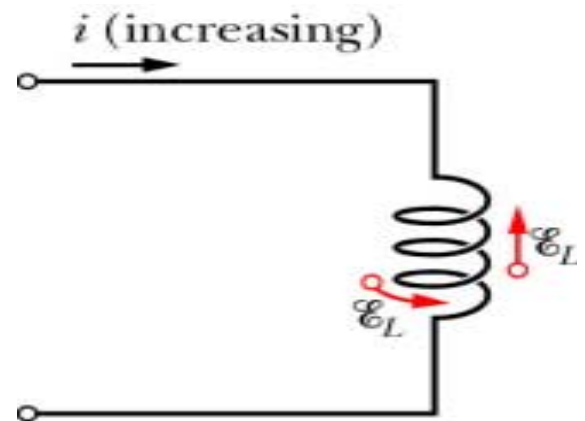
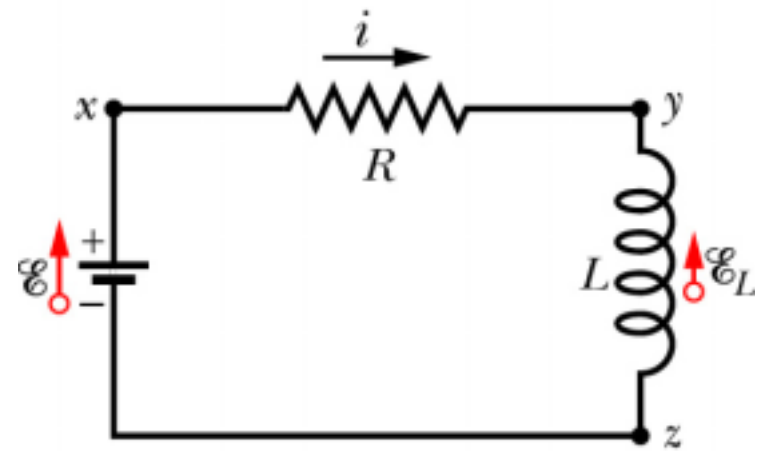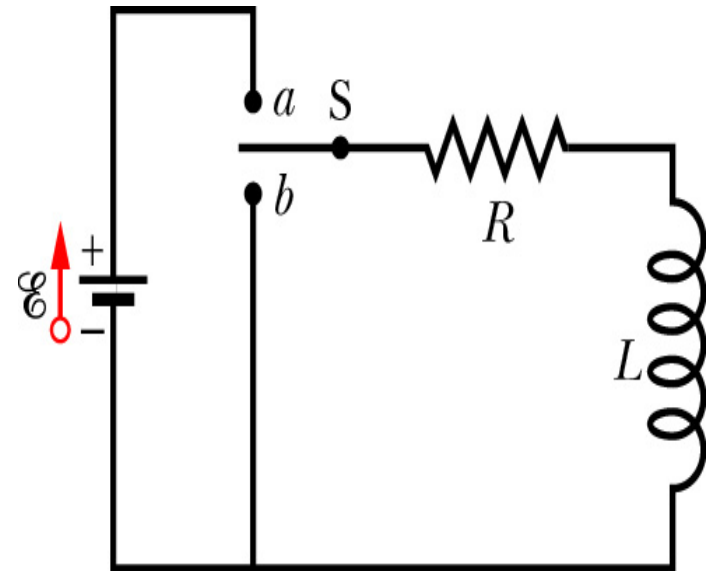
# Inductance

- Initially an inductor acts to oppose changes in current through it
- Long time later inductor acts like ordinary conducting wire
- Apply loop rule right after switch has been closed at a

$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$



# Inductance

- Differential equation similar to capacitors


$$\mathcal{E} = iR + L \frac{di}{dt}$$

- Solution is

$$i = \frac{\mathcal{E}}{R} \left( 1 - e^{-t/\tau_L} \right)$$

- Inductive time constant is

$$\tau_L = \frac{L}{R}$$

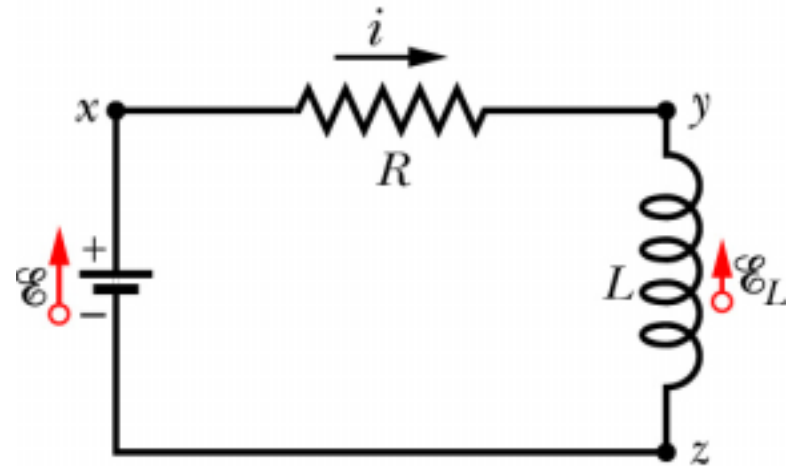

- Satisfies conditions:

- At  $t=0$ ,  $i = 0$
- At  $t=\infty$ ,  $i = \mathcal{E}/R$




# Inductance

- Now move switch to position b so battery is out of system
- Current will decrease with time and loop rule gives

$$iR + L \frac{di}{dt} = 0$$

- Solution is
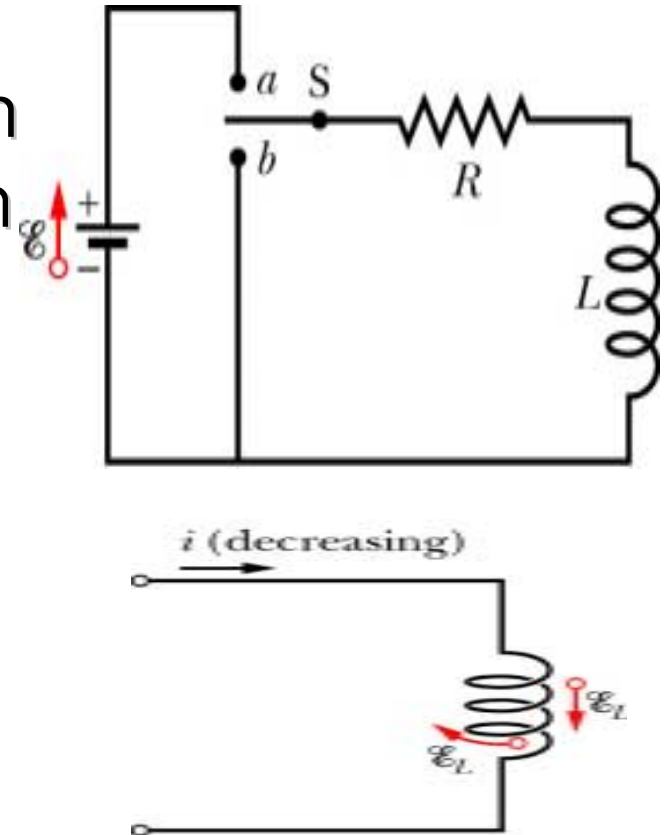
$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$



- Satisfies conditions
  - At  $t=0$ ,  $i = i_0 = \mathcal{E}/R$
  - At  $t=\infty$ ,  $i = 0$

# RL circuits Summary

- Circuit is closed (switch to "a")


$$i = \frac{\mathcal{E}}{R} \left(1 - e^{-t/\tau_L}\right)$$

- Circuit is opened (switch to "b")

$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$

- Time constant is

$$\tau_L = \frac{L}{R}$$


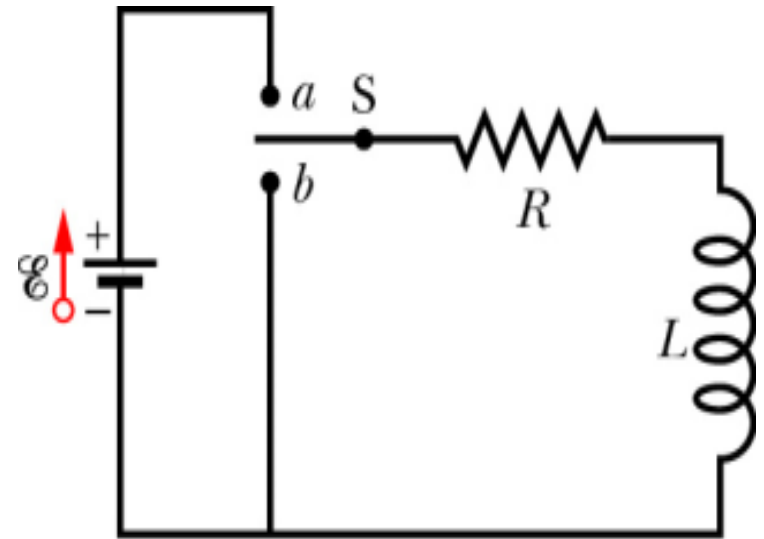


Switch at a, current through inductor is:

- Initially  $i = 0$  (acts like **broken wire**)
- Long time later  $i = \mathcal{E}/R$  (acts like **simple wire**)
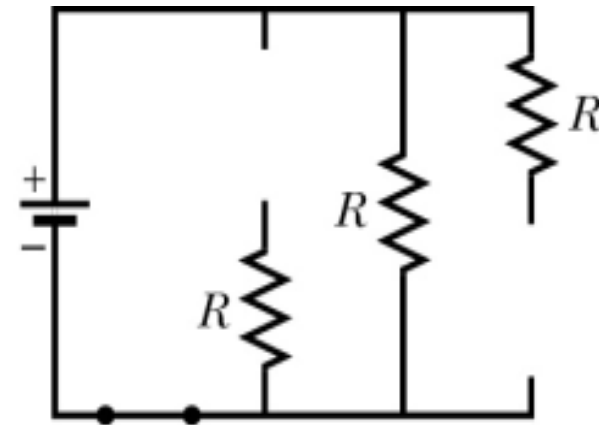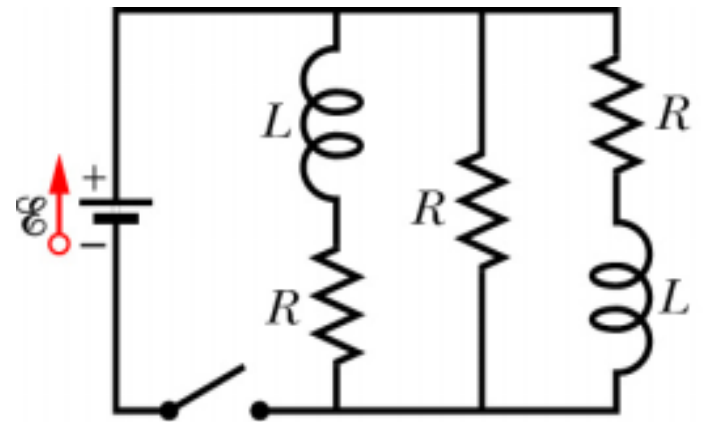
# Inductance (Prob. 31-5)

- Have a circuit with resistors and inductors
- What is the current through the battery **just after** closing the switch?
- Inductor oppose change in current through it
- Right after switch is closed, current through inductor is 0
- **Inductor acts like broken wire**





# Inductance (Prob. 31-5)

- Apply loop rule

$$E - iR = 0$$

- Immediately after switch closed, current through the battery is

$$i = \frac{E}{R}$$

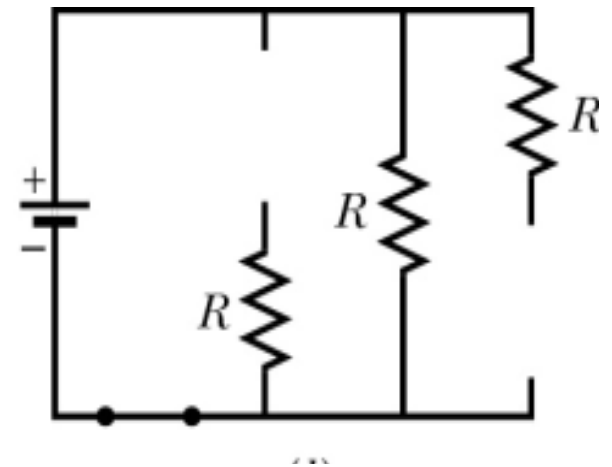
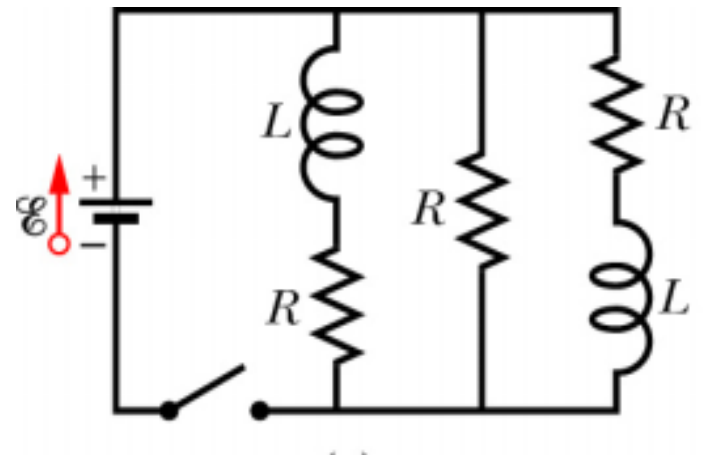


# Inductance (Prob. 31-5)

- What is the current through the battery a **long time after** the switch has been closed?
- Currents in circuit have reached equilibrium so **inductor acts like simple wire**
- Circuit is 3 resistors in parallel

$$i = \frac{E}{R_{eq}}$$

$$R_{eq} = \frac{R}{3}$$

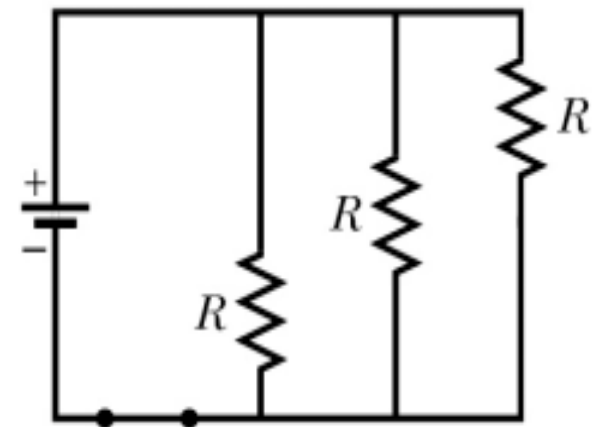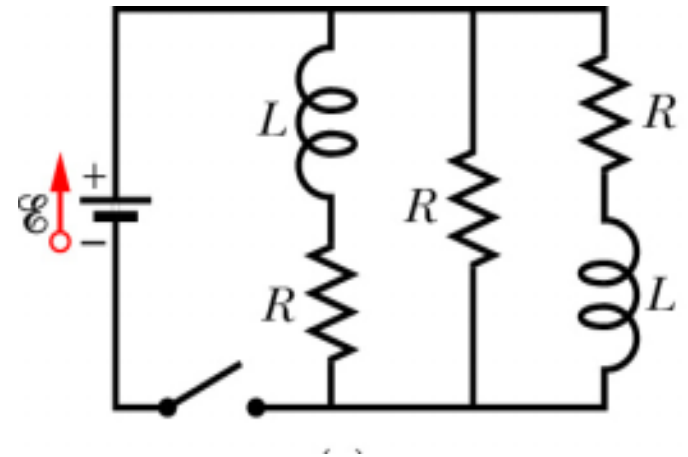

(c)


# Inductance

- How much energy is stored in a  $B$  field?
- Conservation of energy expressed in loop rule

$$\mathcal{E} = L \frac{di}{dt} + iR$$

- Multiply each side by  $i$
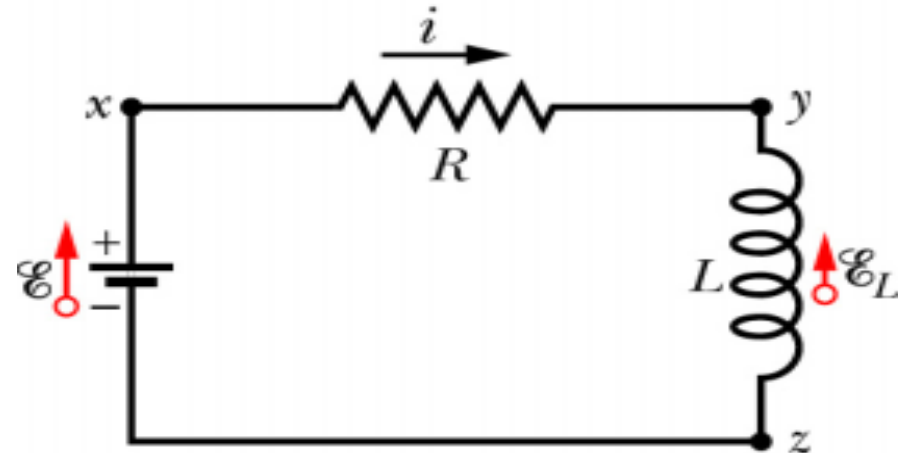
$$\mathcal{E}i = Li \frac{di}{dt} + i^2 R$$



- $P=i\mathcal{E}$  is the rate at which the battery delivers energy to rest of circuit
- $P=i^2 R$  is the rate at which energy appears as thermal energy in resistor

# Inductance

- Middle term is rate at which energy  $dU_B/dt$  is stored in the  $B$  field

$$\frac{dU_B}{dt} = Li \frac{di}{dt}$$

- Energy stored in magnetic field

$$U_B = \frac{1}{2} Li^2$$

- Similar to energy stored in electric field

$$U_E = \frac{1}{2} \frac{q^2}{C}$$

# Inductance

- What is the energy density of a  $B$  field?
- Energy density,  $u_B$  is energy per unit volume

$$u_B = \frac{U_B}{Al}$$

- Magnetic energy density

$$u_B = \frac{1}{2} \frac{B^2}{\mu_0}$$



- Similar to electric energy density

$$u_E = \frac{1}{2} \epsilon_0 E^2$$



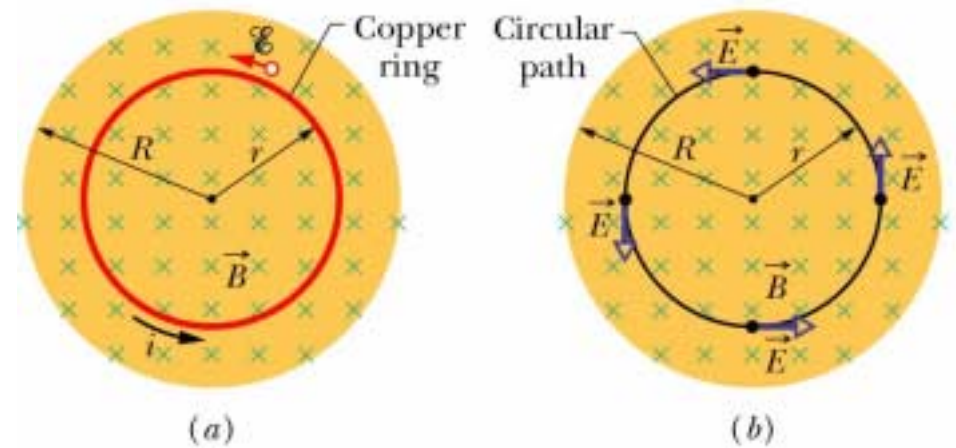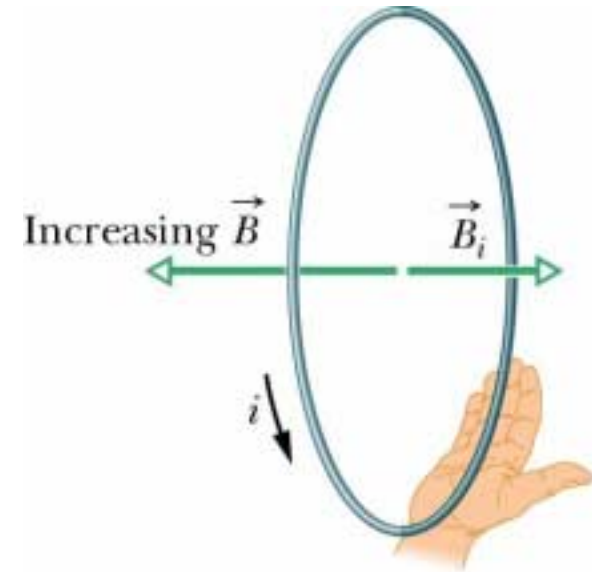
# Induced Electric Fields

- Put a copper ring in a uniform  $B$  field which is increasing in time so the magnetic flux through the copper ring is changing
- By Faraday's law an induced emf and current are produced
- If there is a current there must be an  $E$  field present to move the conduction electrons around ring


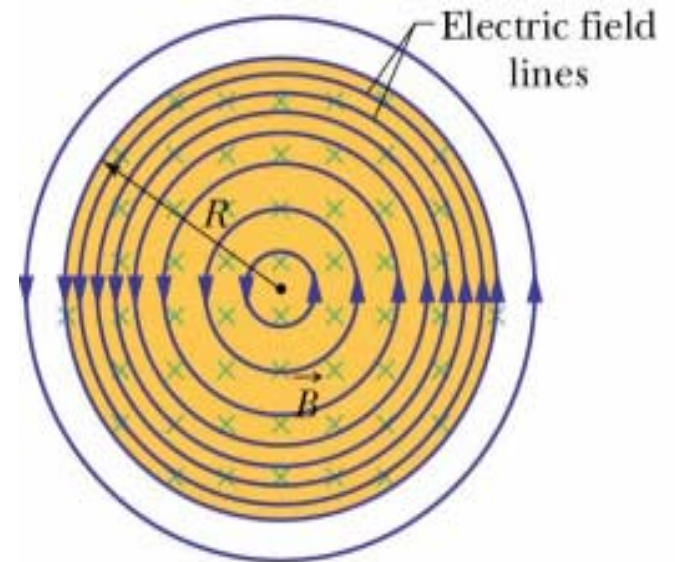
# Induced Electric Fields (Fig. 31-13)

- Induced  $E$  field acts the same way as an  $E$  field produced by static charges, it will exert a force,  $F=qE$ , on a charged particle
- True even if there is no copper ring (the picture shows a region of magnetic field increasing into the board which produces circular electric field lines).
- Restate Faraday's law – A changing  $B$  field produces an  $E$  field given by



$$\oint \vec{E} \cdot d\vec{s} = -\frac{d\Phi_B}{dt}$$