

Happy Halloween

Chapter 33 LC Circuits



RC circuits (chapter 28)

A resistor and capacitor in series

- Charging up a capacitor (switch to "a")

The loop rule gives


$$\mathcal{E} - iR - \frac{q}{C} = 0$$

$$\mathcal{E} = \frac{dq}{dt} R + \frac{q}{C}$$

- The solution of this differential equation is:

$$q = C \mathcal{E} (1 - e^{-t/\tau_c})$$

where $\tau_c = RC$


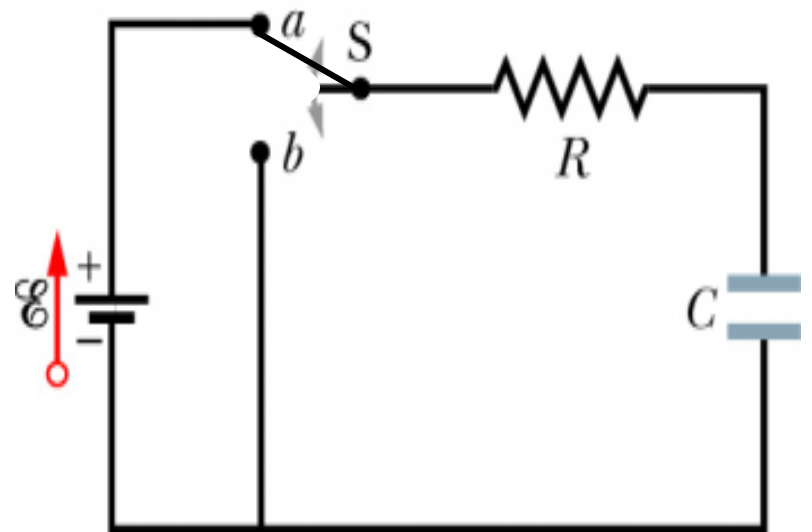


RC circuits (chapter 28)

- Graphical results

$$q = C \mathcal{E} (1 - e^{-t/\tau_c})$$
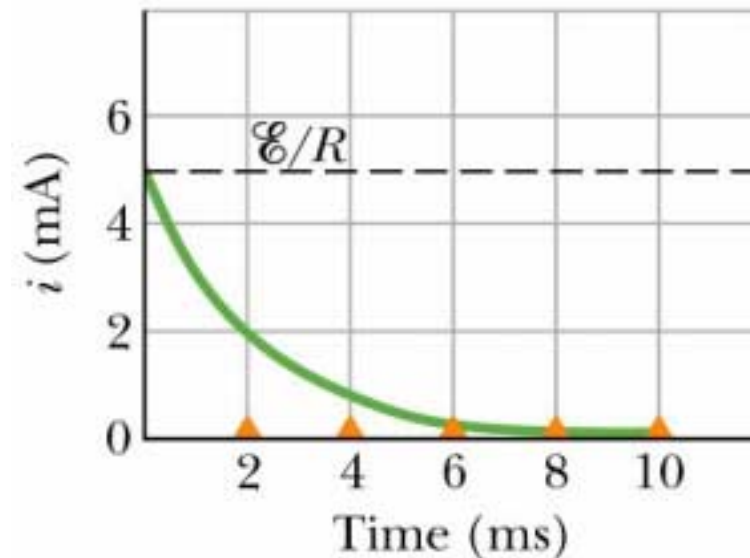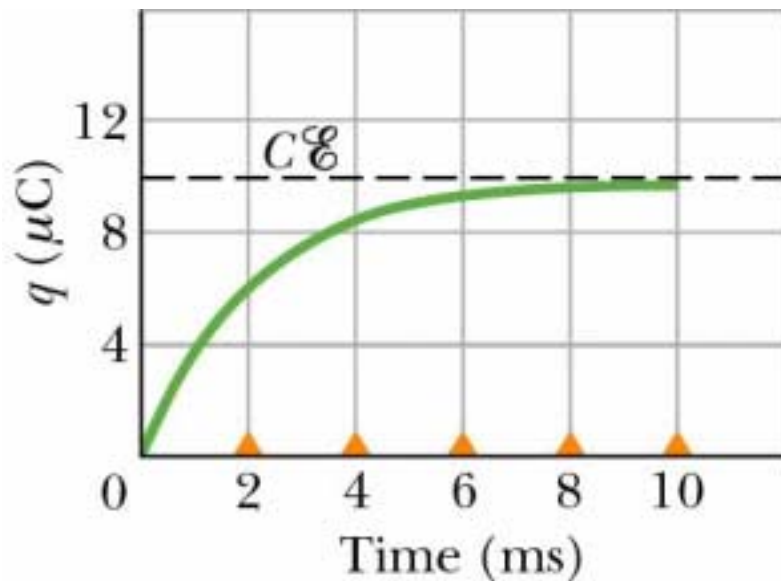
$$i = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/\tau_c}$$



- Initially the current flows easily, but then drops exponentially as the capacitor get filled up.

RC circuits (chapter 28)

- Discharging capacitor (switch to "b") gives the differential equation:


$$iR + \frac{q}{C} = 0$$

$$\frac{dq}{dt} R + \frac{q}{C} = 0$$

- The solution is

$$q = q_0 e^{-t/\tau_c}$$

$$\tau_c = RC$$

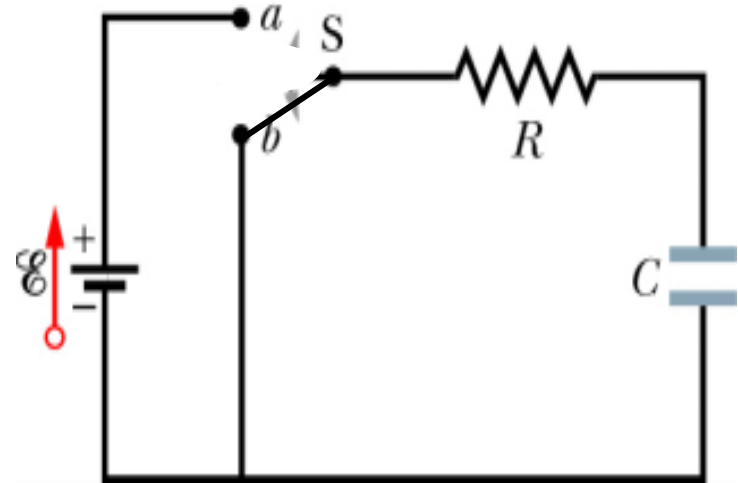

Emf for an Inductor (chapter 31)



$$N\Phi_B = Li$$

- **Self-inductance – changing current** through an inductor gives an emf (voltage change) across the inductor denoted by

$$\mathcal{E}_L = -\frac{d(N\Phi_B)}{dt} = -\frac{d(Li)}{dt}$$

$$\mathcal{E}_L = -L\frac{di}{dt}$$

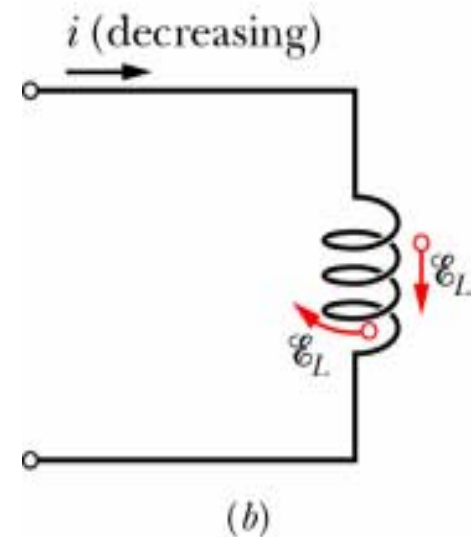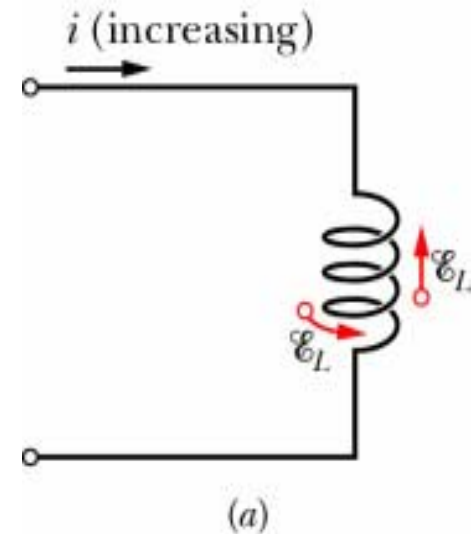- Note the sign of this emf goes against the current change



RL circuits (chapter 31 – Fig.17)

A resistor and inductor in series


- Charging up a inductor (switch to "a")

The loop rule gives

$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$

- The solution of this differential equation is:
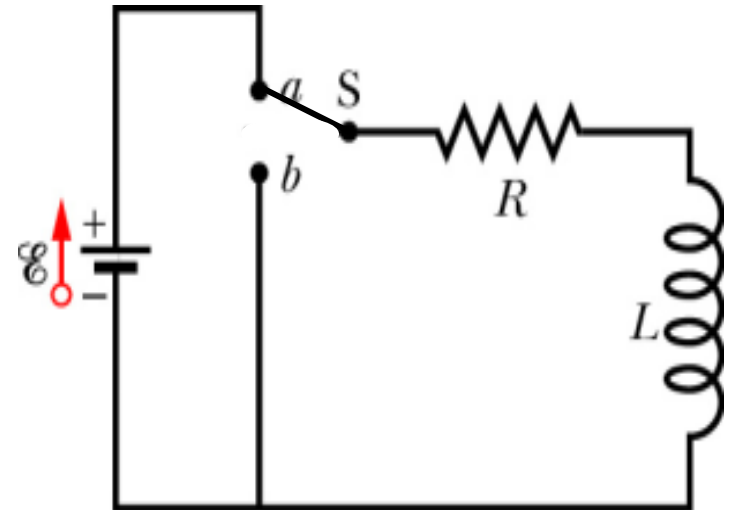
$$i = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau_L})$$



Where $\tau_L = \frac{L}{R}$



is the inductive time constant

RL circuits (chapter 31 Fig. 19)

- Graphical results

$$V_R = iR = \mathcal{E} (1 - e^{-t/\tau_L})$$
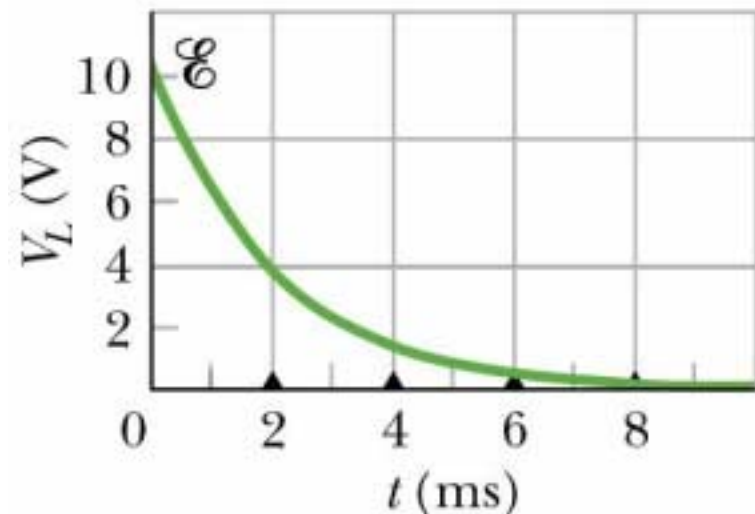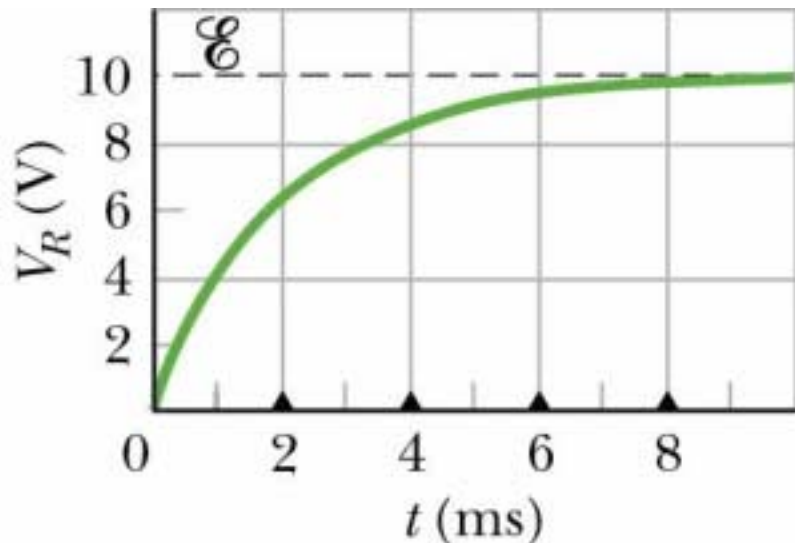
$$V_L = -L \frac{di}{dt} = \mathcal{E} e^{-t/\tau_L}$$



- Initially inductor acts to oppose changes in current ($i=0$).
- Long time later, inductor acts like simple wire with ($i=\mathcal{E}/R$).


RL circuits (chapter 31)

- Circuit is opened (switch to "b")

$$-iR - L \frac{di}{dt} = 0$$

$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$

$$\tau_L = \frac{L}{R}$$

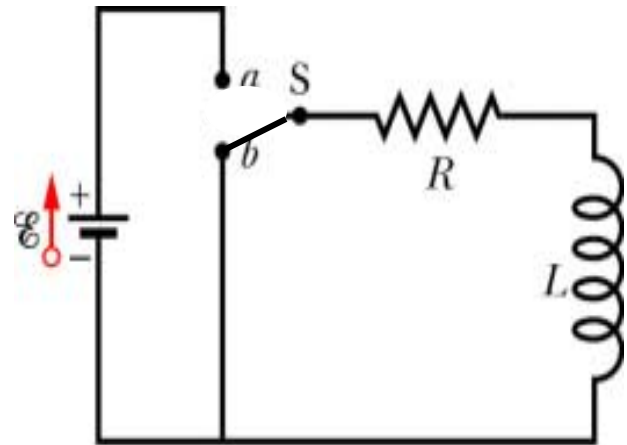

Energy stored in fields

- Energy stored in the electric field of a capacitor (chapter 28)

$$U_E = \frac{1}{2} \frac{q^2}{C}$$


- Energy stored in the B field of an inductor (chapter 31)

$$U_B = \frac{1}{2} Li^2$$

LC Circuits

- LC Circuit – inductor & capacitor in series
- Find q , i and V vary sinusoidally with period T (angular frequency ω)

$$\omega = \frac{2\pi}{T}$$

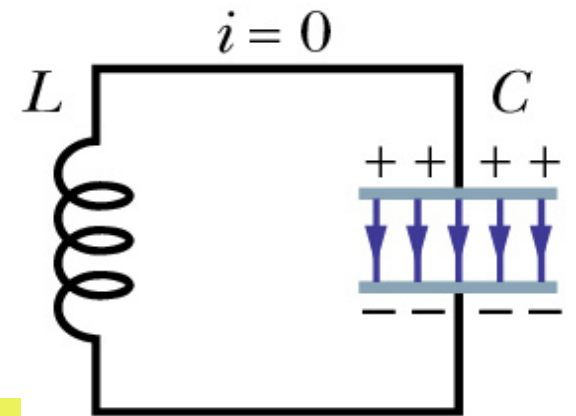

- E field of capacitor and B field of inductor oscillate
- The energy oscillates between E field stored in the capacitor and the B field stored in the inductor

$$U_E = \frac{1}{2} \frac{q^2}{C}$$

$$U_B = \frac{1}{2} Li^2$$



LC Circuits


- Total energy of LC circuit

$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}$$

- Analogy to block-spring system (183)
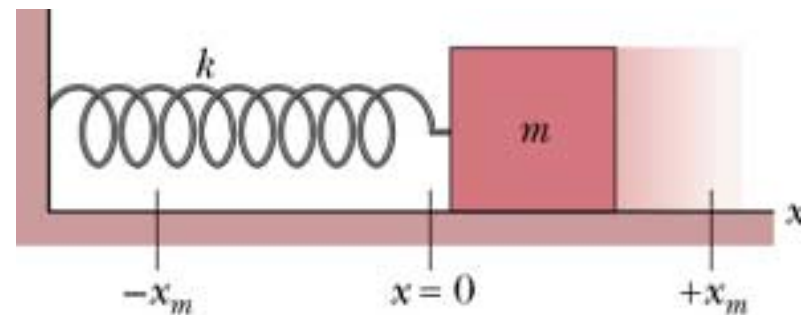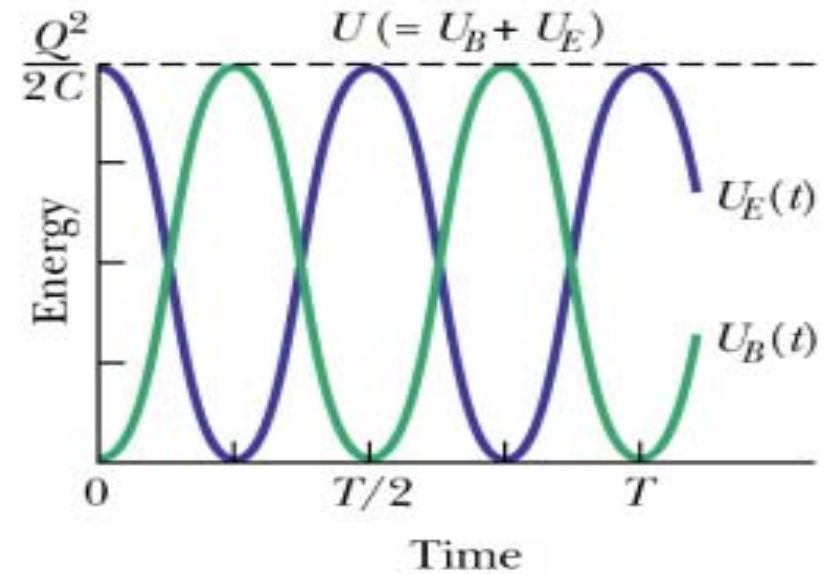
$$U = \frac{1}{2}mv^2 + \frac{1}{2}kx^2$$



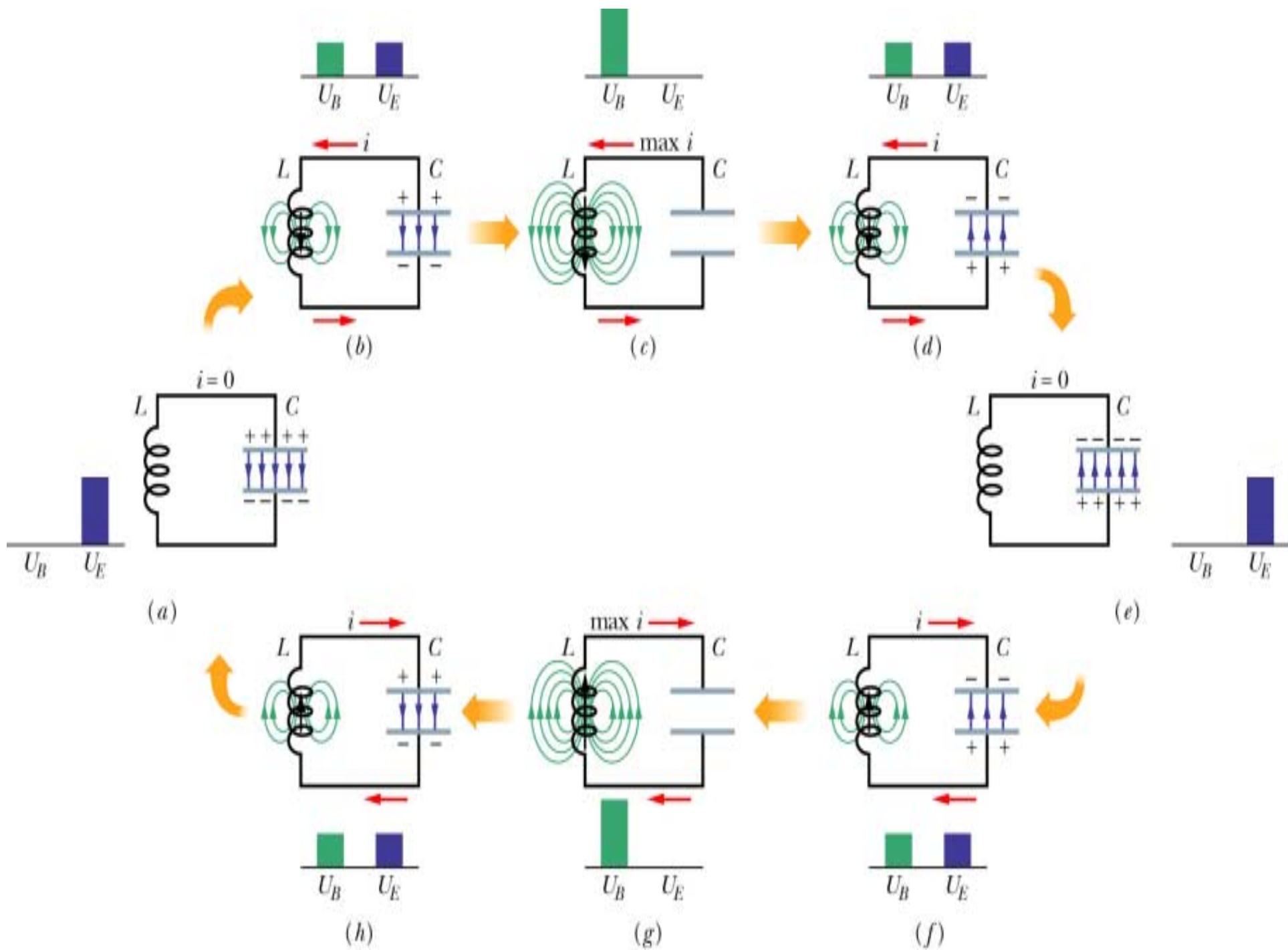

LC Circuits (checkpoint #1)

- A charged capacitor & inductor are connected in series at time $t=0$. In terms of period, T , how much later will the following reach their maximums:

- q of capacitor

$T/2$

- V_C with original polarity



T

- Energy stored in E field

$T/2$

- The current

$T/4$

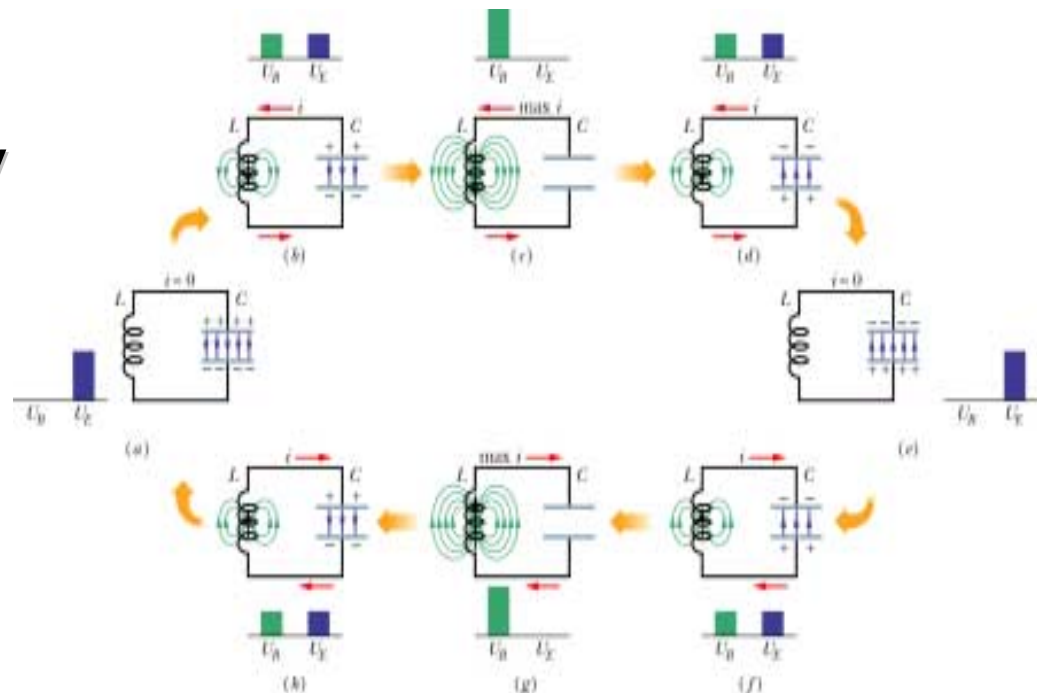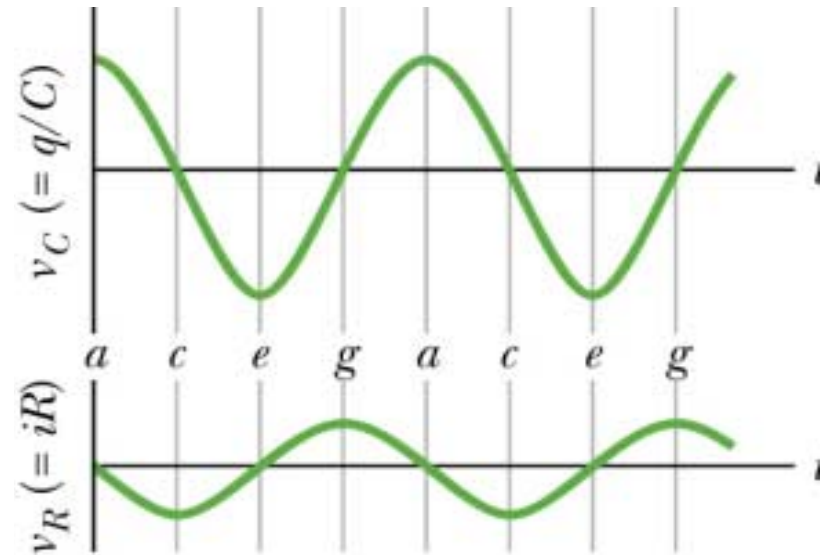

LC Circuits

- Total energy of LC circuit


$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}$$

- Total energy is constant

$$\frac{dU}{dt} = 0$$

- Differentiating gives
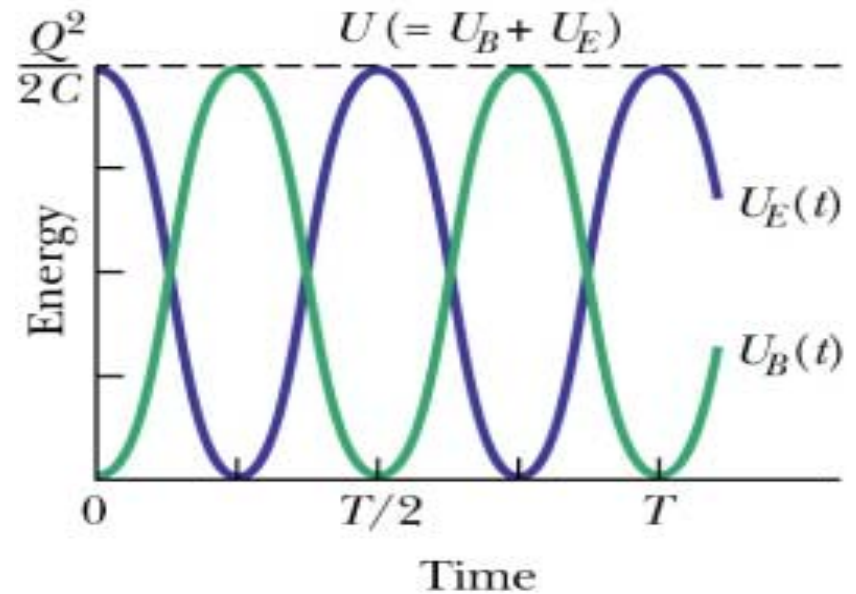
$$\frac{dU}{dt} = \frac{d}{dt} \left(\frac{Li^2}{2} + \frac{q^2}{2C} \right) = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = 0$$



LC Circuits

- Using $i = \frac{dq}{dt}$ $\frac{di}{dt} = \frac{d^2q}{dt^2}$

- We obtain $L \frac{d^2q}{dt^2} + \frac{1}{C} q = 0$

- Solution is $q = Q \cos(\omega t + \phi)$


- where q is the variable, Q is the amplitude (maximum value for q)

LC Circuits

- The phase constant, ϕ , is determined by the conditions at time $t=0$ (or some other time)

$$q = Q \cos(\omega t + \phi)$$

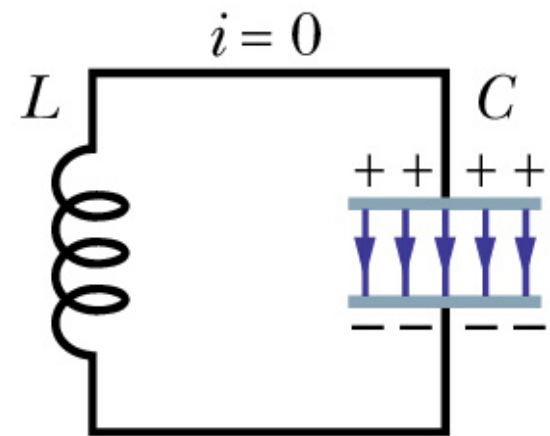- If $\phi = 0$ then at $t = 0$, $q = Q$
- I will take $\phi = 0$ for the rest of the lecture notes. To get the full result when you see ωt replace it by $\omega t + \phi$



LC Circuits

- Charge of LC circuit

$$q = Q \cos(\omega t)$$

- Find current by


$$i = \frac{dq}{dt}$$

$$i = \frac{d}{dt} [Q \cos(\omega t)] = -Q \omega \sin(\omega t)$$

- Amplitude I is

$$I = \omega Q$$

$$i = -I \sin(\omega t)$$

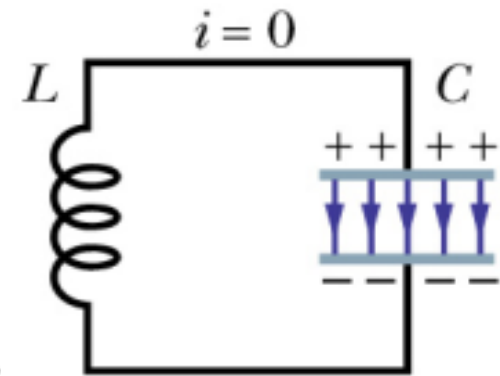

LC Circuits

- What is ω for an LC circuit?

$$q = Q \cos(\omega t)$$

$$\frac{d^2 q}{dt^2} = -\omega^2 Q \cos(\omega t)$$

- Substitute into

$$L \frac{d^2 q}{dt^2} + \frac{1}{C} q = 0$$

$$-L\omega^2 Q \cos(\omega t) + \frac{1}{C} Q \cos(\omega t) = 0$$

- Find ω for LC circuit is

$$\omega = \sqrt{\frac{1}{LC}}$$

LC Circuits

- The energy stored in an LC circuit at any time, t

$$U = U_B + U_E$$

- Substitute

$$q = Q \cos(\omega t)$$

$$i = -I \sin(\omega t)$$

$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2(\omega t)$$

$$U_B = \frac{Li^2}{2} = \frac{L}{2} \omega^2 Q^2 \sin^2(\omega t)$$

- Using

$$\omega = \sqrt{\frac{1}{LC}}$$


$$U_B = \frac{Q^2}{2C} \sin^2(\omega t)$$

LC Circuits

- Thus

$$U_E = \frac{Q^2}{2C} \cos^2(\omega t)$$
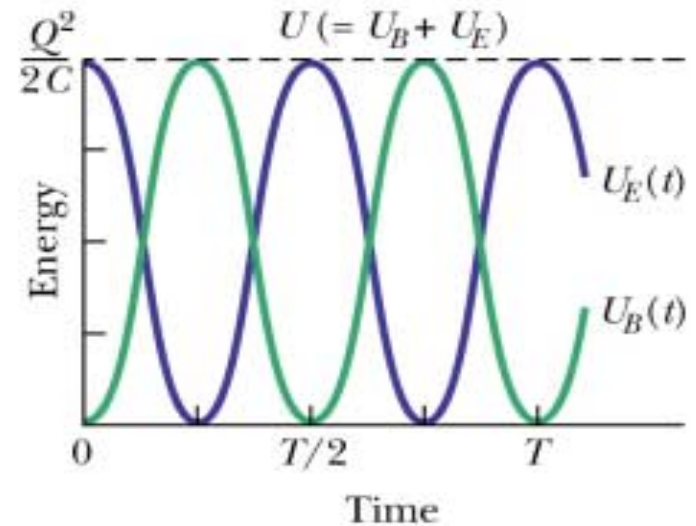
$$U_B = \frac{Q^2}{2C} \sin^2(\omega t)$$



- Maximum value for both

$$U_{E,\max} = U_{B,\max} = Q^2 / 2C$$

- At any instant, sum is $U = U_B + U_E = Q^2 / 2C$
- When $U_E = \max$, $U_B = 0$, and conversely, when $U_B = \max$, $U_E = 0$

LC Circuits (checkpoint #2)-quiz

- Capacitor in LC circuit has $V_{C,max} = 15\text{ V}$ and $U_{E,max} = 150\text{ J}$. When capacitor has $V_C = 5\text{ V}$ and $U_E = 50\text{ J}$, what are the


- 1) emf across the inductor?
- 2) the energy stored in the B field?

- Apply the loop rule

- Net potential difference around the circuit must be zero

$$V_L(t) = V_C(t)$$

$$U_{E,max} = U_E(t) + U_B(t)$$

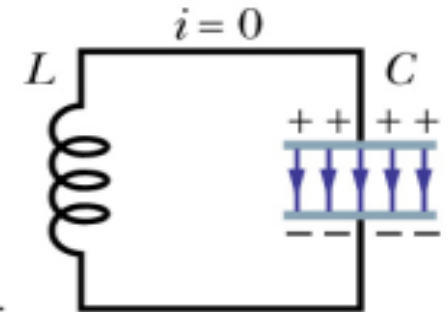

- | | a, | b, | c, | d, | e |
|----|----|-----|------|------|-------|
| 1) | 0, | 5, | 10, | 15, | 20 V |
| 2) | 0, | 50, | 100, | 150, | 200 J |