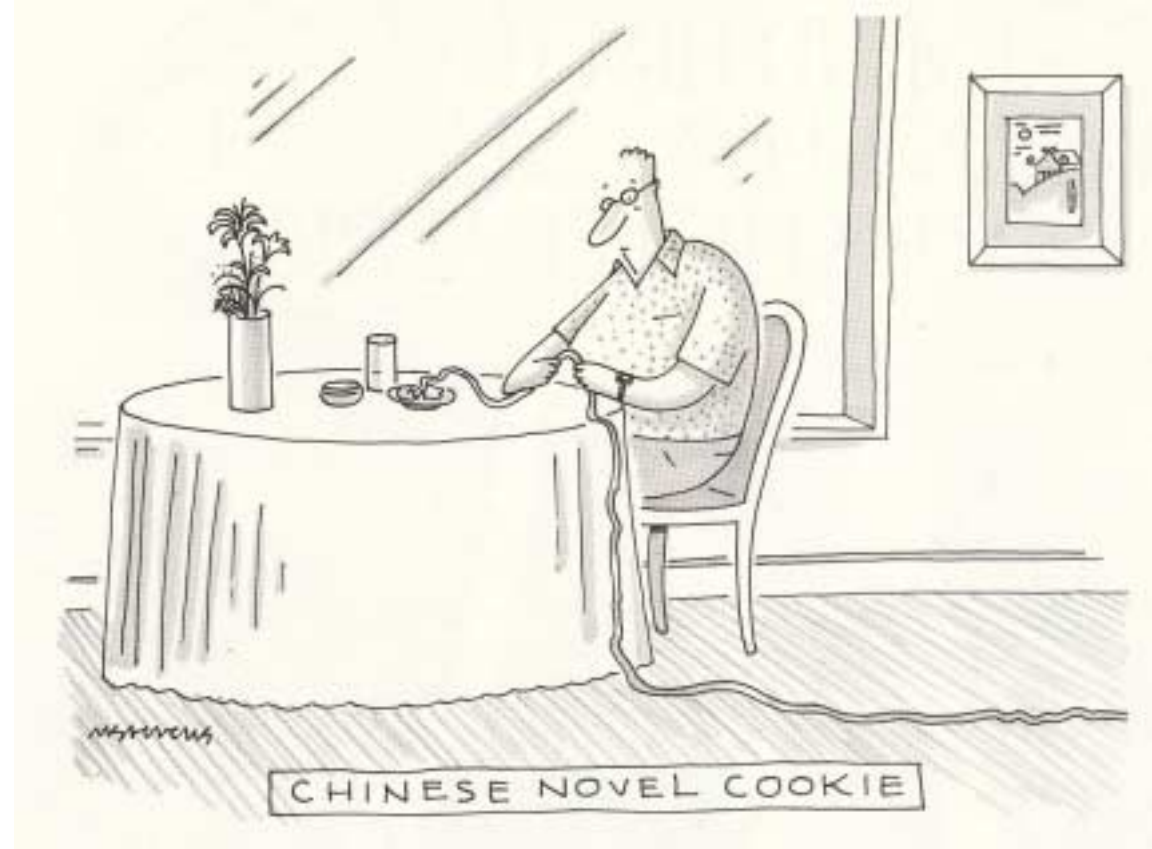


November  
24th

Review for  
midterm 3



# Schedule for rest of term

- Nov. 25 (Tues) - no class - Midterm-3 at 6pm
- Nov. 26 (Wed) – 8am midterm-3 make-ups
- Nov. 26 (Wed) – class – finish Chpt. 36
- Dec. 1-2 (Mon-Tues) – cover Chpt. 37
- Dec. 3-5 (Wed-Fri) – Review for final
- Dec. 3 (Wed) – HW set #12 due
- Dec. 8 (Mon) – Corrections #3 due
- Dec. 8 (Mon) – 5:45-7:45 pm Final Exam
  - N130 BCC (Business College) for section 1
  - 158 NR (Natural Resources) for section 2

# Midterm-3

- Tuesday November 25 at 6pm
  - Section 1 – N100 BCC (Business College)
  - Section 2 – 158 NR (Natural Resources)
- Allowed one sheet of notes (both sides) and calculator
- Covers Chapters 32-35 (HW sets 9,10, and 11)
- Need photo ID
- Send me an email if you have another class on Tuesday night - **tell me which class it is** - makeup will be on Wednesday morning.
- Use the help-room to prepare

# Elements of RLC circuits

Resistor

Inductor

Capacitor

- Energy stored

$$U = 0$$

$$U_B = \frac{1}{2} Li^2$$

$$U_E = \frac{1}{2} \frac{q^2}{C}$$

- Voltage change

$$V = iR$$

$$V = -L \frac{di}{dt}$$

$$V = \frac{q}{C}$$

- Power lost

$$P = i^2 R$$

$$P = 0$$

$$P = 0$$

# LC Circuits

- Charge

$$q = Q \cos(\omega t)$$


- Current

$$i = \frac{dq}{dt} = -Q\omega \sin(\omega t)$$

- Angular frequency

$$\omega = \sqrt{\frac{1}{LC}}$$

- No power loss

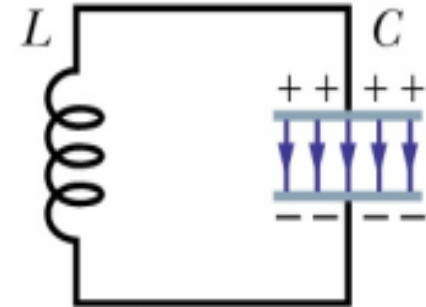

# RLC circuits

- Charge on capacitor


$$q = Qe^{-Rt/2L} \cos(\omega't)$$

- Angular frequency

$$\omega' = \sqrt{\omega^2 - (R/2L)^2}$$

- Natural frequency

$$\omega = \sqrt{\frac{1}{LC}}$$

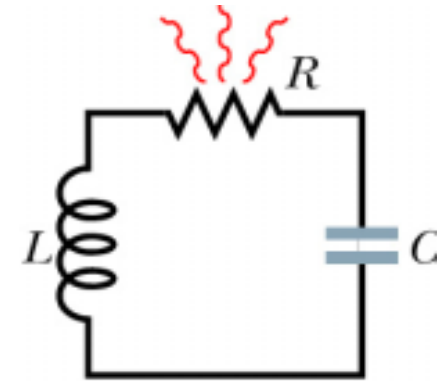

# AC circuits

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t, \quad \omega_d = \text{driving frequency}$$

Resistive load

$$I_R = \frac{V_R}{R}$$

Capacitive load

$$I_C = \frac{V_C}{X_C}$$




$$X_C = \frac{1}{\omega_d C}$$

Inductive load

$$I_L = \frac{V_L}{X_L}$$


$$X_L = \omega_d L$$
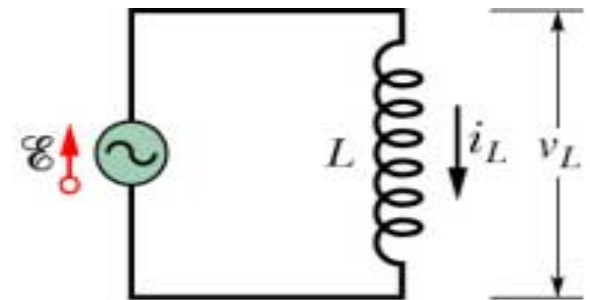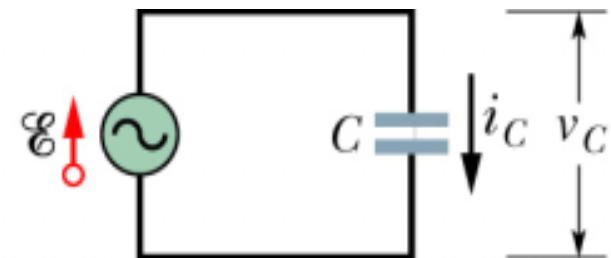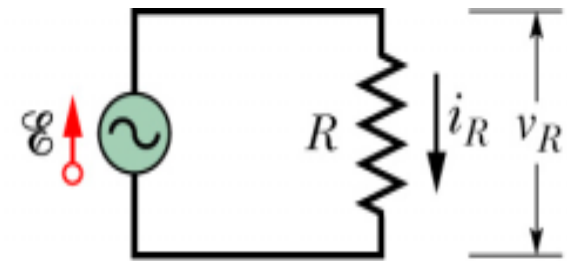
$$V_x = \mathcal{E}_m, \quad x = R, C, L$$



$X$  is the reactance

# AC circuits

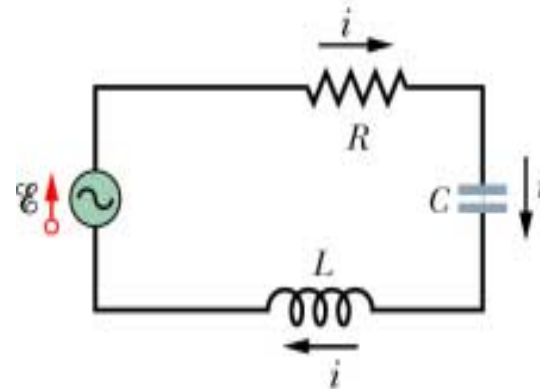

- Current (same everywhere)  $i = I \sin(\omega_d t - \phi)$

- Solution  $I = \frac{\mathcal{E}_m}{Z}$   $\tan \phi = \frac{X_L - X_C}{R}$   $\frac{X_L}{X_C} = \frac{(\omega_d)^2}{\omega^2}$

- $Z$  is the impedance  $Z = \sqrt{R^2 + (X_L - X_C)^2}$

- $I$  is maximum on resonance where

$$X_L = X_C$$

$$Z = R$$


$$\omega_d = \omega$$



# Transformer

$$I_S = I_P \frac{N_P}{N_S}$$

$$V_S = V_P \frac{N_S}{N_P}$$

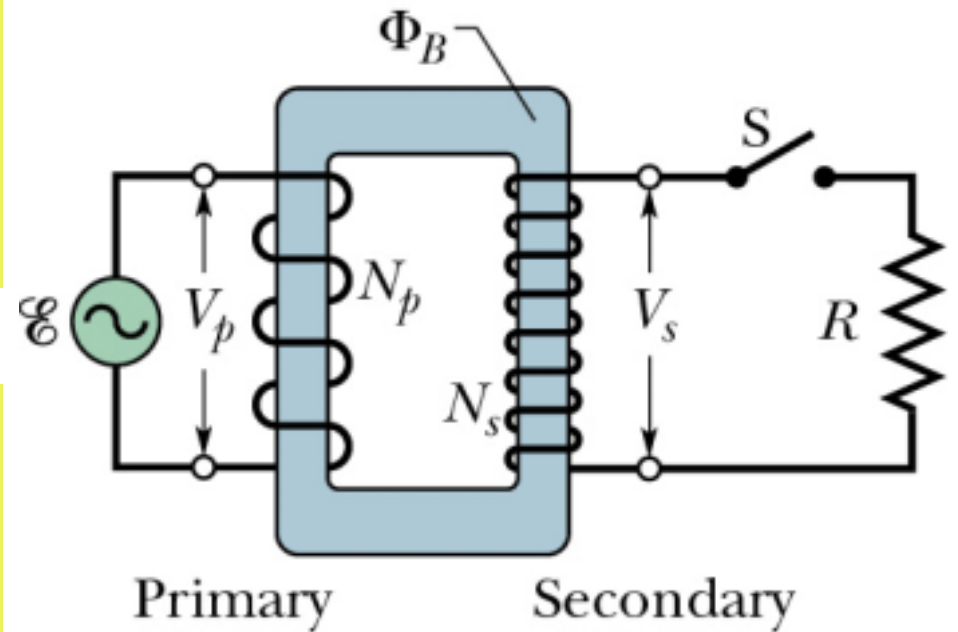


# EM Waves

$$E = E_m \sin(kx - \omega t)$$

$$B = B_m \sin(kx - \omega t)$$
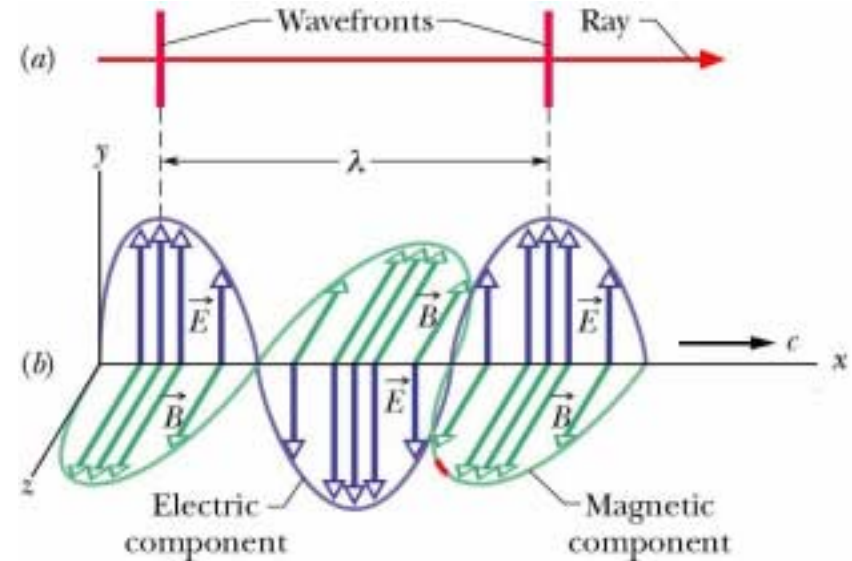
$$c = \frac{E}{B} = \frac{1}{\sqrt{\mu_0 \epsilon_0}} = 3 \times 10^8 \text{ m/s}$$



Direction and power per unit area

$$\vec{S} = \frac{1}{\mu_0} \vec{E} \times \vec{B}$$


Intensity  $I = \frac{1}{\mu_0 c} E_{rms}^2$

Pressure  $p_r = \frac{I}{c}$   $p_r = \frac{2I}{c}$

absorption reflection
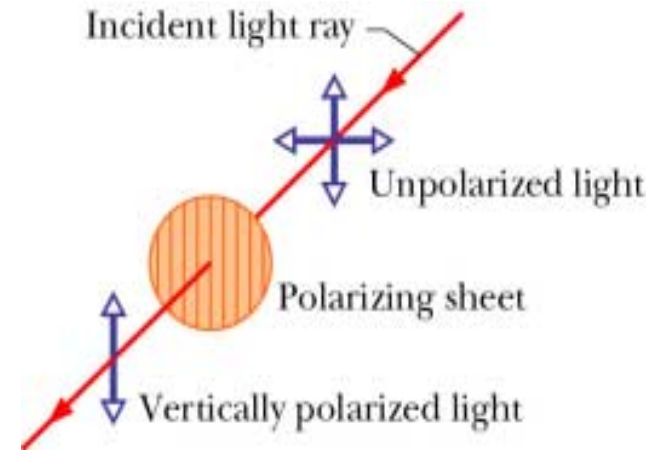
# Polarization

- Polarization is the direction of the  $E$  field
- Intensity of **unpolarized** light with intensity  $I_0$  after hitting a polarizing sheet
- Intensity of **polarized** light with intensity  $I_0$  after hitting a polarizing sheet



$$I = \frac{1}{2} I_0$$

$$I = I_0 \cos^2 \theta$$

# Reflection & Refraction (Fig. 34-17)

- Reflection:  $\theta'_1 = \theta_1$
- Refraction (Snell's law)

$$n_2 \sin \theta_2 = n_1 \sin \theta_1$$


- Index of refraction

$$n = \frac{\text{speed in vacuum}}{\text{speed in medium}} = \frac{c}{v}$$

$$\frac{v_1}{v_2} = \frac{\lambda_1}{\lambda_2} = \frac{n_2}{n_1}$$

Frequency does not change with  $n$

$$f = \lambda/v$$

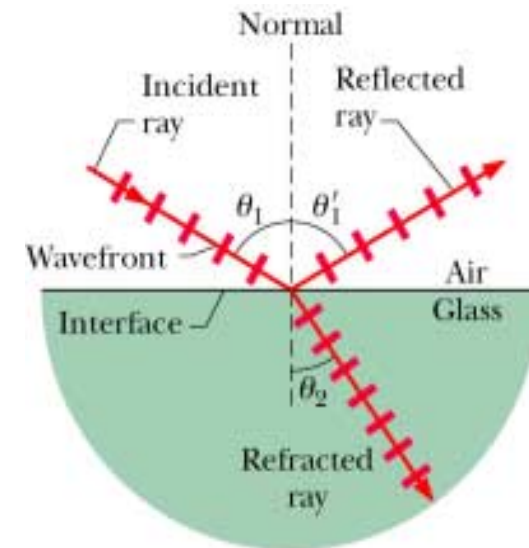

- Critical angle (no refracted wave)

$$\theta_c = \sin^{-1} \frac{n_2}{n_1}$$

# Mirrors

- **Plane** – flat mirror
- **Concave** – caved in towards object
- **Convex** – flexed out away from object




$$\frac{1}{p} + \frac{1}{i} = \frac{1}{f}$$

$$f = \frac{1}{2} r$$

- $r$  = radius of curvature
- $f$  = focal length,  $f > 0$  concave,  $f < 0$  convex
- $p$  = position of object
- $i$  = position of image
- **real images** on side where object is
- **virtual images** on opposite side
- **lateral magnification:**

$$|m| = \frac{h'}{h}$$

$$m = -\frac{i}{p}$$

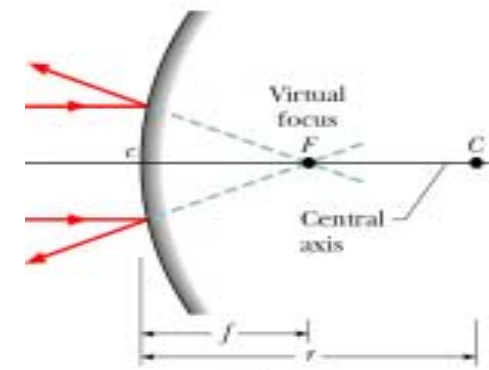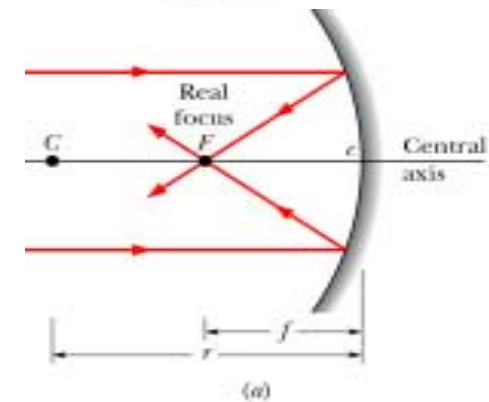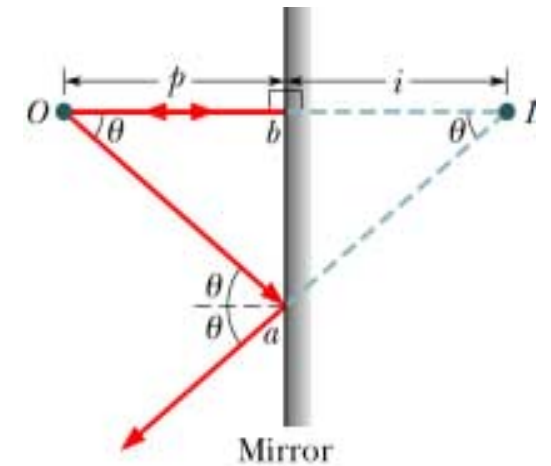

# Thin lenses




- **Real images:** opposite side - **virtual images:** same side
- **Diverging lens** ( $f < 0$ ): smaller, same orientation, virtual images
- **Converging lens** ( $f > 0$ ): both real and virtual images
- Image position and magnification:

$$\frac{1}{p} + \frac{1}{i} = \frac{1}{f}$$

$$m = -\frac{i}{p}$$

- **Lens maker's equation:**
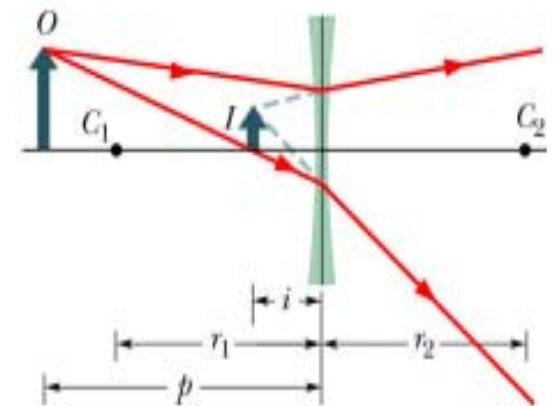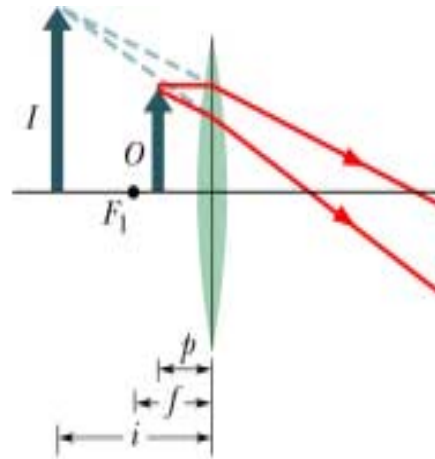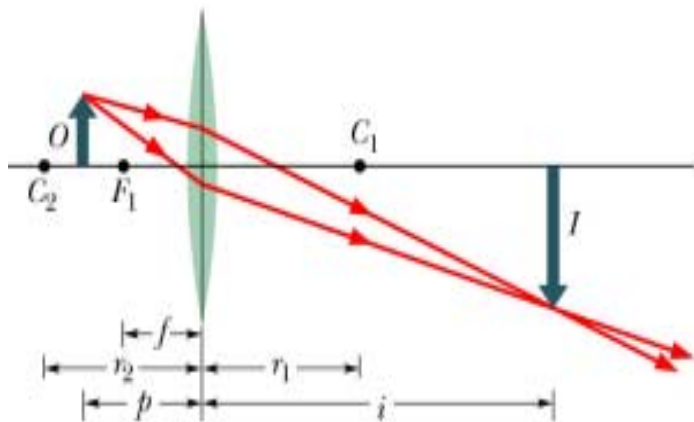
$$\frac{1}{f} = (n - 1) \left( \frac{1}{r_1} - \frac{1}{r_2} \right)$$



# Mirrors

Mirror Type	Object Location	Image Location	Image Size	Image Type	Image Orientation	Sign of $f$	Sign of $i$	Sign of $m$
Plane	Anywhere	$i = -p$	Equal	Virtual	Same	$\infty$	-	<b>+1</b>
Concave	$p < f$	Anywhere	Bigger	Virtual	Same	+	-	+
Concave	$f < p < 2f$	$i > 2f$	Bigger	Real	Invert	+	+	-
Concave	$p = 2f$	$i = 2f$	Equal	Real	Invert	+	+	-
Concave	$p > 2f$	$2f > i > f$	Smaller	Real	Invert	+	+	-
Convex	Anywhere	$ i  <  f $	Smaller	Virtual	Same	-	-	+

# Thin lenses

Converging lens = concave mirror

Diverging lens = convex mirror

Thin Lens Type	Object Location	Image Location	Image Size	Image Type	Image Orientation	Sign of $f$	Sign of $i$	Sign of $m$
Converging	$p < f$	Anywhere	Bigger	Virtual	Same	+	-	+
Converging	$f < p < 2f$	$i > 2f$	Bigger	Real	Invert	+	+	-
Converging	$p = 2f$	$i = 2f$	Equal	Real	Invert	+	+	-
Converging	$p > 2f$	$2f > i > f$	Smaller	Real	Invert	+	+	-
Diverging	Anywhere	$ i  <  f $	Smaller	Virtual	Same	-	-	+