

September 17th

Chapter 26
Capacitance


Capacitance

- Parallel-plate capacitor charged to potential V by battery
- Disconnect battery to have an isolated system
- If the distance, d , between the plates is decreased what happens to C ?

LARGER

- What happens to V ?

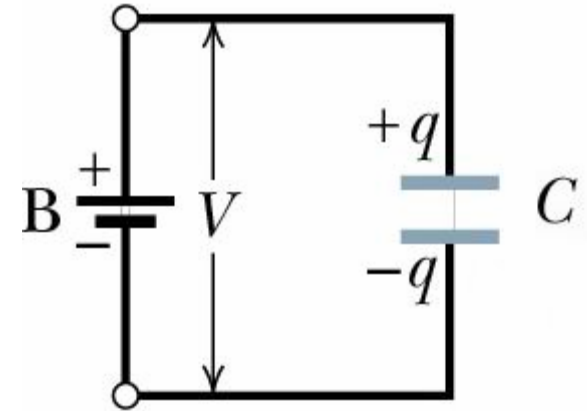Isolated system q stays same so V decreases if C increases



$$C = \frac{\epsilon_0 A}{d}$$


$$V = \frac{q}{C}$$

Capacitance

- What if we have more than one capacitor in a circuit?
 - Replace combination with an equivalent capacitance C_{eq}
- Two basic combinations
 - Parallel
 - Series

Capacitance (Fig. 26-7)

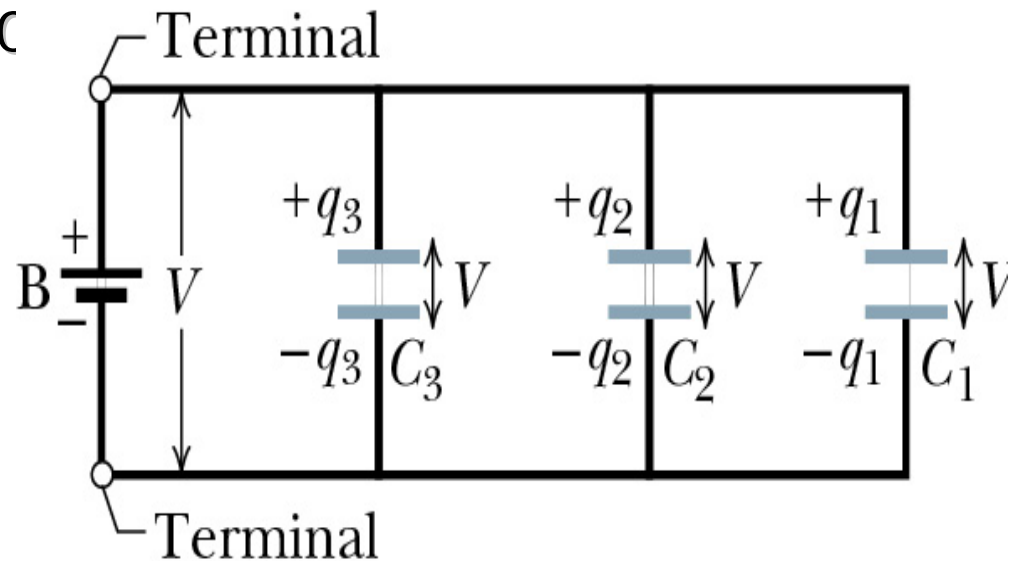- Capacitors in parallel
- Capacitors are directly wired together at each plate and V applied across the group of plates
- V is same across all capacitors



$$V_1 = V_2 = V_3 = V$$


Capacitance (Fig. 26-7)

- Capacitors in parallel
- Total q stored on capacitors is sum of the charges of all capacitors


$$q = q_1 + q_2 + q_3$$

- C_{eq} has total charge q and same V as original capacitors

$$C_{eq} = \frac{q}{V}$$

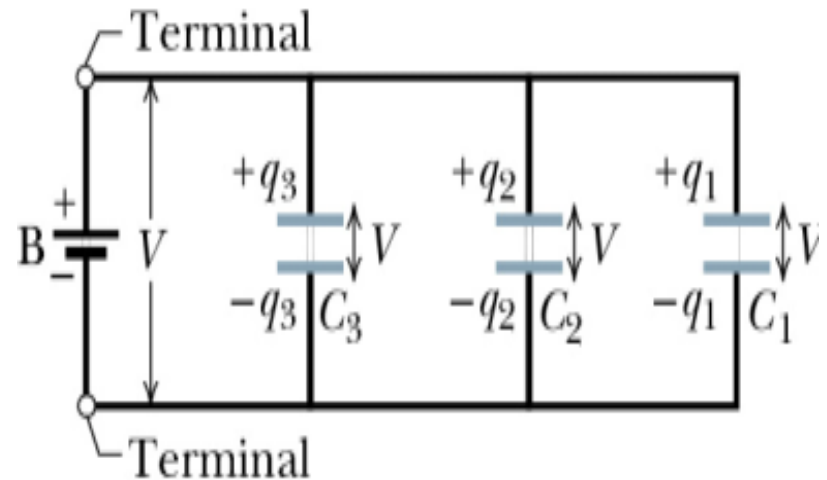

(a)

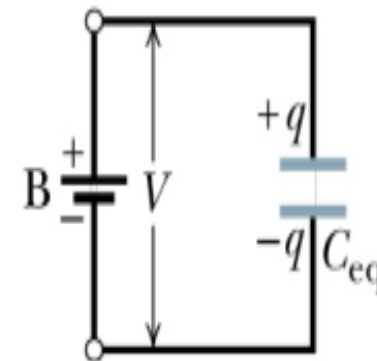

(b)

Capacitance (Fig. 26-7)

- Capacitors in parallel


$$q = q_1 + q_2 + q_3$$

$$q_1 = C_1 V \quad q_2 = C_2 V \quad q_3 = C_3 V$$


$$q = (C_1 + C_2 + C_3) V$$

$$C_{eq} = C_1 + C_2 + C_3$$

$$C_{eq} = \sum_i^n C_i$$

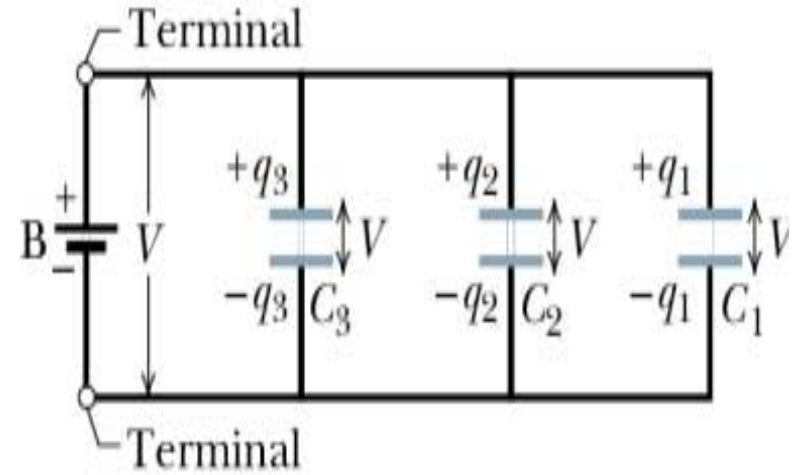

(a)

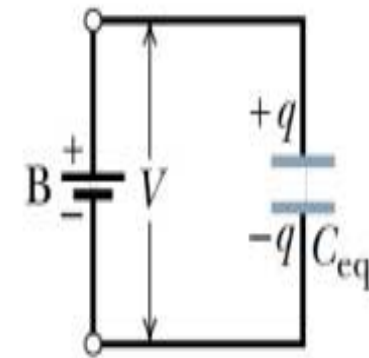

(b)


Capacitance (Fig. 26-8)

- Capacitors in series
- Capacitors are wired one after the other and V is applied across the two ends of the series

- Capacitors have identical q

$$q_1 = q_2 = q_3 = q$$

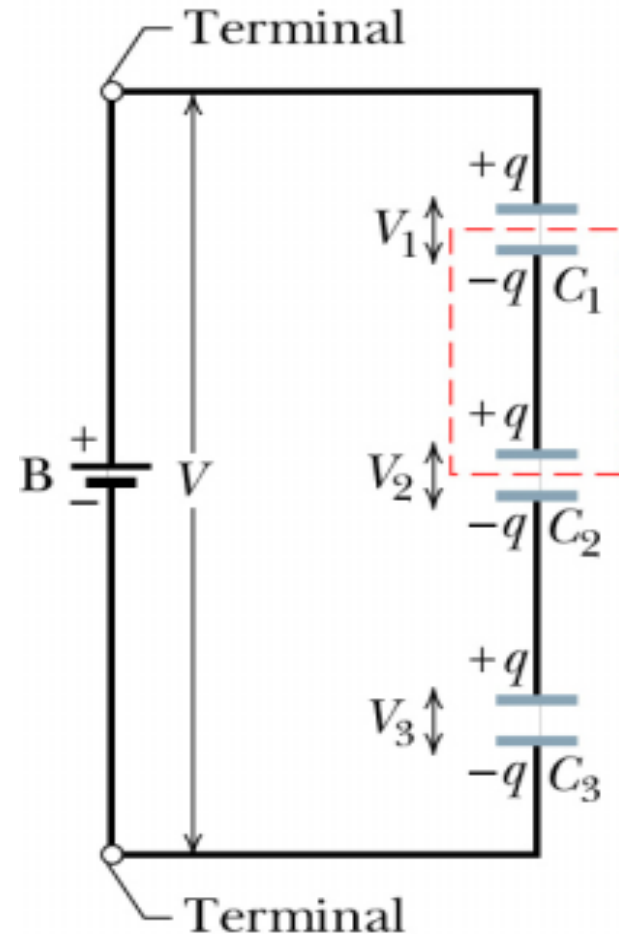- Battery produces q only on top and bottom plates, induced q on other plates





Capacitance (Fig. 26-8)

- Capacitors in series
- Sum of V across all capacitors is equal to applied V

$$V = V_1 + V_2 + V_3$$

- C_{eq} has same q and total V as original capacitors

$$C_{eq} = \frac{q}{V}$$

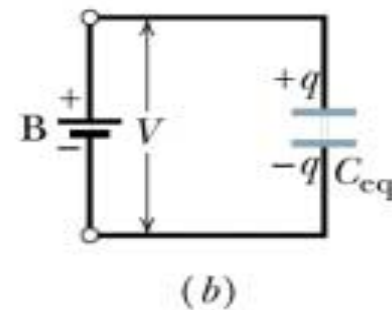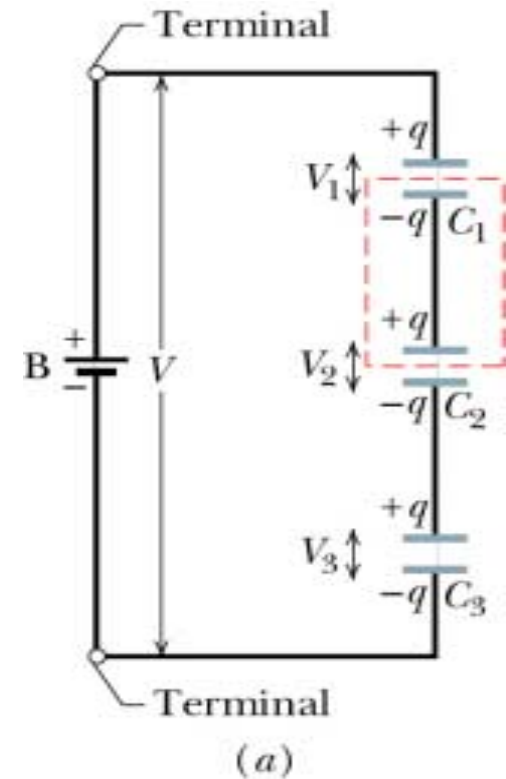

Capacitance (Fig. 26-8)

- Capacitors in series

$$V = V_1 + V_2 + V_3$$


$$V_1 = \frac{q}{C_1}$$

$$V_2 = \frac{q}{C_2}$$


$$V_3 = \frac{q}{C_3}$$

$$V = q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$
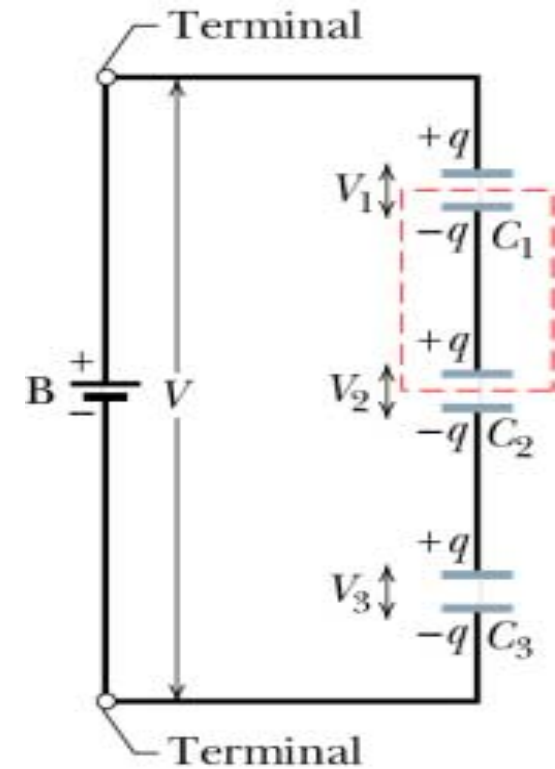
$$\frac{1}{C_{eq}} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$



(a)

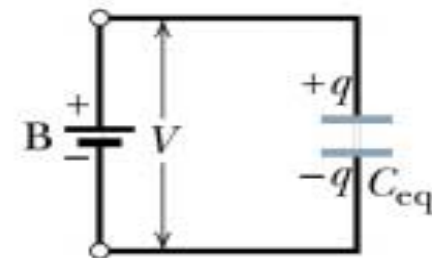


(b)

Capacitance (Fig. 26-8)


- Capacitors in series
- Charge can only be shifted from one capacitor to another.

$$\frac{1}{C_{eq}} = \sum_i^n \frac{1}{C_i}$$

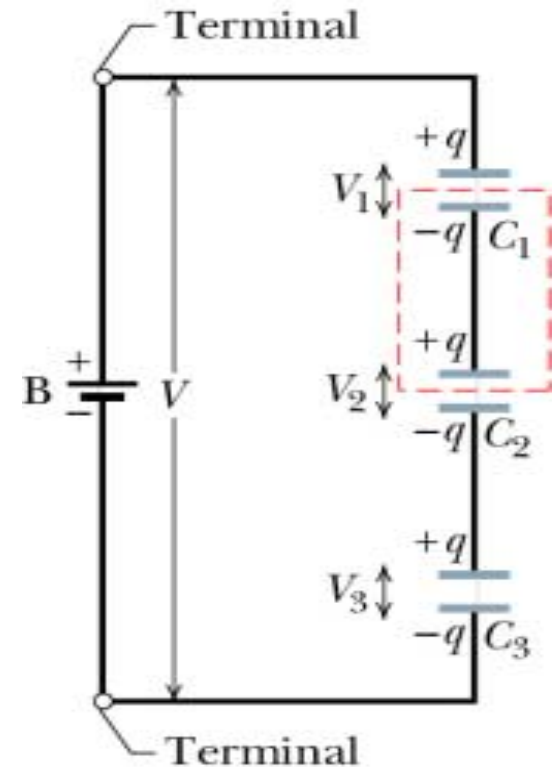- C_{eq} is always less than smallest capacitance



(a)

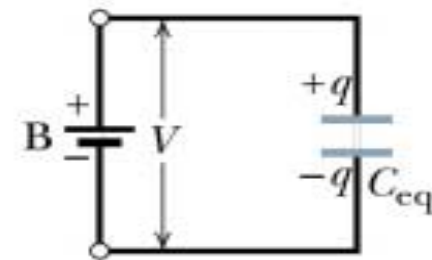

(b)

Capacitance


- Capacitors in parallel
 - V across each is equal
 - Total q is sum
 - Multiple paths for q

- Capacitors in series
 - q is equal on each
 - Total V is sum
 - One path for q

$$C_{eq} = \sum_i^n C_i$$

$$\frac{1}{C_{eq}} = \sum_i^n \frac{1}{C_i}$$

Capacitance (Fig. 26-9)




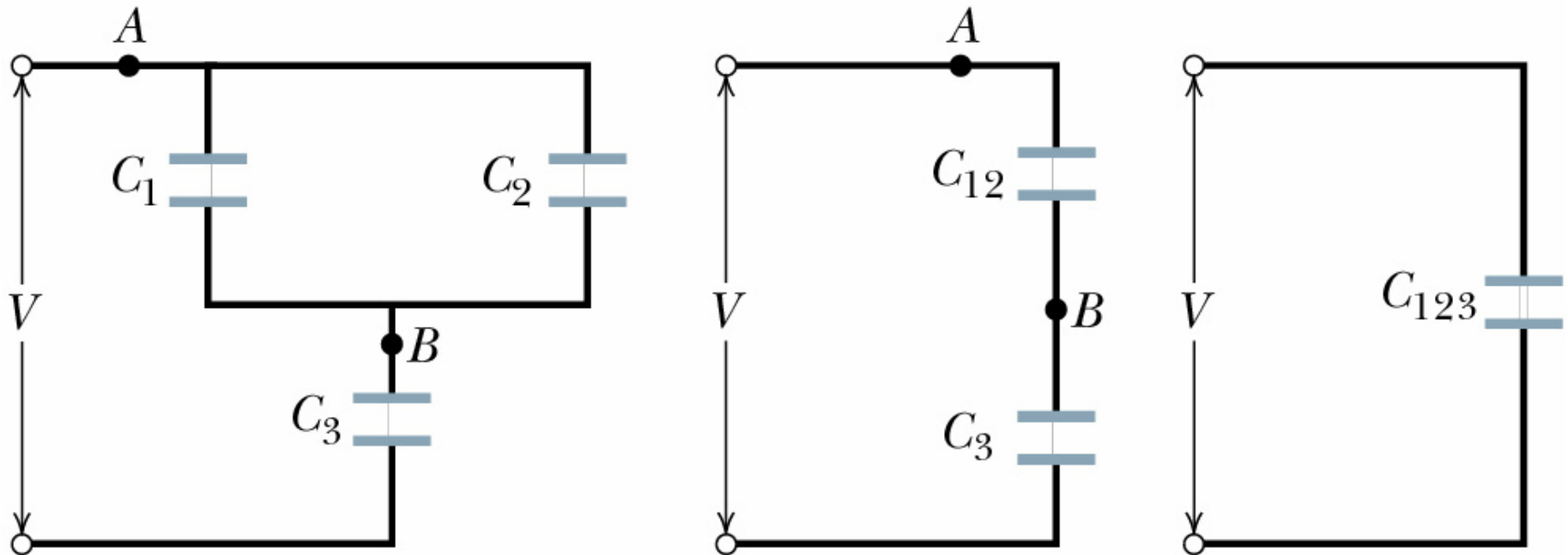


$$C_1 = 12\mu\text{F}, \quad C_2 = 5.3\mu\text{F}, \quad C_3 = 4.5\mu\text{F}, \quad V = 12.5\text{V}$$

What is the charge on C_1 ?

Capacitance (Question #4)

These are all
the same

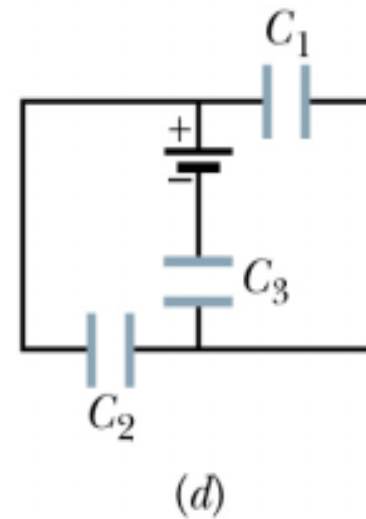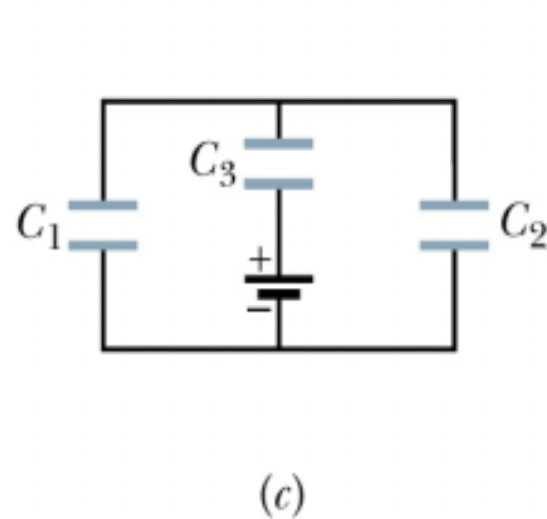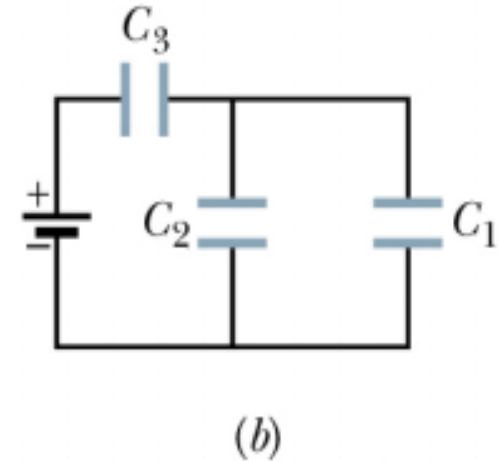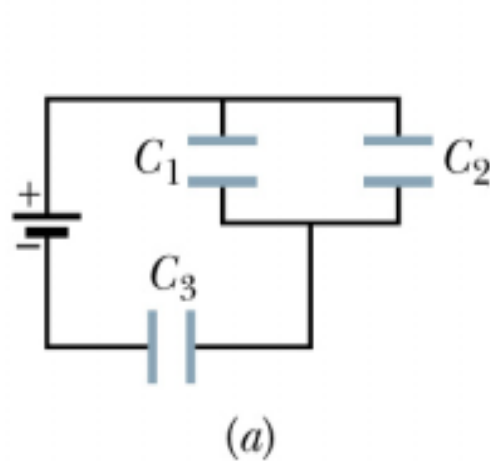

Capacitance (Checkpoint #3)

- A battery with V stores total charge q on two identical capacitors
- a) What is V across and q on either capacitor if they are in parallel?
- V is same for each and equal to V of battery.
- Total charge conserved and $q = q_1 + q_2$
- BUT $q_1 = q_2$ SO $q_{cap} = \frac{q}{2}$

Capacitance (Checkpoint #3)

- A battery with V stores charge q on two identical capacitors
- b) What is V across and q on either capacitor if they are in series?
- q is same for each
- V is sum of V across capacitors

$$V = V_1 + V_2$$

- BUT $V_1 = V_2$ SO $V_{cap} = \frac{V}{2}$