

September 29th

Circuits - Chapter 28

# Review of Chpt. 27

- **Current**,  $i$ , is defined as amount of charge  $q$  passing through plane in time  $t$

$$i = \frac{dq}{dt}$$


- SI unit **ampere**, A

$$1A = 1C/s$$

- Charge is conserved

$$i_0 = i_1 + i_2$$

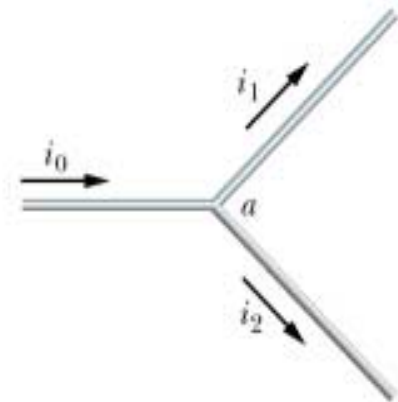- Current arrow drawn in the direction (+) charge carriers would move (actually it is the electrons that move).



# Review of Chpt. 27

- **Resistance** is defined as
- SI unit is the **ohm**,  $\Omega$

$$1\Omega = 1V / A$$

- Resistance of conducting wire of length  $L$ , **resistivity**  $\rho$ , and cross section  $A$

- **Ohm's Law** –  $R$  is independent of magnitude and polarity of  $V$

$$R = \frac{V}{i}$$

$$R = \rho \frac{L}{A}$$

$$V = iR$$

# Review of Chpt. 27

- Power :


$$P = Vi$$

- For a resistive device, the power dissipated in the resistor is:


$$P = i^2 R = \frac{V^2}{R}$$
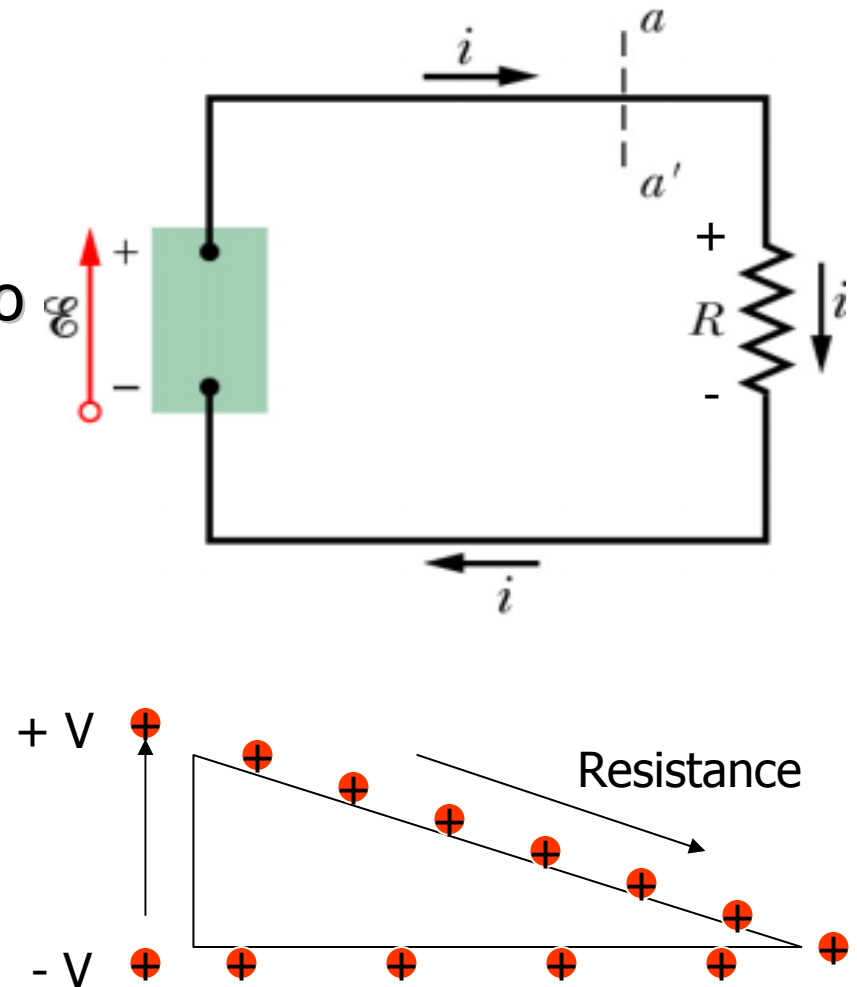
# Circuits (Fig. 28-1)

- **emf device** (label terminal at higher  $V$  as + and lower  $V$  as -)
- Draw emf,  $\mathcal{E}$ , arrow from - to + terminal
- Label the  $R$  with a + and -
- + charge carriers are moved against the *Electric* field in emf device from lower (-) to higher (+)  $V$ . The emf must do work on the charge. Normally this is supplied by chemical energy.



# Circuits (Fig. 28-3)

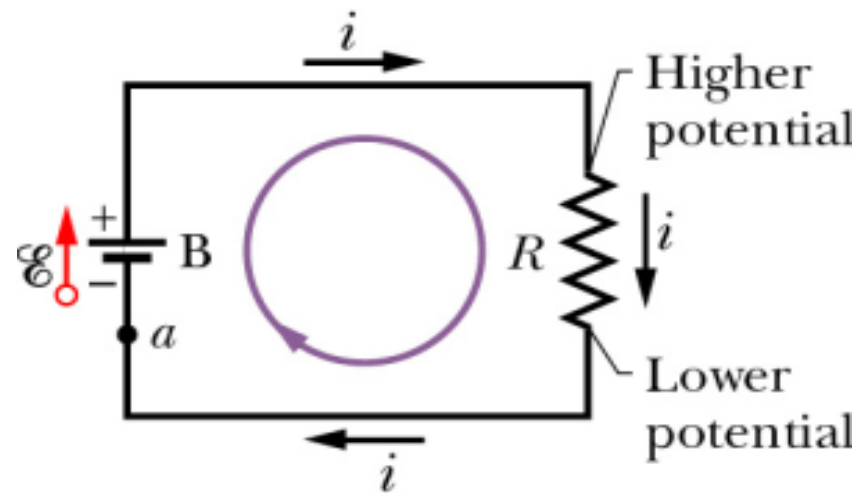


Ohm's Law:

$$E = iR$$

(the  supplies the potential difference  $V$ )

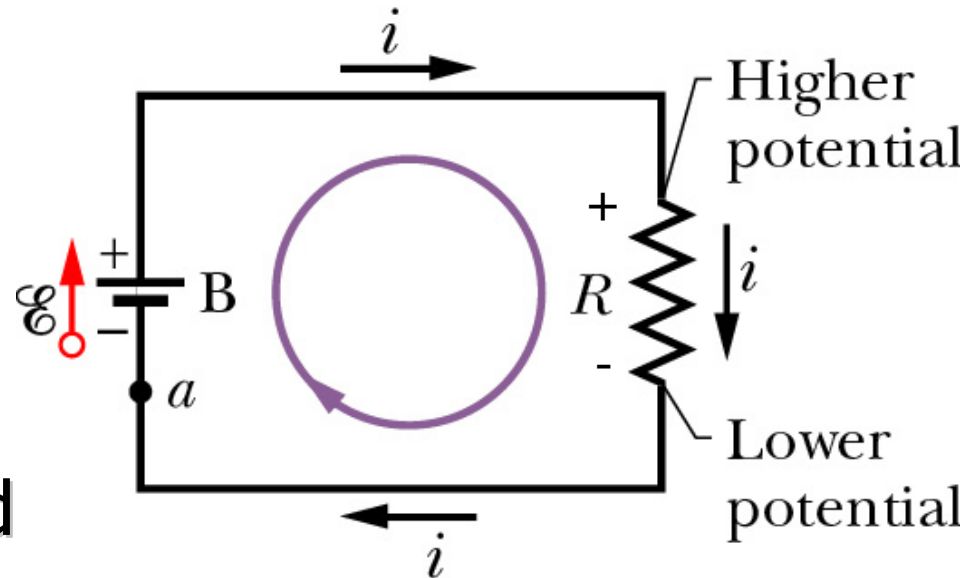
# Circuits (Fig. 28-3)

- Calculate the current in single-loop circuit
- Use potential method (as called by the text book).
- Travel around circuit in either direction and algebraically add potential differences


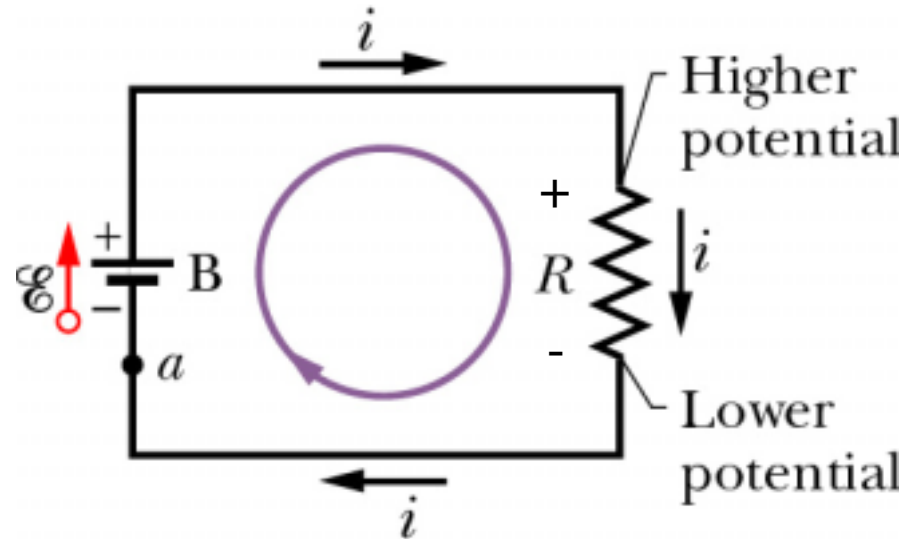
# Circuits (Fig. 28-3)

- Start at point  $a$  with potential  $V_a$
- Move clockwise around circuit
- Pass through battery moving to higher  $V$ , change in  $V$  is  $+E$
- Neglect resistance of connecting wires



$$V_a + E$$




# Circuits (Fig. 28-3)

- Top of resistor at same  $V$  as battery
- Pass through resistor  $V$  decreases and

$$V = iR$$

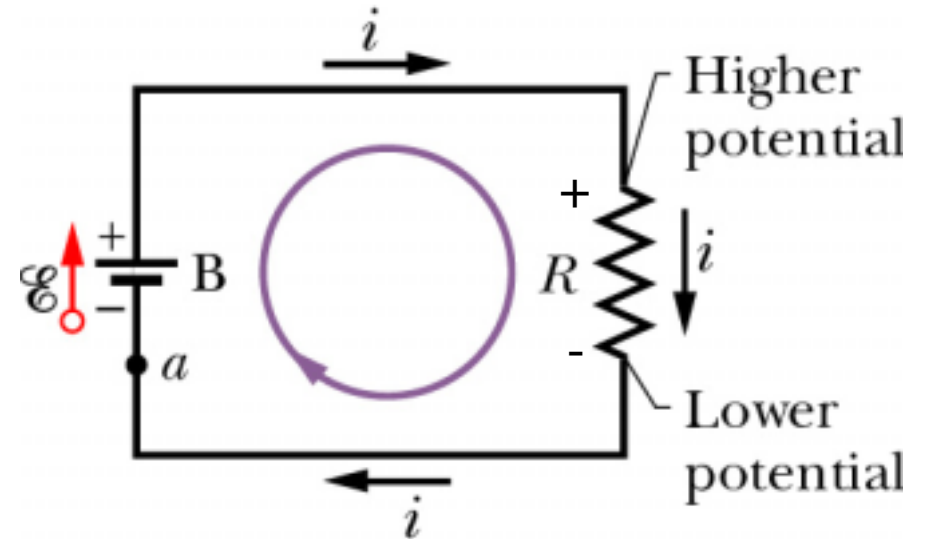- Return to point  $a$  on bottom wire back to potential  $V_a$  so




$$V_a + \mathcal{E} - iR = V_a$$

# Circuits (Fig. 28-3)

- We get back to Ohm's Law

$$E = iR$$

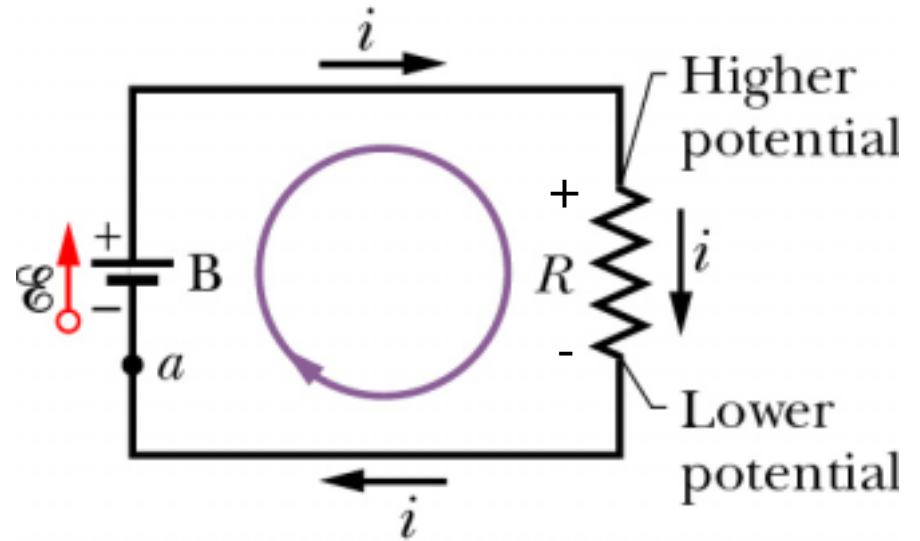

- Could move around circuit counterclockwise

$$V_a - E + iR = V_a$$


$$E = iR$$

# Circuits (Fig. 28-3)

- **Kirchhoff's loop rule** – in traversing a circuit loop the sum of the changes in  $V$  is zero,  $\Delta V = 0$
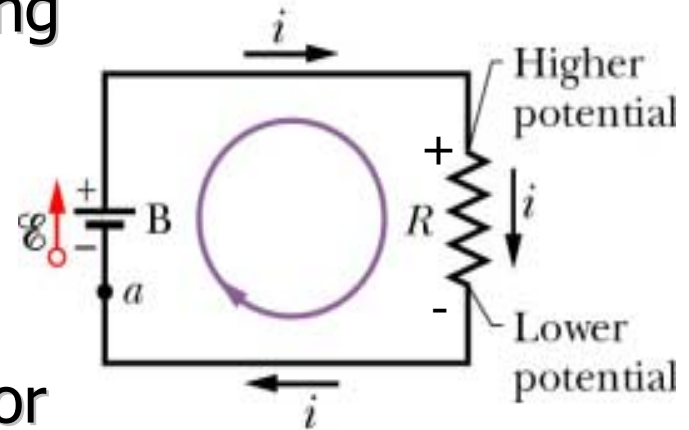
## How do we add the changes in $V$ ?

- **Resistance** – Move through resistor in direction of current  $V = -iR$  (- because it is down the hill), in opposite direction  $V = +iR$  (+ because we move up the hill)
- **Emf** – Move lower (-) to (+) adds potential and  $V = +E$ , in the opposite direction  $V = -E$ .




# Circuits - Checkpoint #1

- A) What direction should the emf arrow point?

RIGHTWARD

- B) Rank magnitude of current at points a, b, and c.


All same

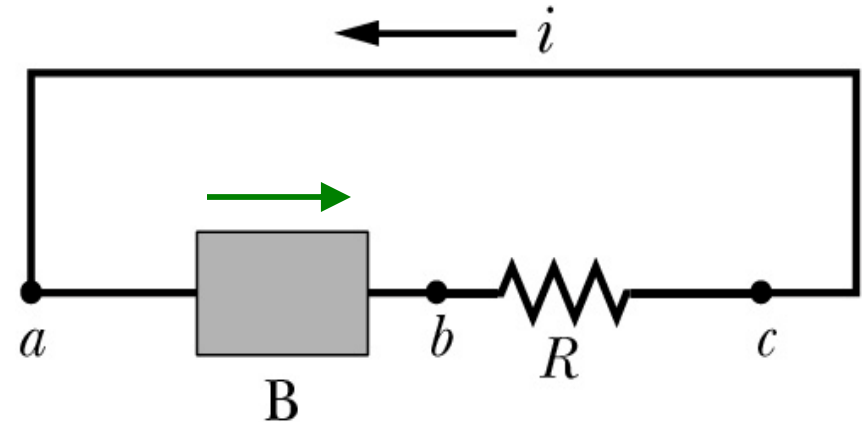

- C) Rank  $V$  and  $U$ .  
b, then a and c tie
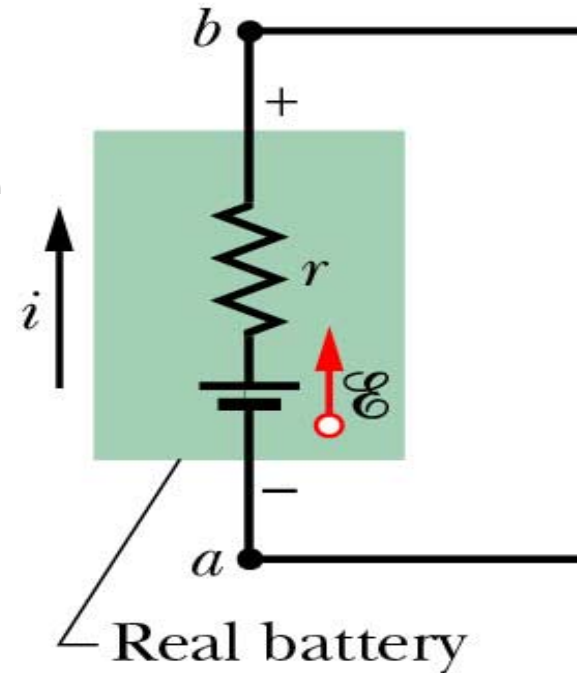
# Circuits (Fig. 28-4)

- So far assumed **ideal battery** – has no internal resistance
- **Real battery** has internal resistance to movement of charge
- Not in circuit  $V = E$  of battery
- If current present  $V = E - iR$ , where  $R$  is the internal resistance of the battery



# Circuits (Fig. 28-4a)


- Put **real** battery in circuit
- Using Kirchhoff's loop rule and starting at point a gives

$$E - ir - iR = 0$$

$$E = i(r + R)$$

- For ideal battery,  $r = 0$  and we get same as before



$$E = iR$$

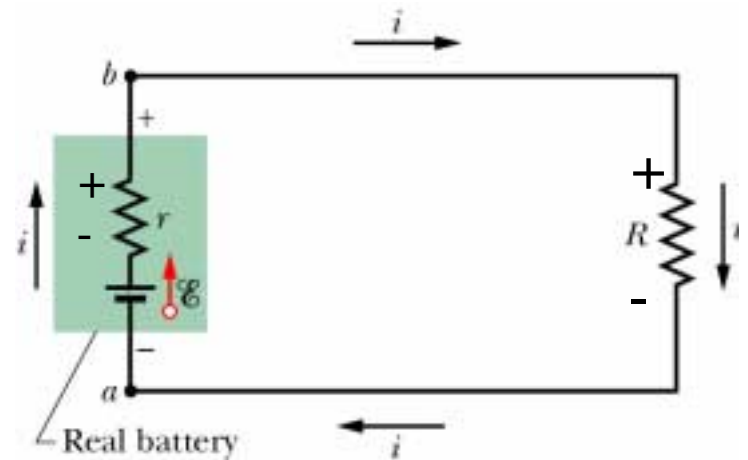

# Circuits (Figs. 28-4a, 28-4b)


- Can represent changes in potential graphically

$$\mathcal{E} - ir - iR = 0$$

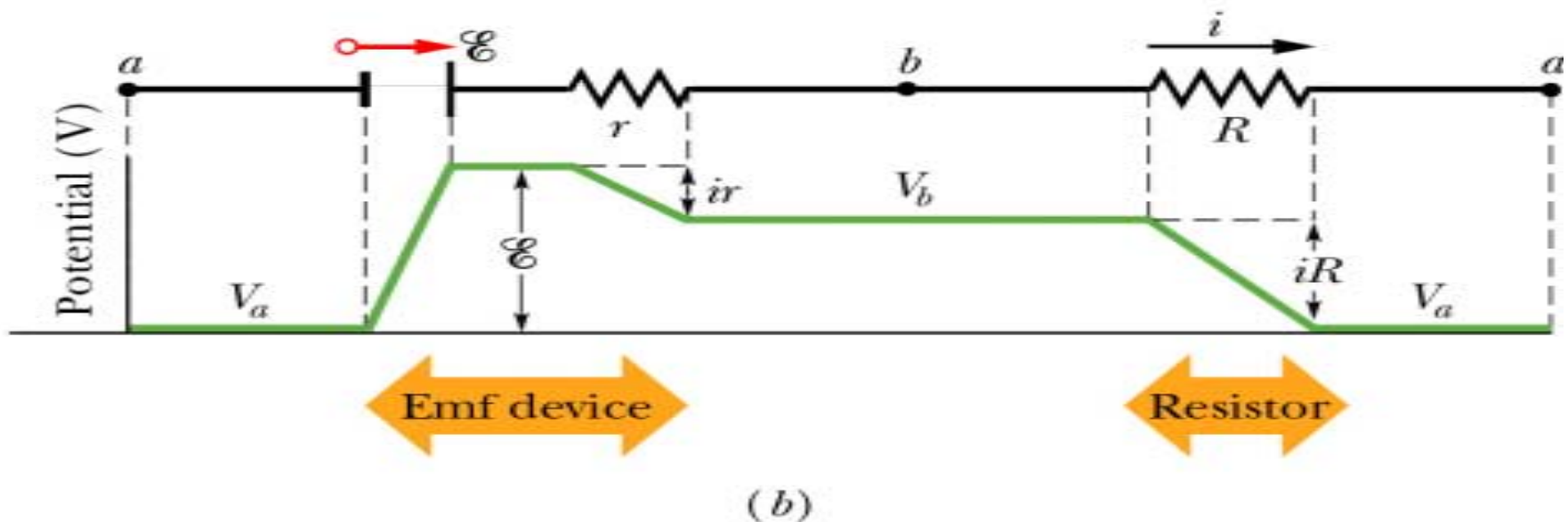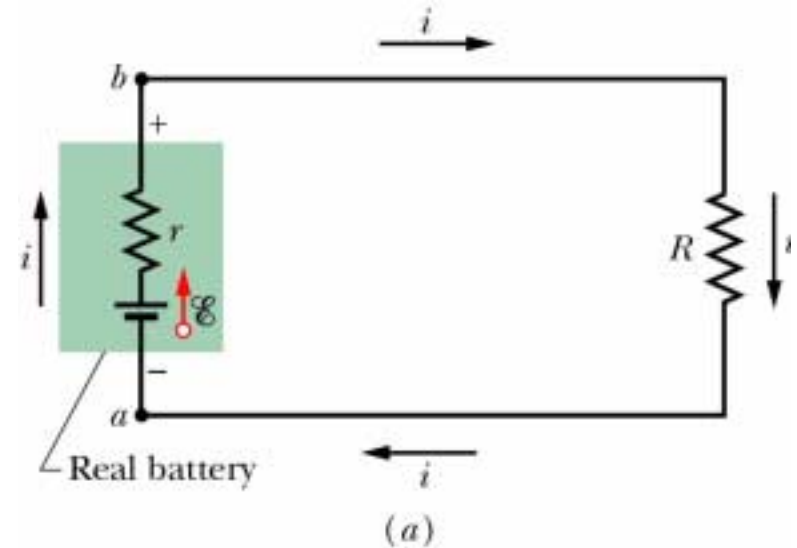
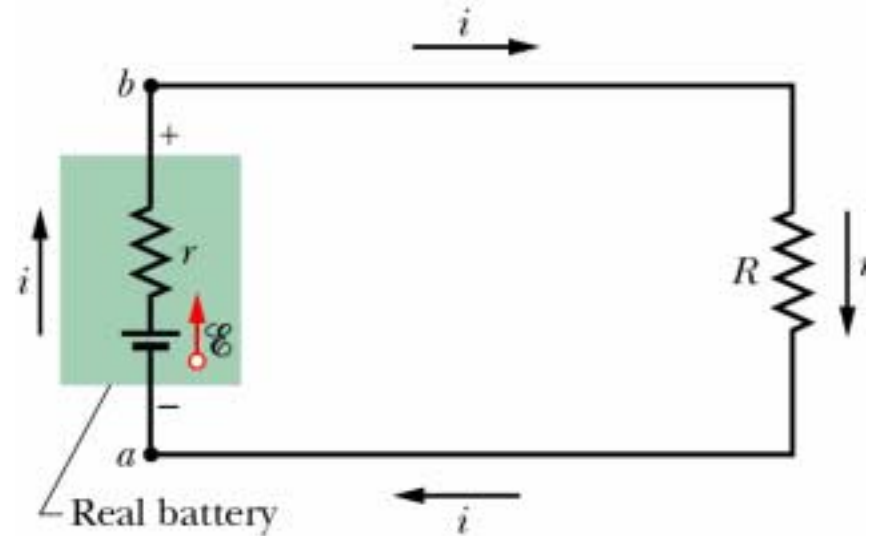
# Circuits (Fig. 28-4a)

- What is the potential difference,  $V$ , between points  $a$  and  $b$ ?
- To find  $V$  between any 2 points in circuit
  - Start at one point and traverse circuit to other following any path
  - Add changes in  $V$  algebraically





# Circuits (Fig. 28-4a)

- Moving from b to a clockwise gives


$$V_b - iR = V_a$$

$$V_b - V_a = iR$$

- From loop rule know

$$\mathcal{E} - ir - iR = 0$$


$$i = \frac{\mathcal{E}}{r + R}$$

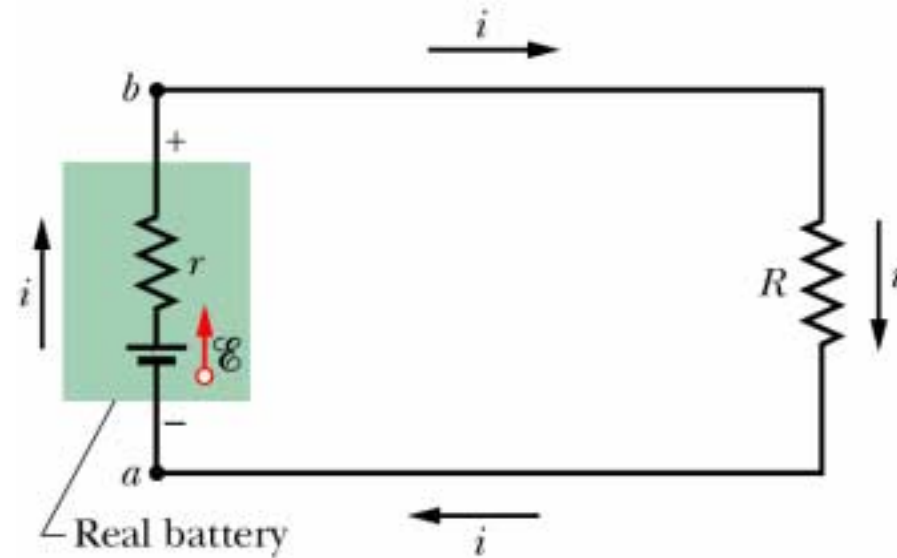

# Circuits (Fig. 28-4a)

$$V_b - V_a = iR$$

$$i = \frac{\mathcal{E}}{r + R}$$

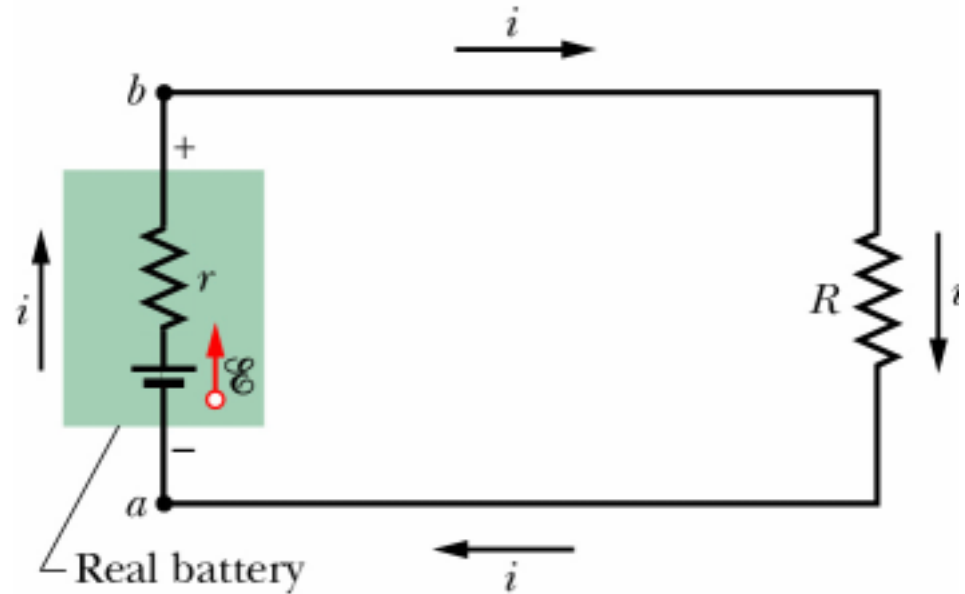

- Substituting for  $i$  gives

$$V_b - V_a = \mathcal{E} \frac{R}{R + r}$$

# Circuits (Fig. 28-4a)

- Now move from  $b$  to  $a$  counterclockwise


$$V_b + ir - \mathcal{E} = V_a$$

$$V_b - V_a = \mathcal{E} - ir$$

- Substituting  $i$  from loop rule


$$i = \frac{\mathcal{E}}{r + R}$$
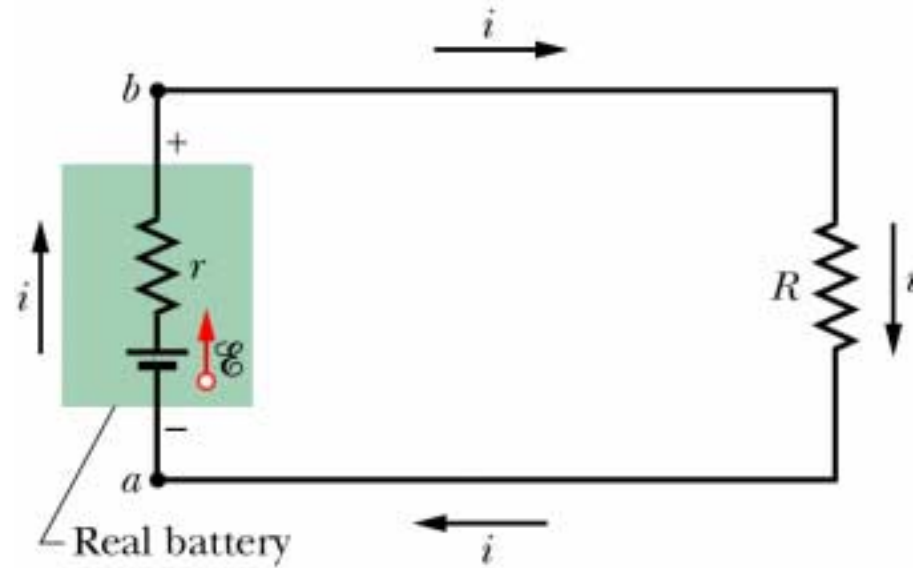
$$V_b - V_a = \mathcal{E} \frac{R}{R + r}$$


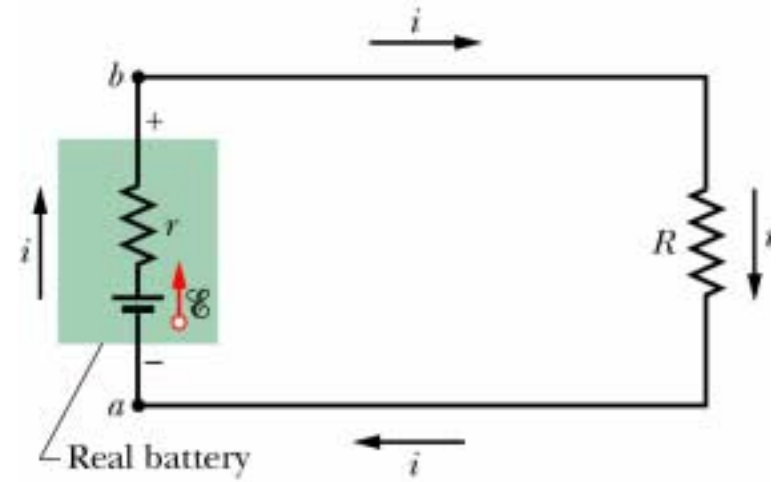
# Circuits (Fig. 28-4a)

- Suppose  $E = 12V$ ,  $R=10\ \Omega$  and  $r=2\ \Omega$
- Potential across battery's terminals is



$$V_b - V_a = E \frac{R}{R + r} = (12V) \frac{10\Omega}{10\Omega + 2\Omega} = 10V$$

- $V$  across terminals only equal to  $E$  if no internal resistance ( $r=0$ ) or no current ( $i=0$ )