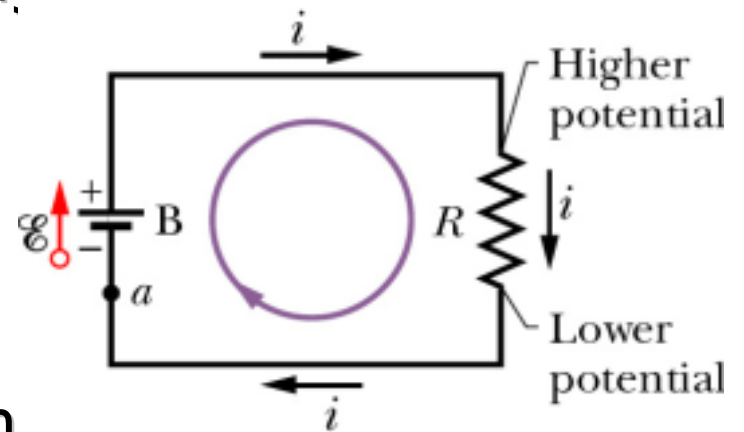


September 30th

Circuits - Chapter 28

Review (Fig. 28-3)

- **Kirchhoff's loop rule** – in traversing a circuit loop the sum of the changes in V is zero, $\Delta V = 0$
- **Resistance rule** – Move through resistor in direction of current $V = -iR$ (+ to -; higher to lower), in opposite direction $V = +iR$ (- to +; up the hill).
- **Emf rule** – Move through emf device $V = +E$ going - to +, in opposite direction $V = -E$.




Circuits (Fig. 28-5a)

- Resistors in series (one path from b to a)
- Have identical currents, i , through them
- Use Kirchhoff's loop rule

$$E - iR_1 - iR_2 - iR_3 = 0$$

$$i = \frac{E}{R_1 + R_2 + R_3}$$

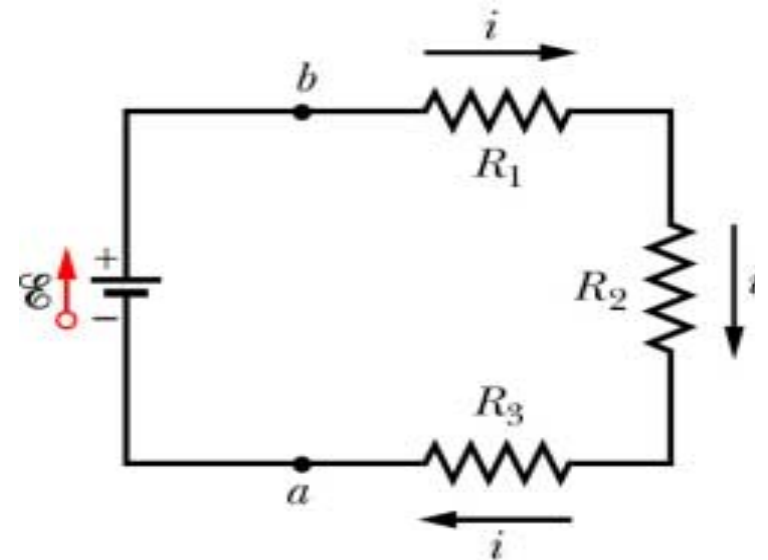


Circuits (Figs. 28-5a, 28-5b)


- Resistors in series
- The 3 resistors act the same as an equivalent resistor R_{eq} .

$$i = \frac{\mathcal{E}}{R_1 + R_2 + R_3} = \frac{\mathcal{E}}{R_{eq}}$$

$$R_{eq} = R_1 + R_2 + R_3$$

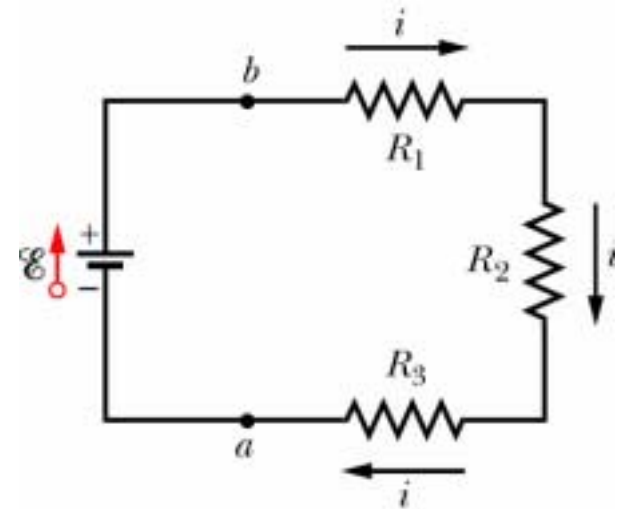

(a)


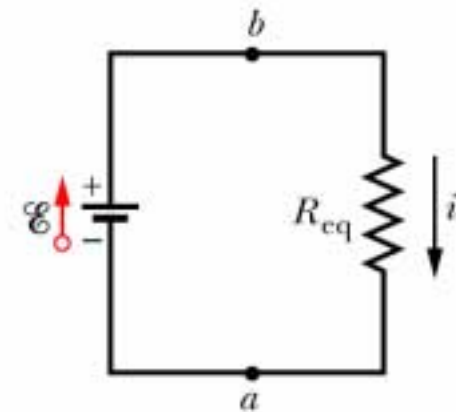


(b)

Circuits (Figs. 28-5a, 28-5b)

- Resistors in series
- Resistors have identical currents, i
- Sum of V 's across resistors = applied V
- R_{eq} is sum of all resistors

$$R_{eq} = \sum_{j=1}^n R_j$$

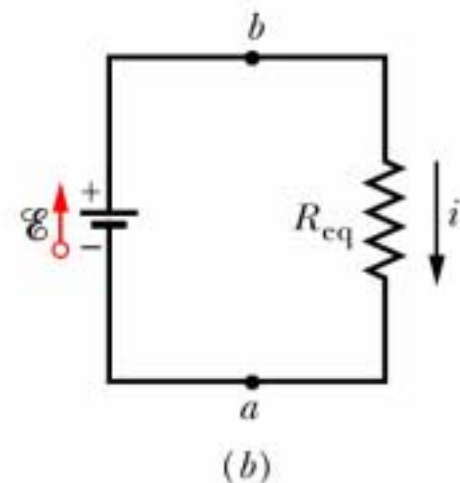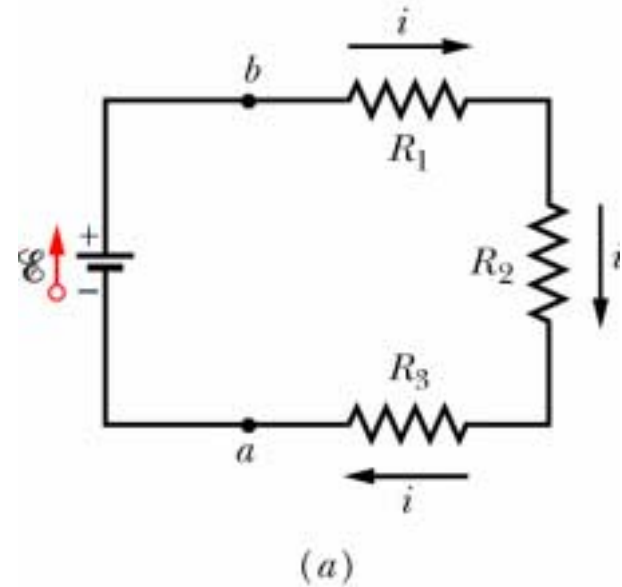


Circuits - Checkpoint #2 (Fig. 28-5a)

- If $R_1 > R_2 > R_3$, rank greatest first
- A) current through resistors

i is same for all, tie


$$V = iR$$

- B) V across them
 R_1, R_2, R_3

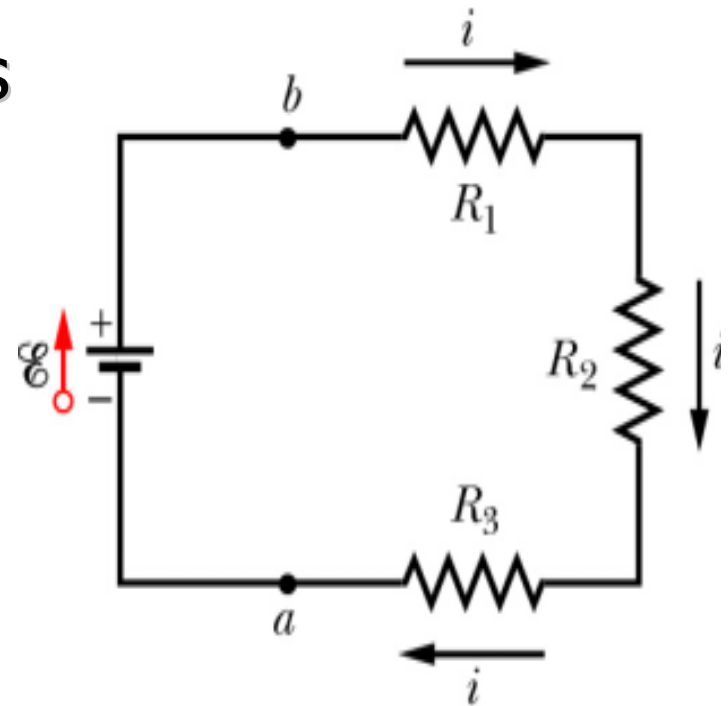

Circuits (Fig. 28-8a)

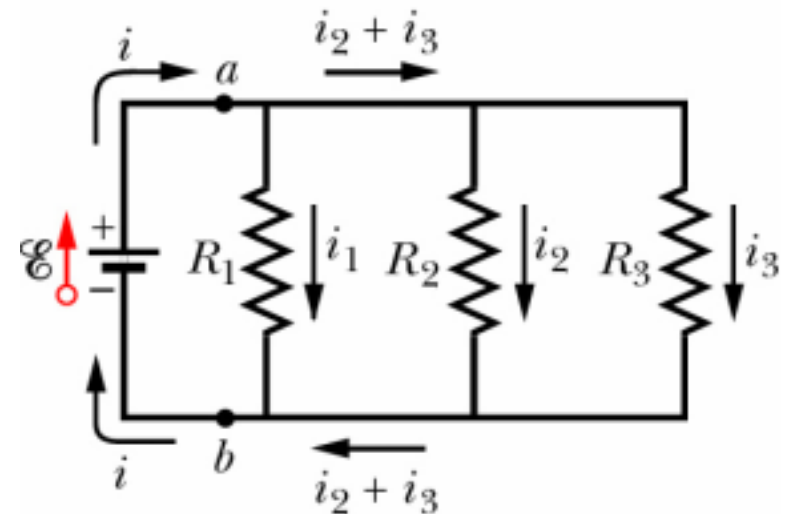- Resistors in parallel
- Have same V across them
- Arbitrarily choose direction for currents in each branch
- Write down current relation for each resistor




$$i_1 = \frac{V}{R_1}$$

$$i_2 = \frac{V}{R_2}$$

$$i_3 = \frac{V}{R_3}$$

Circuits (Fig. 28-8a)

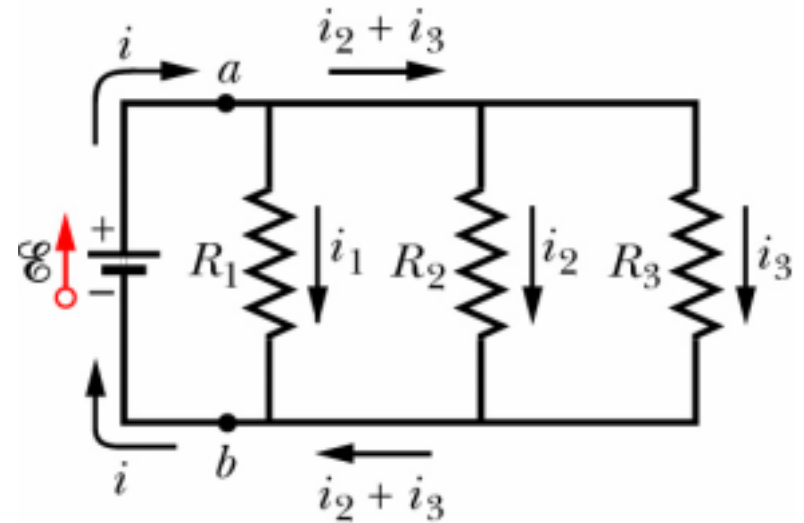- Resistors in parallel (more than one path from a to b)
- Apply Kirchhoff's junction rule at point a
- Substitute current values





$$i = i_1 + i_2 + i_3$$

$$i = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

Circuits (Figs. 28-8a,28-8b)

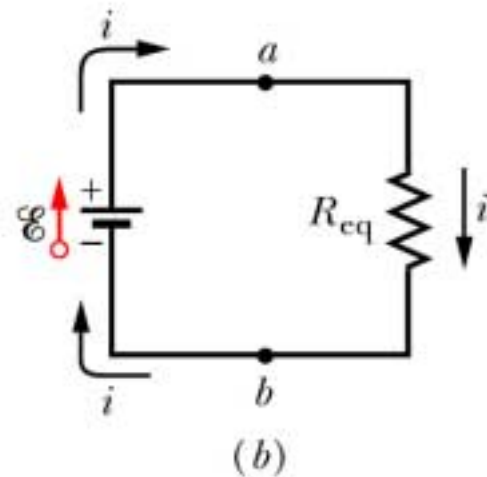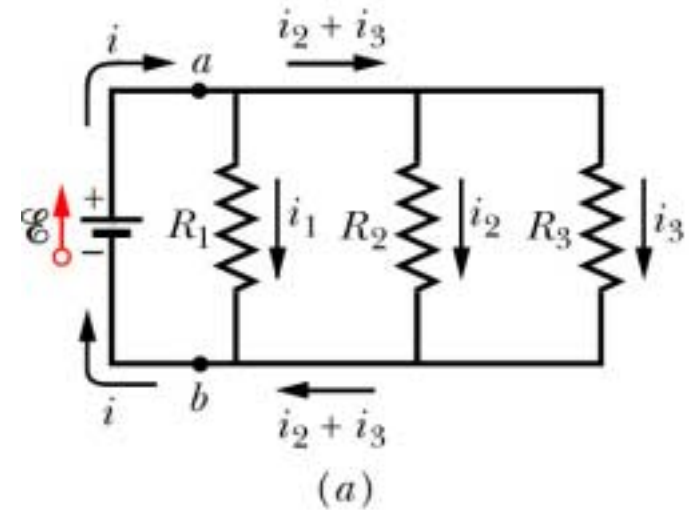- Resistors in parallel
- Replace 3 resistors with equivalent resistor, R_{eq}



$$\frac{1}{R_{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

Circuits - Checkpoint #4

- Battery with potential V supplies current i to 2 identical resistors

- What is V across and i through either of the resistors if they are connected in

- A) Series – What is constant?

i is same, $V_1 = V/2$

- B) Parallel – What is constant?

V is same, $i_1 = i/2$

$$V = iR$$

Circuits

- Resistors
- Series

$$R_{eq} = \sum_{j=1}^n R_j$$

- Parallel

$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$$

- Capacitors
- Series

$$\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j}$$

- Parallel

$$C_{eq} = \sum_{j=1}^n C_j$$

How to Analyze Complex Circuits

- **Kirchhoff's junction rule (or current law) –**
 - From conservation of charge
 - Sum of currents entering a junction is equal to sum of currents leaving that junction
- **Kirchhoff's loop rule (or voltage law) –**
 - From conservation of energy
 - Sum of changes in potential going around a complete circuit loop equals zero

Kirchhoff's Rule #1: Circuits (Fig. 28-8a)

- Arbitrarily label currents, using different subscript for each branch
- Using conservation of charge at each junction


$$i_{in} = i_{out}$$

- At point d

$$i_1 + i_3 = i_2$$

- At point b

$$i_1 + i_3 = i_2$$

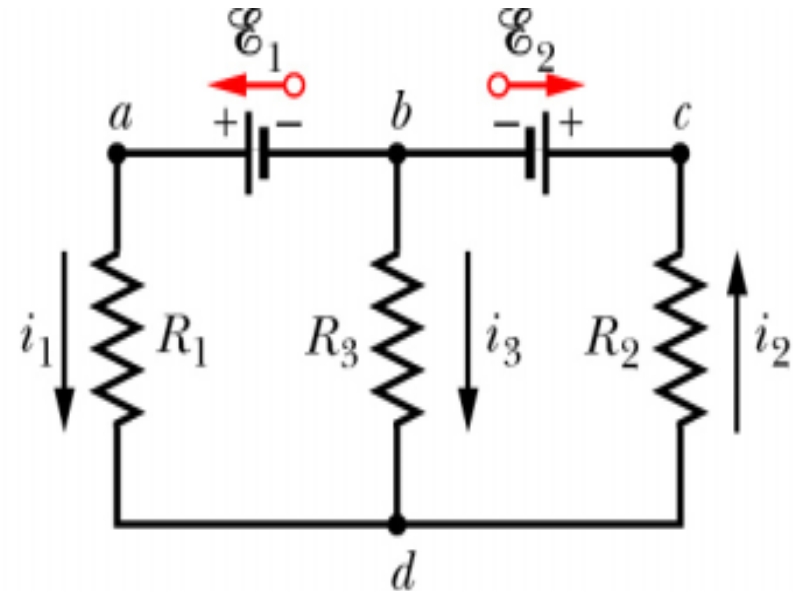

- At point a



$$i_1 = i_1$$

- At point c


$$i_2 = i_2$$

Circuits (Figs. 28-6a, 28-6b)

- What is i of the circuit?

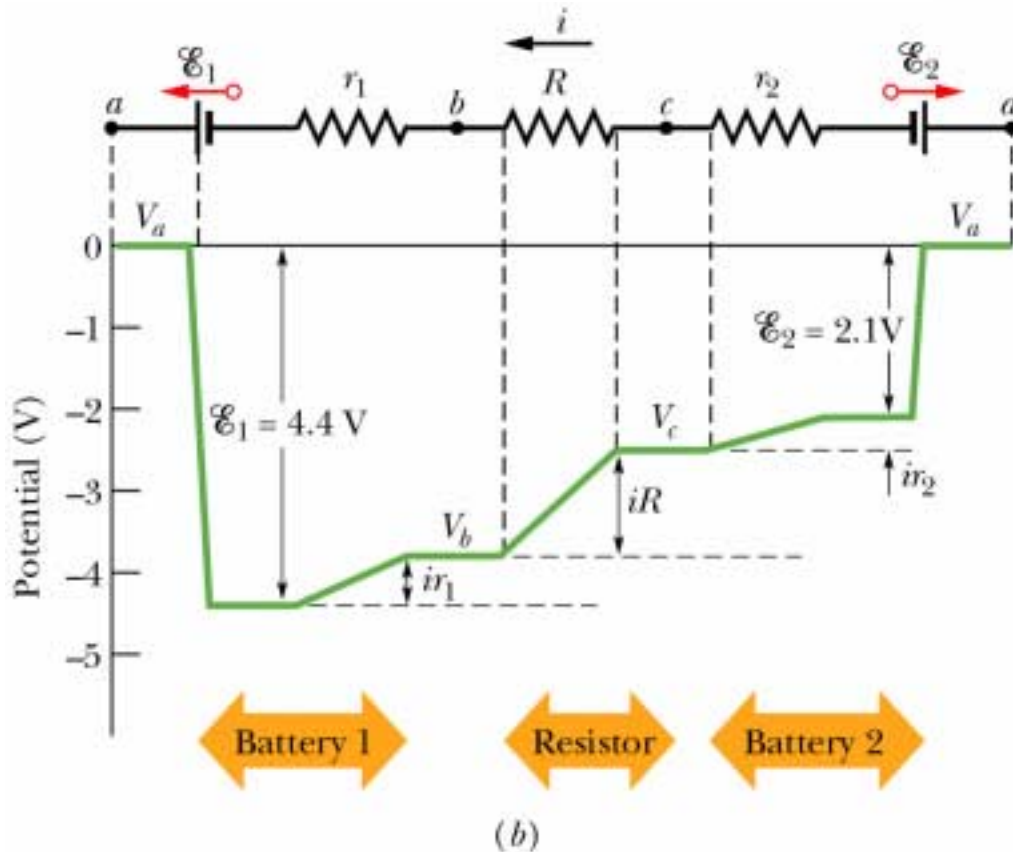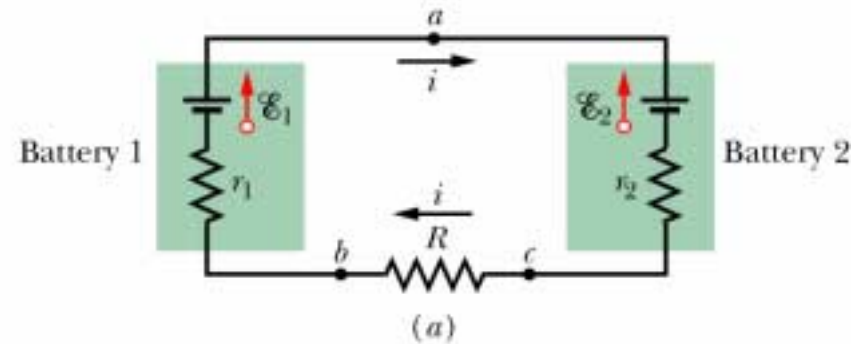

- Use Kirchhoff's loop rule

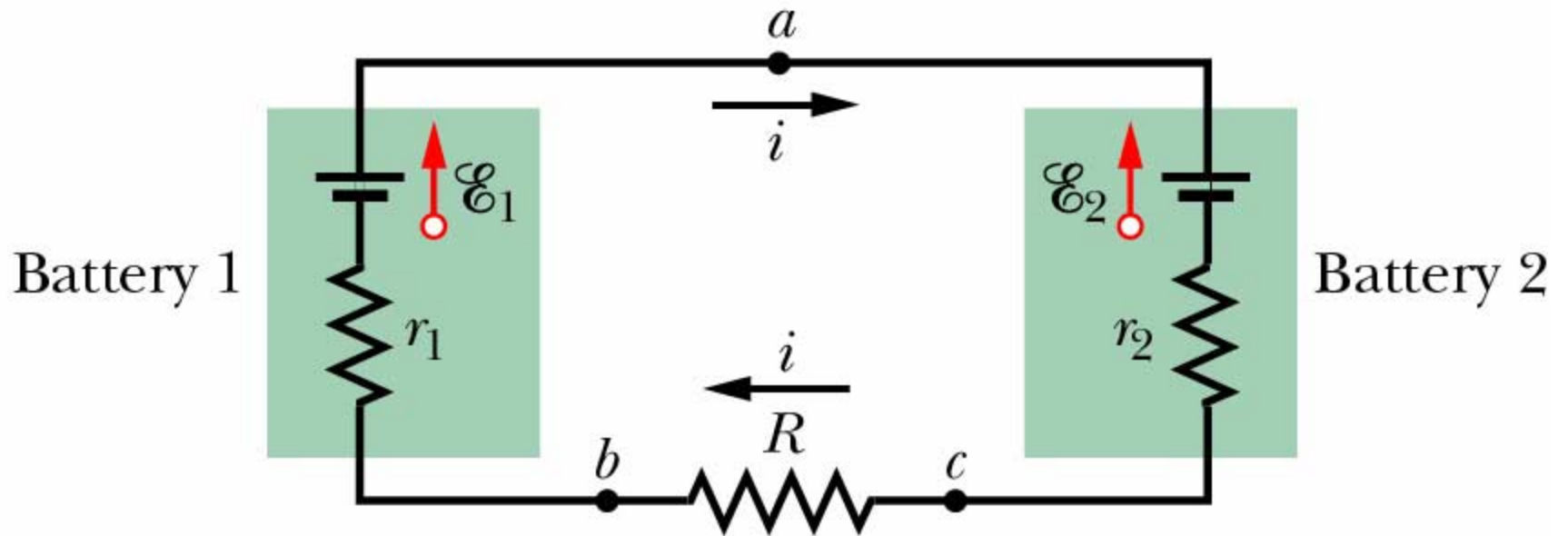

- Clockwise from point a gives

$$-\text{⤵}_2 - ir_2 - iR - ir_1 + \text{⤵}_1 = 0$$

- Counterclockwise from point a gives

$$-\text{⤵}_1 + ir_1 + iR + ir_2 + \text{⤵}_2 = 0$$

Circuits (Fig. 28-6a)

• Solve for i
$$-\mathcal{E}_1 + ir_1 + iR + ir_2 + \mathcal{E}_2 = 0$$

$$i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R + r_1 + r_2}$$

$$\mathcal{E}_1 = 4.4\text{V}$$


$$\mathcal{E}_2 = 2.1\text{V}$$

$$r_1 = 2.3\Omega$$

$$r_2 = 1.8\Omega$$

$$R = 5.5\Omega$$
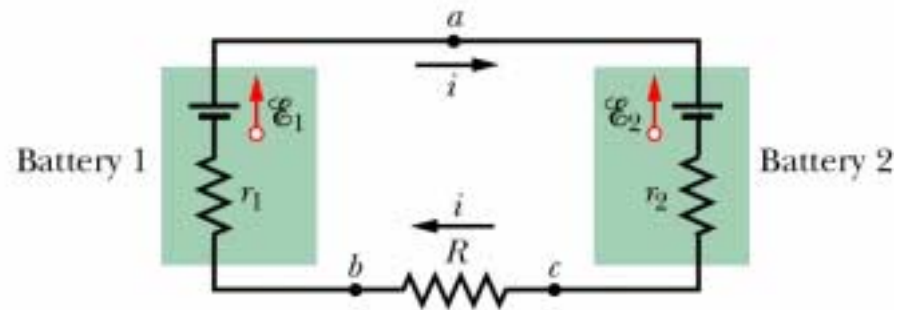
$$i = 0.2396\text{A} \approx 240\text{mA}$$



Checkpoint #3 (Fig. 28-4a)

- A real battery has $E = 12\text{V}$ and $r = 2\Omega$. Is the V across the terminals greater than, less than or equal to 12V if the current in the battery is

- A) from $-$ to $+$ terminal

LESS THAN

$$V_a + E - ir = V_b$$

- B) from $+$ to $-$

GREATER THAN

$$V_a + E + ir = V_b$$

- C) $i = 0$

EQUAL TO 12V

