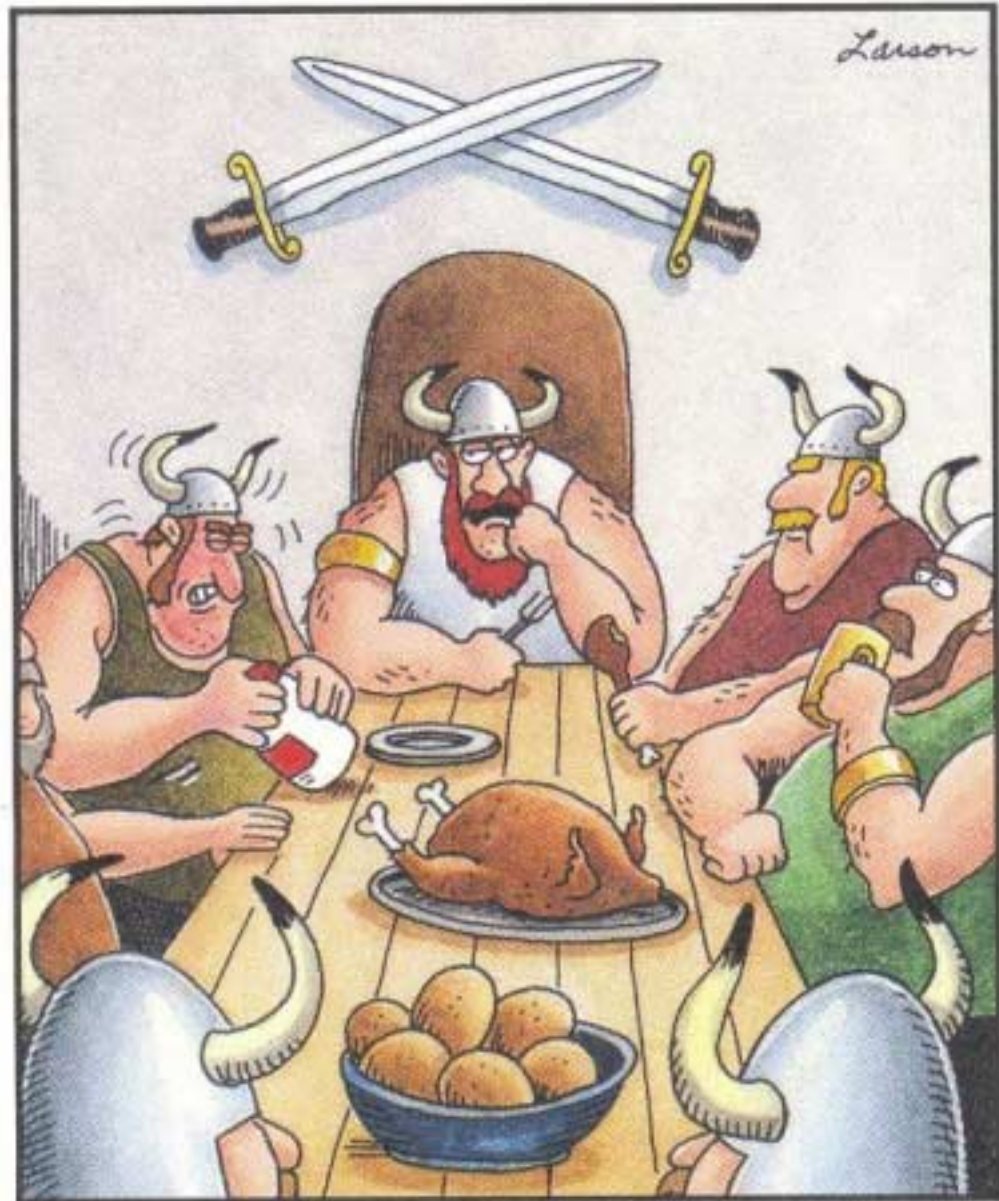


November
3rd


Chapter 33
RLC Circuits



"I can't believe this! ... Can't anyone here get the lid off the mayonnaise?"

LC Circuits

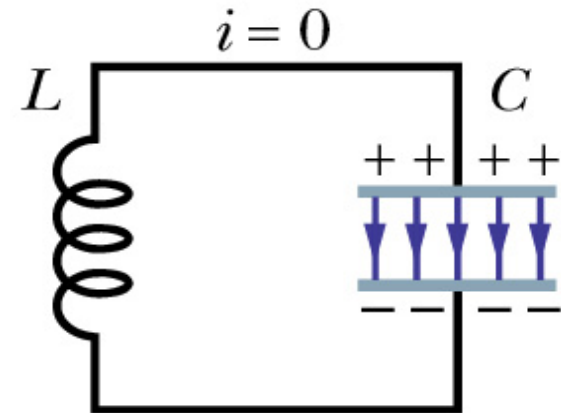- LC Circuit – inductor & capacitor in series



- Find q , i and V vary sinusoidally with period T (angular frequency ω)

$$\omega = \frac{2\pi}{T} = 2\pi f$$

- The energy oscillates between E field stored in the capacitor and the B field stored in the inductor

$$U_E = \frac{1}{2} \frac{q^2}{C}$$

$$U_B = \frac{1}{2} Li^2$$

LC Circuits



- Total energy of LC circuit


$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}$$

- Analogy to block-spring system (PHY183)

$$U = \frac{1}{2}mv^2 + \frac{1}{2}kx^2$$

$$\omega = \sqrt{\frac{k}{m}}$$

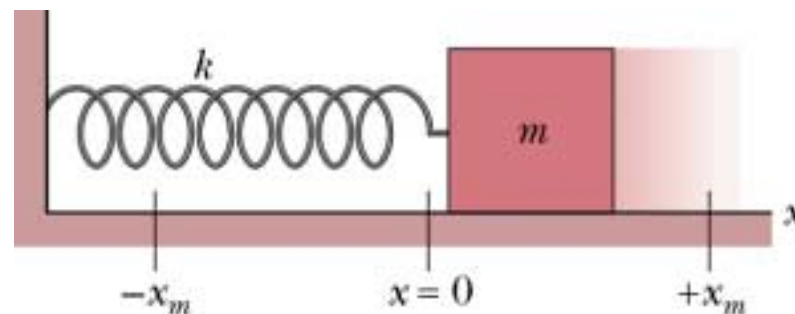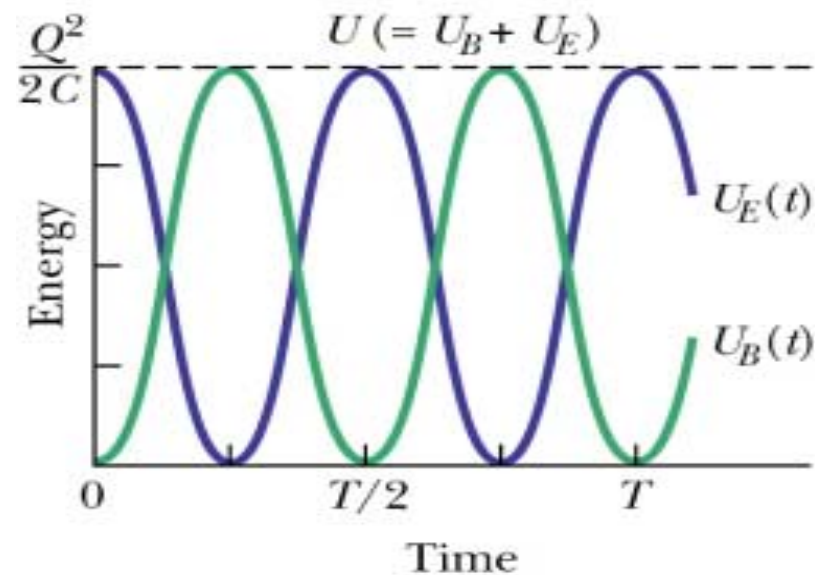

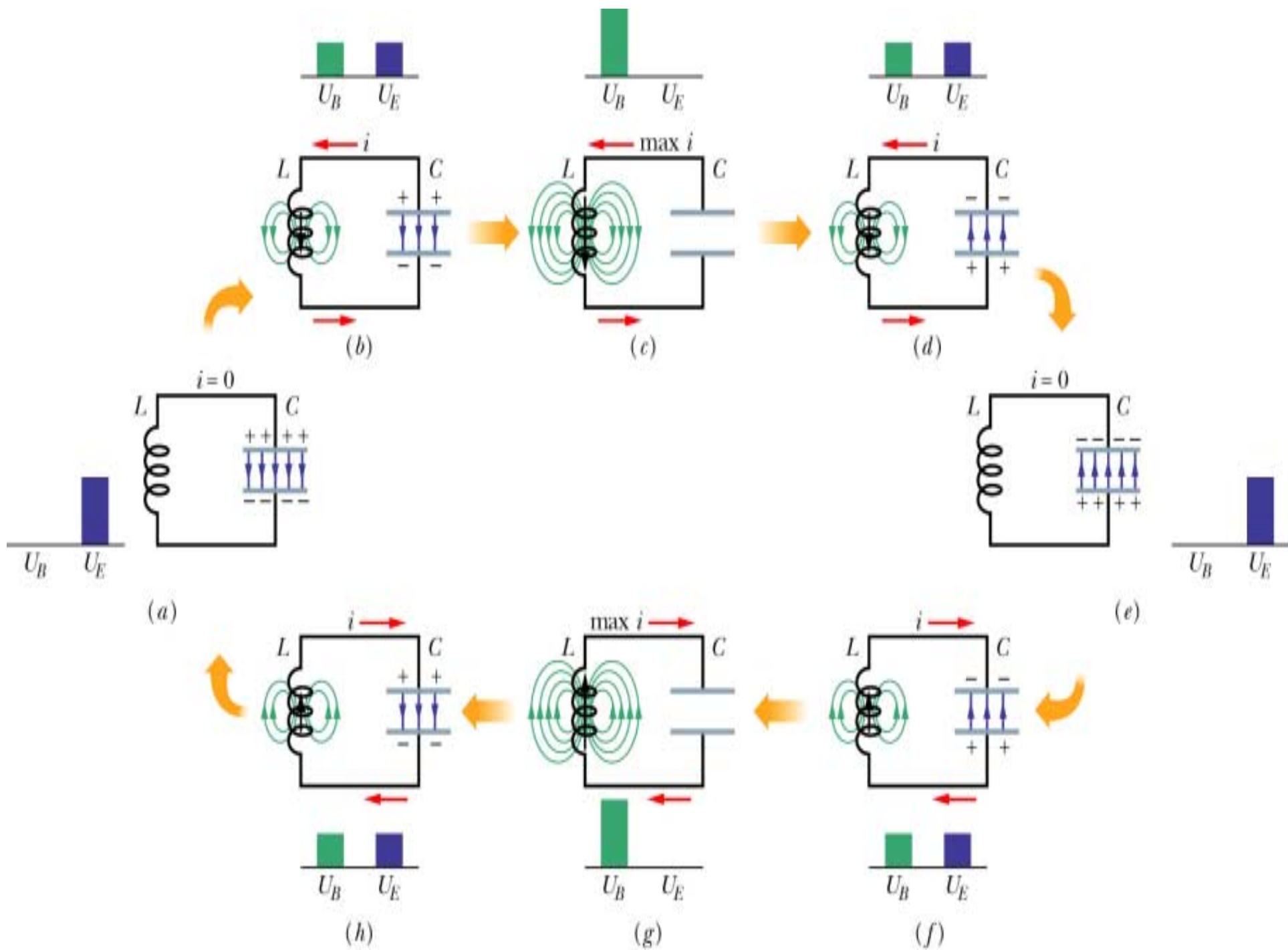

LC Circuits (checkpoint #1)

- A charged capacitor & inductor are connected in series at time $t=0$. In terms of period, T , how much later will the following reach their maximums:

- q of capacitor

$T/2$

- V_C with original polarity



T

- Energy stored in E field

$T/2$

- The current

$T/4$

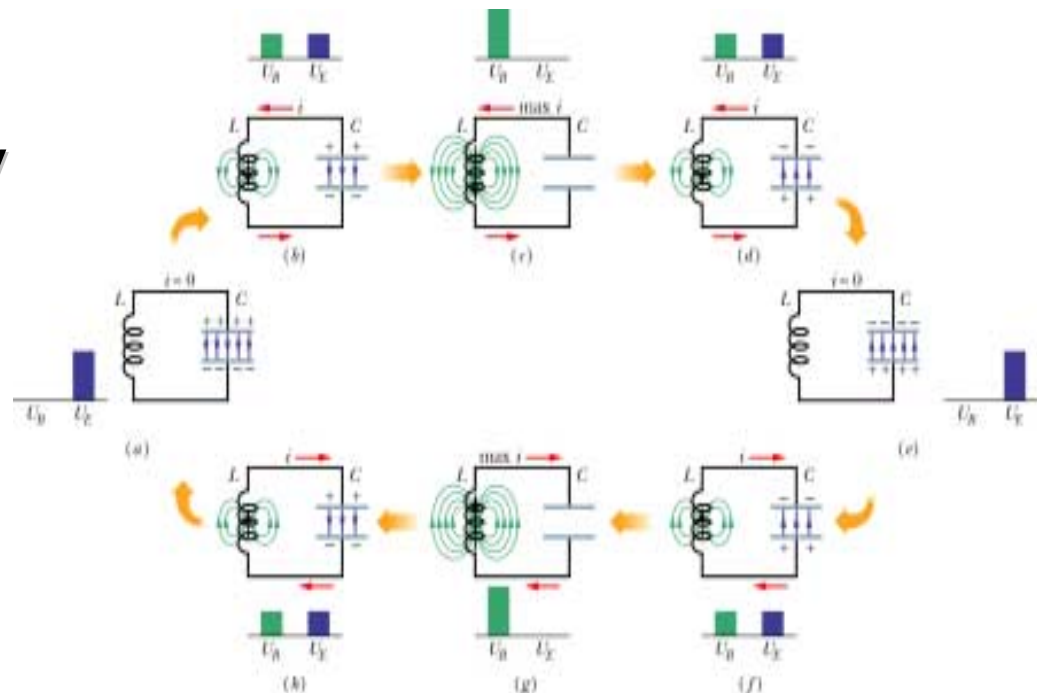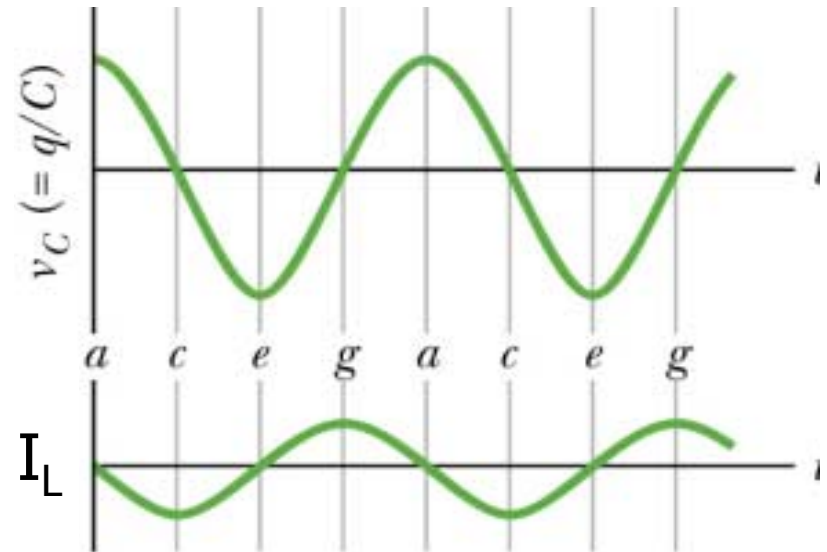

LC Circuits

- The phase constant, ϕ , is determined by the conditions at time $t=0$ (or some other time)


$$q = Q \cos(\omega t + \phi)$$

- If $\phi = 0$ then at $t = 0$, $q = Q$

- Current is $i = -I \sin(\omega t)$

- Where $I = \omega Q$ and


$$\omega = \sqrt{\frac{1}{LC}}$$

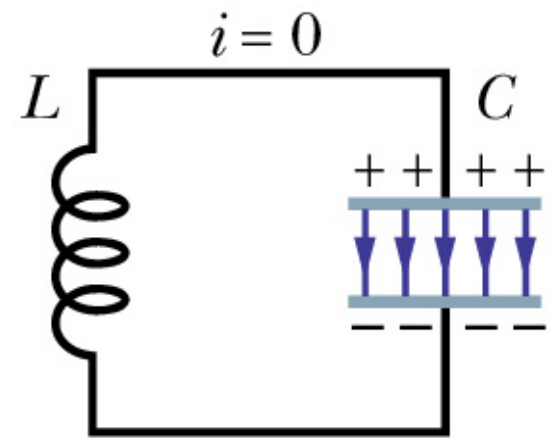

LC Circuits

$$U_E = \frac{Q^2}{2C} \cos^2(\omega t)$$
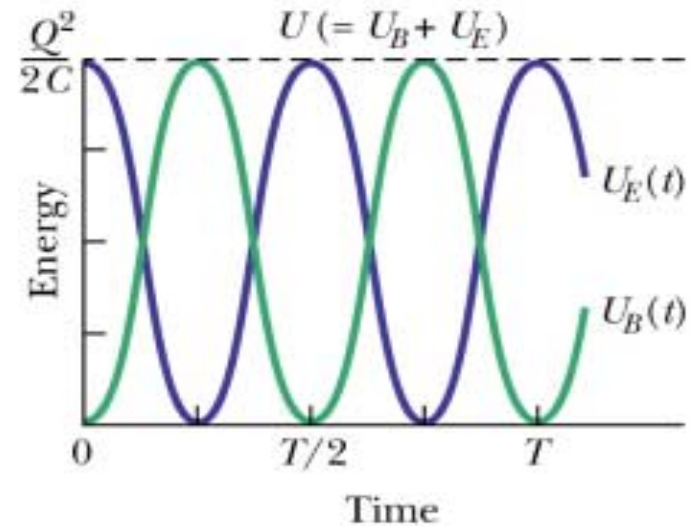
$$U_B = \frac{Q^2}{2C} \sin^2(\omega t)$$




- Maximum value for both

$$U_{E,\max} = U_{B,\max} = Q^2/2C$$

- At any instant, sum is $U = U_B + U_E = Q^2/2C$
- When $U_E = \max$, $U_B = 0$, and conversely, when $U_B = \max$, $U_E = 0$

LC Circuits (checkpoint #2)-quiz

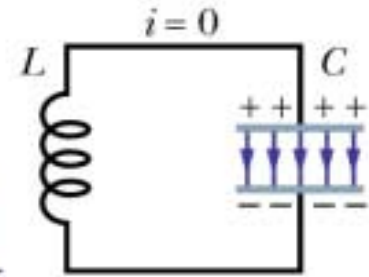- Capacitor in LC circuit has $V_{C,max} = 15\text{ V}$ and $U_{E,max} = 150\text{ J}$. When capacitor has $V_C = 5\text{ V}$ and $U_E = 50\text{ J}$, what are the
 - 1) emf across the inductor?
 - 2) the energy stored in the B field?



- Apply the loop rule
 - Net potential difference around the circuit must be zero

$$v_L(t) = v_C(t)$$



1) 5 V - answer B

2) 100 J - answer C

$$U_{E,max} = U_E(t) + U_B(t)$$

Damped oscillator

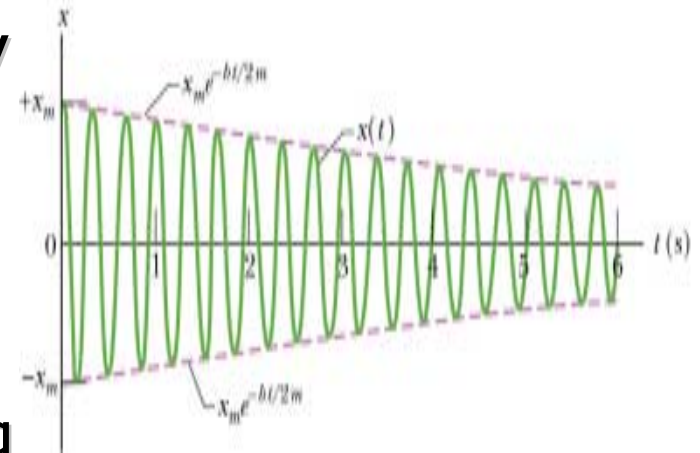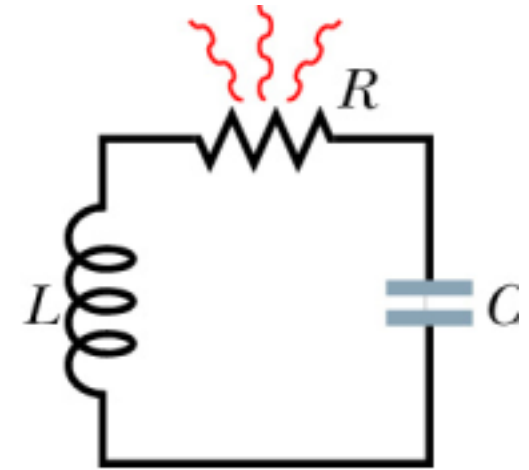- RLC circuit – resistor, inductor and capacitor in series
- Total electromagnetic energy, $U = U_E + U_{B,I}$ is no longer constant
- Energy decreases with time as it is transferred to thermal energy in the resistor
- Oscillations in q , i and V are **damped**
 - Same as damped block and spring



RLC Circuits

- Resistor does not store electromagnetic energy so total energy at any time is


$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}$$

- Rate of transfer to thermal energy is (minus sign means U is decreasing)

$$\frac{dU}{dt} = -i^2 R$$

- Differentiating gives
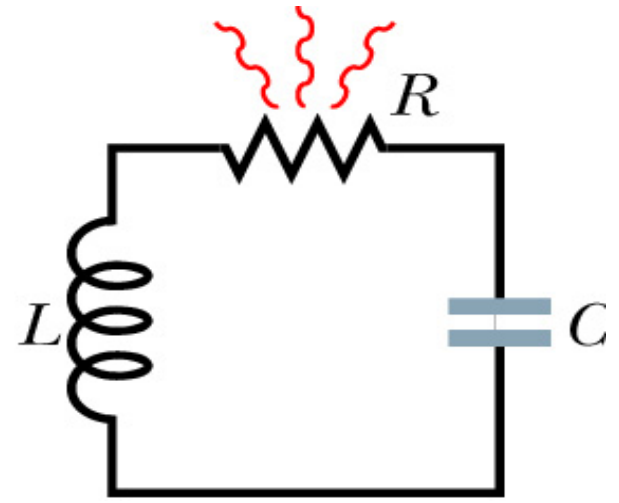
$$\frac{dU}{dt} = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = -i^2 R$$



RLC Circuits

$$\frac{dU}{dt} = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = -i^2 R$$

- Use relations $i = \frac{dq}{dt}$ $\frac{di}{dt} = \frac{d^2 q}{dt^2}$

- Differential equation for damped RLC circuit is

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0$$

- Solution

$$q = Q e^{-Rt/2L} \cos(\omega' t)$$

RLC Circuits

$$q = Qe^{-Rt/2L} \cos(\omega' t)$$

- Where $\omega' = \sqrt{\omega^2 - (R/2L)^2}$ $\omega = \sqrt{\frac{1}{LC}}$
- Charge in RLC circuit is sinusoidal but with an exponentially decaying amplitude $Qe^{-Rt/2L}$
- Damped angular frequency, ω' , is always less than ω of the undamped oscillations
- If R is small enough can replace ω' with ω

RLC Circuits

$$q = Q e^{-Rt/2L} \cos(\omega' t)$$

- Find U_E as function of time


$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} e^{-Rt/L} \cos^2(\omega' t)$$

- Total energy decreases as

$$U_{tot} = \frac{Q^2}{2C} e^{-Rt/L}$$


AC generator

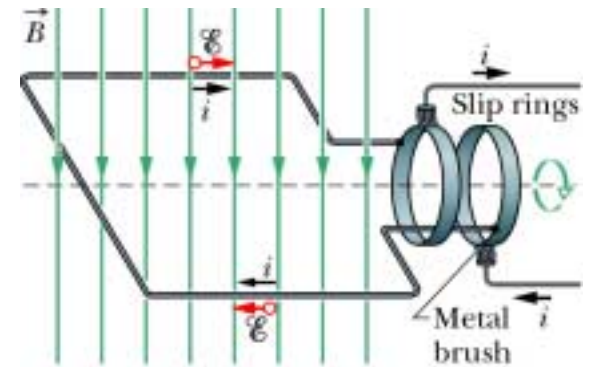- Mechanically turn loop in B field, induces a current and therefore an emf
- Driving angular frequency ω_d is equal to angular speed that loop rotates in B field.
- Used Faraday's law to find emf



$$\mathcal{E} = -N \frac{d\Phi_B}{dt} = NBA \omega_d \sin \omega_d t$$
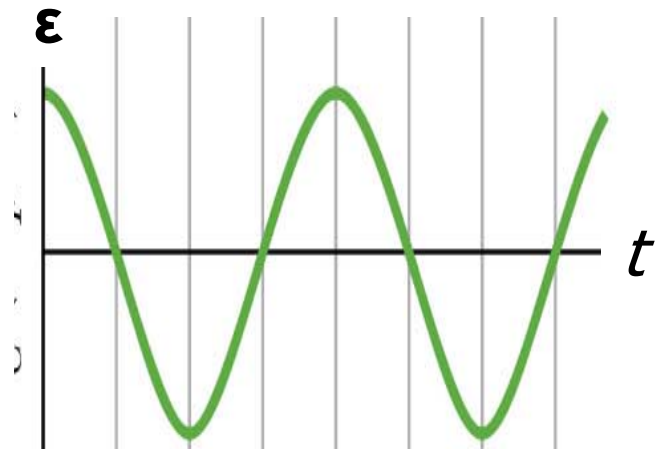
$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t \quad \mathcal{E}_m = NBA \omega_d$$




Forced Oscillations

Driving frequency ω_d will overpower the natural frequency ω

Resistive load

$$v_R = V_R \sin \omega_d t$$


$$V_R = \mathcal{E}_m$$

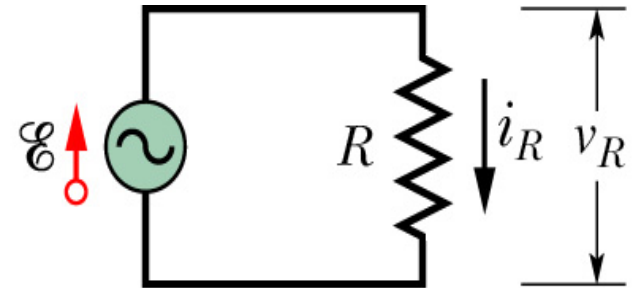

Capacitive load

$$v_C = V_C \sin \omega_d t$$


$$V_C = \mathcal{E}_m$$

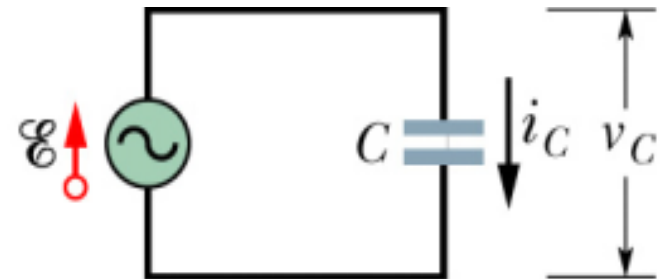

Inductive load

$$v_L = V_L \sin \omega_d t$$

$$V_L = \mathcal{E}_m$$

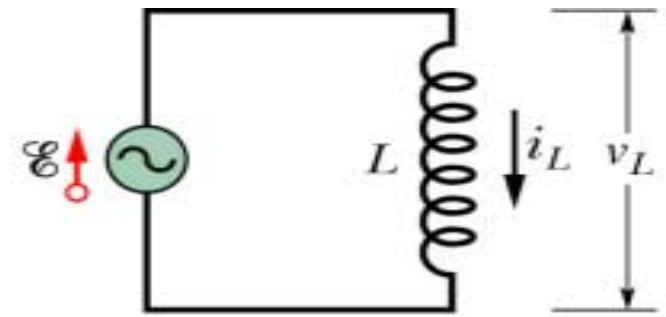



Forced oscillations - Resistive load

- Use definition of resistance to find i_R

$$v_R = V_R \sin \omega_d t$$

$$i_R = \frac{v_R}{R} = \frac{V_R}{R} \sin \omega_d t$$

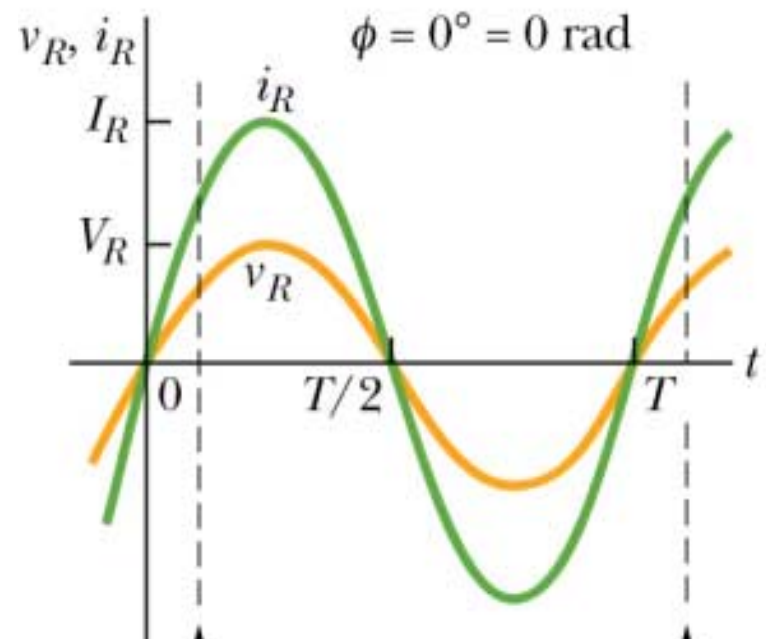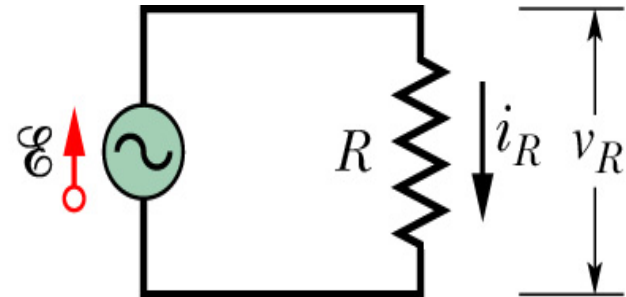- **Voltage and current** are functions of $\sin(\omega_d t)$ with $\phi = 0$ so are **in phase**
- No damping of v_R and i_R , since the generator supplies energy




Forced oscillations - Resistive load

- Compare current to general form

$$i_R = \frac{v_R}{R} = \frac{V_R}{R} \sin \omega_d t$$

$$i_R = I_R \sin(\omega_d t - \phi)$$

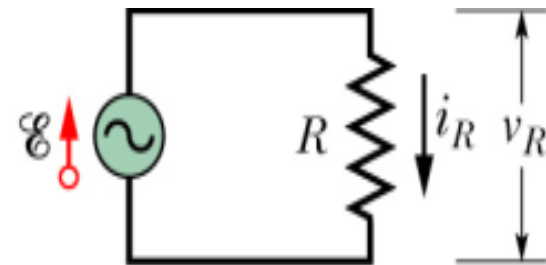- Minus sign for phase is tradition
- For purely resistive load the phase constant $\phi = 0$
- Voltage amplitude is related to current amplitude




$$I_R = \frac{V_R}{R}$$

$$V_R = I_R R$$

Forced oscillations - Capacitive load

- Use definition of capacitance

$$q_C = Cv_C = CV_C \sin \omega_d t$$

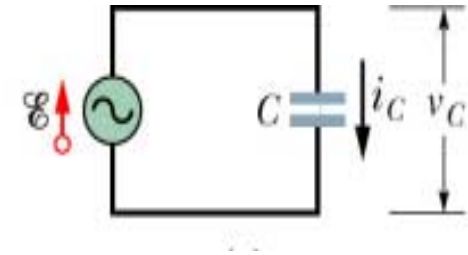

- Use definition of current and differentiate

$$i_C = \frac{dq_C}{dt} = \omega_d CV_C \cos \omega_d t$$


- Replace cosine term with a phase-shifted sine term

$$\cos \omega_d t = \sin(\omega_d t + 90^\circ)$$

Capacitive load

- Voltage and current relations

$$v_C = V_C \sin \omega_d t$$

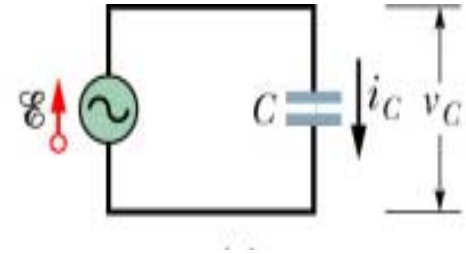

$$i_C = \omega_d C V_C \sin(\omega_d t + 90^\circ) = I_C \sin(\omega_d t + 90^\circ)$$

$$I_C = \frac{V_C}{X_C}$$

$$X_C = \frac{1}{\omega_d C}$$


- X_C is called the **capacitive reactance** has units of ohms

Forced oscillations - Capacitive load


- Compare v_C and i_C of capacitor

$$v_C = V_C \sin \omega_d t$$
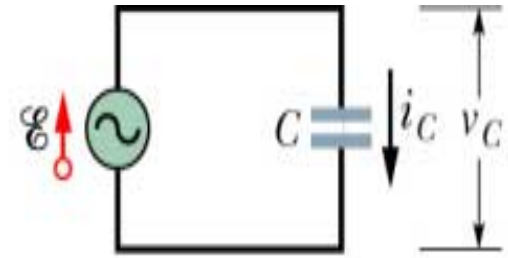
$$i_C = \omega_d C V_C \sin(\omega_d t + 90^\circ)$$



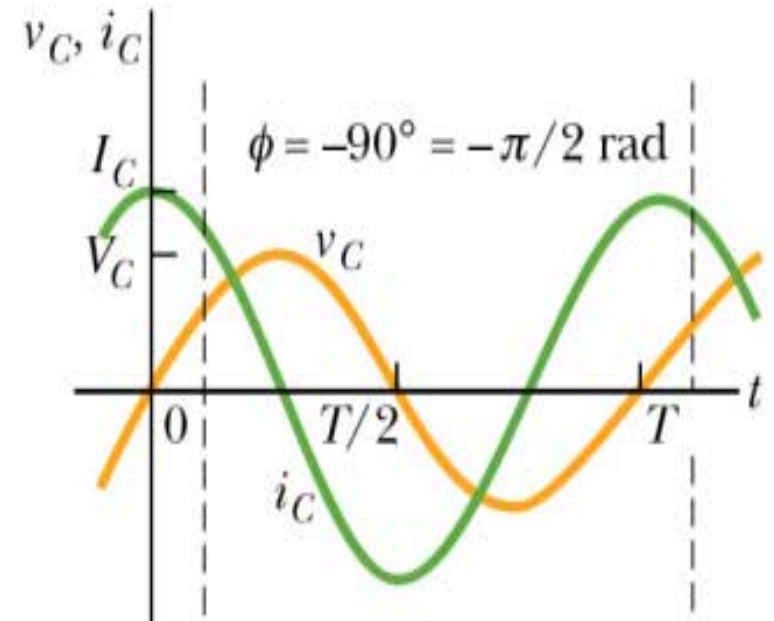
- Voltage and current are out of phase by 90°
- Current leads voltage by $T/4$



Forced Oscillations - Inductive load

- Voltage and current relations

$$v_L = V_L \sin \omega_d t$$

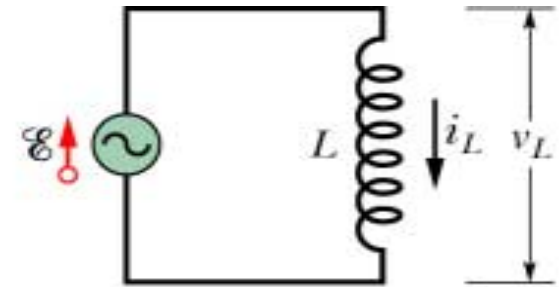

$$i_L = \frac{V_L}{\omega_d L} \sin(\omega_d t - 90^\circ) = I_L \sin(\omega_d t - 90^\circ)$$

$$I_L = \frac{V_L}{X_L}$$

$$X_L = \omega_d L$$


- X_L is called the **inductive reactance** has units of ohms

Forced Oscillations - Inductive load


- Compare v_L and i_L of inductor

$$v_L = V_L \sin \omega_d t$$
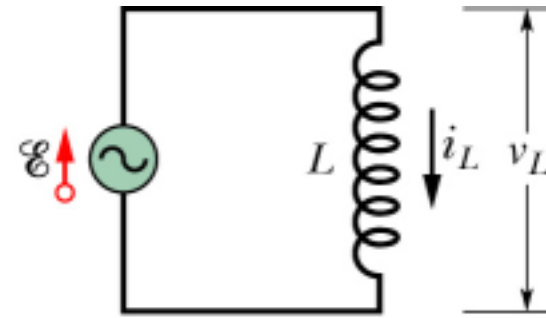
$$i_L = I_L \sin(\omega_d t - 90^\circ)$$



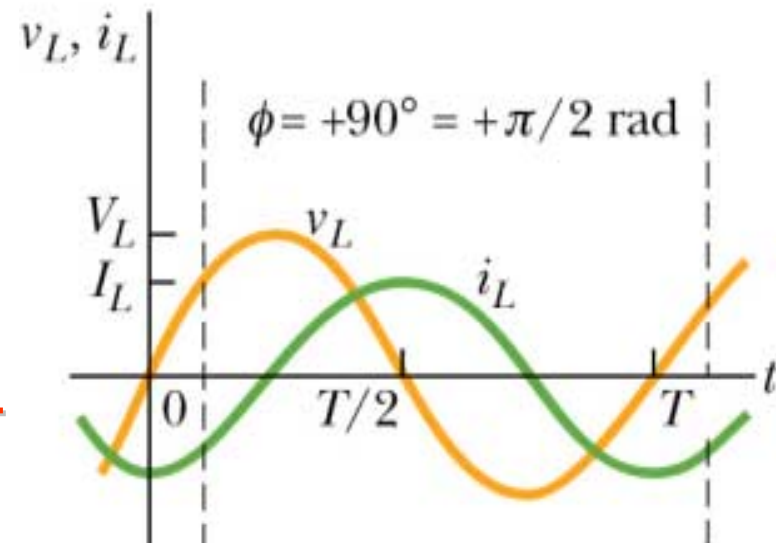- Compare i_L to v_L
- i_L and v_L are 90° out of phase
- Current lags voltage by $T/4$



Summary of Forced Oscillations

Element	Reactance/ Resistance	Phase of Current	Phase angle ϕ	Amplitude Relation
Resistor	R	In phase	0°	$V_R = I_R R$
Capacitor	$X_C = 1/\omega_d C$	Leads v_C (ICE)	-90°	$V_C = I_C X_C$
Inductor	$X_L = \omega_d L$	Lags v_L (ELI)	$+90^\circ$	$V_L = I_L X_L$

- **ELI (positively) is the ICE man**
 - Voltage or emf (E) before current (I) in an inductor (L)
 - Phase constant ϕ is positive for an inductor
 - Current (I) before voltage or emf (E) in capacitor (C)