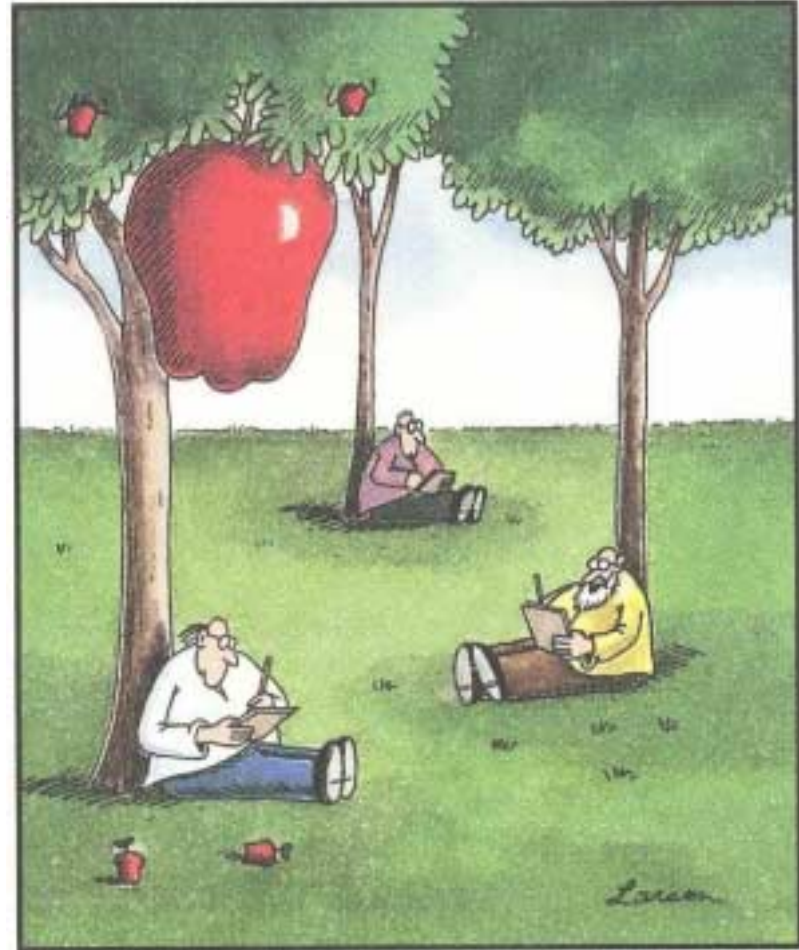


November
4th

Chapter 33
RLC Circuits





"Nothing yet. ... How about you, Newton?"

Review

- RL and RC circuits
 - Charge, current, and potential grow and decay exponentially
- LC circuit
 - Charge, current, and potential change sinusoidally
 - Total electromagnetic energy is
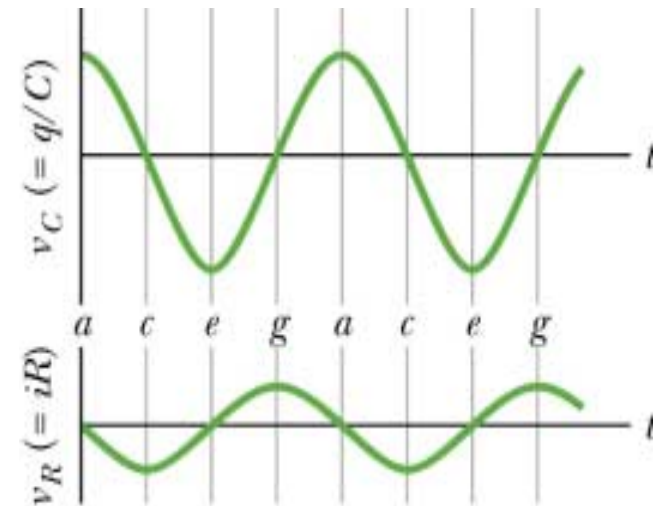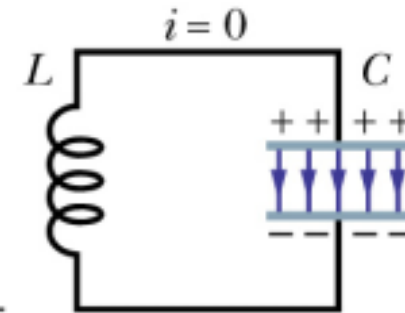
$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}$$



Review

- Ideal LC circuit

$$\frac{dU}{dt} = 0$$

- Total energy conserved
- Solved differential equation to find

$$q = Q \cos(\omega t)$$

$$i = -I \sin(\omega t)$$

$$\omega = \sqrt{\frac{1}{LC}}$$


- Substituting q and i into energy equations

$$U_E = \frac{Q^2}{2C} \cos^2(\omega t)$$

$$U_B = \frac{Q^2}{2C} \sin^2(\omega t)$$

$$U = U_B + U_E = Q^2 / 2C$$

Review

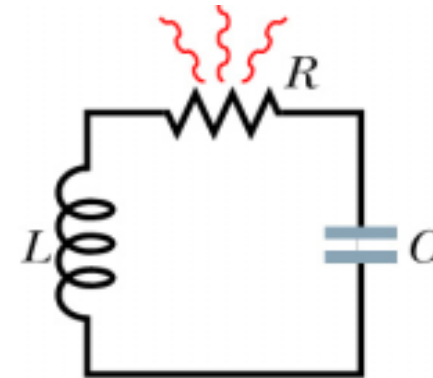

- RLC circuit
 - Energy is no longer conserved, becomes thermal energy in resistor
 - Oscillations are damped
 - Solved differential equation to find

$$\frac{dU}{dt} = -i^2 R$$

$$q = Qe^{-Rt/2L} \cos(\omega't)$$

$$\omega' = \sqrt{\omega^2 - (R/2L)^2}$$

If R is very small

$$\omega' = \omega$$

- Energy goes as

$$U_E = \frac{Q^2}{2C} e^{-Rt/L} \cos^2(\omega't)$$

$$U_{tot} = \frac{Q^2}{2C} e^{-Rt/L}$$

Resistive Load

- Apply loop rule

$$\mathcal{E} - v_R = 0$$

$$v_R = \mathcal{E}$$

- Using

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t$$

- We have


$$v_R = \mathcal{E}_m \sin \omega_d t$$

- Amplitude across resistor is same as across emf

$$\mathcal{E}_m = V_R$$

- Rewrite v_R as

$$v_R = V_R \sin \omega_d t$$

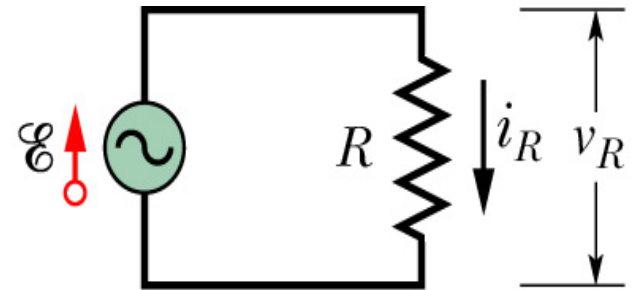


Forced Oscillations

Resistive load

$$v_R = V_R \sin \omega_d t$$


$$V_R = \mathcal{E}_m$$

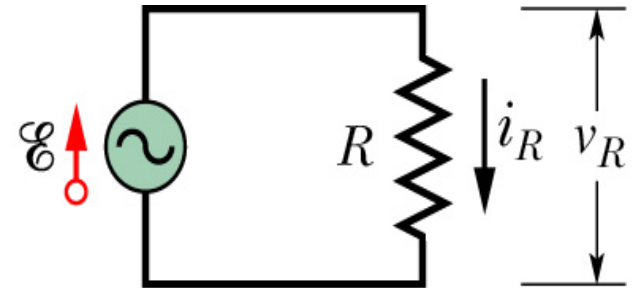

Capacitive load

$$v_C = V_C \sin \omega_d t$$


$$V_C = \mathcal{E}_m$$

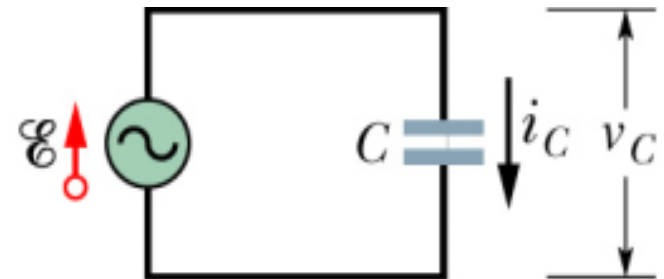

Inductive load

$$v_L = V_L \sin \omega_d t$$

$$V_L = \mathcal{E}_m$$

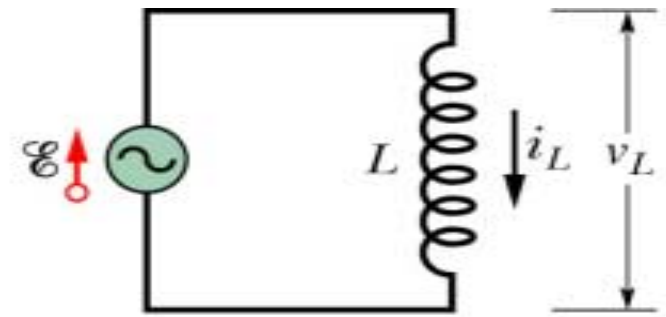



Resistive load

- Use definition of resistance to find i_R

$$v_R = V_R \sin \omega_d t$$

$$i_R = \frac{v_R}{R} = \frac{V_R}{R} \sin \omega_d t$$

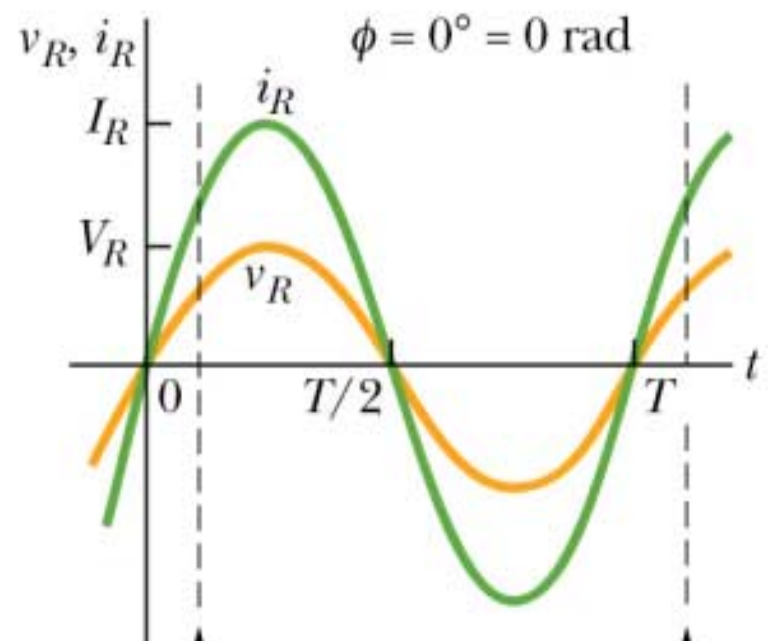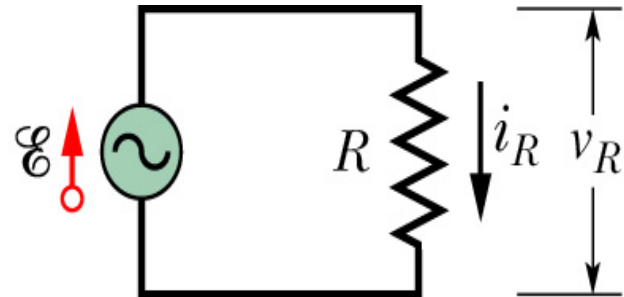- **Voltage and current** are functions of $\sin(\omega_d t)$ with $\phi = 0$ so are **in phase**
- No damping of v_R and i_R , since the generator supplies energy



Resistive load

- Compare current to general form

$$i_R = \frac{v_R}{R} = \frac{V_R}{R} \sin \omega_d t$$

$$i_R = I_R \sin(\omega_d t - \phi)$$

- Minus sign for phase is tradition
- For purely resistive load the phase constant $\phi = 0$
- Voltage amplitude is related to current amplitude



$$I_R = \frac{V_R}{R}$$

$$V_R = I_R R$$

Capacitive load

- Use definition of capacitance


$$q_C = Cv_C = CV_C \sin \omega_d t$$

- Use definition of current and differentiate

$$i_C = \frac{dq_C}{dt} = \omega_d CV_C \cos \omega_d t$$

- Replace cosine term with a phase-shifted sine term

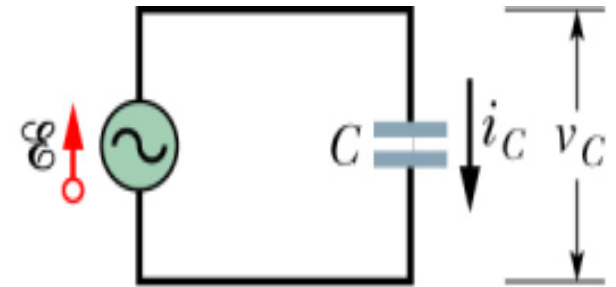
$$\cos \omega_d t = \sin(\omega_d t + 90^\circ)$$



Capacitive load

- Voltage and current relations

$$v_C = V_C \sin \omega_d t$$

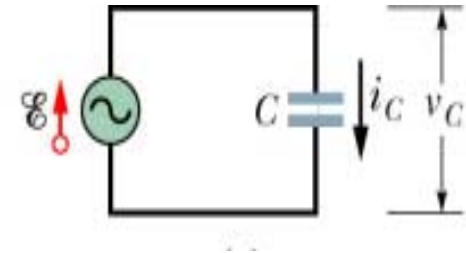

$$i_C = \omega_d C V_C \sin(\omega_d t + 90^\circ) = I_C \sin(\omega_d t + 90^\circ)$$

$$I_C = \frac{V_C}{X_C}$$

$$X_C = \frac{1}{\omega_d C}$$

- X_C is called the **capacitive reactance** and has units of ohms

Capacitive load



- Compare v_C and i_C of capacitor

$$v_C = V_C \sin \omega_d t$$

$$i_C = \omega_d C V_C \sin(\omega_d t + 90^\circ)$$

$$i_R = I_R \sin(\omega_d t - \phi)$$

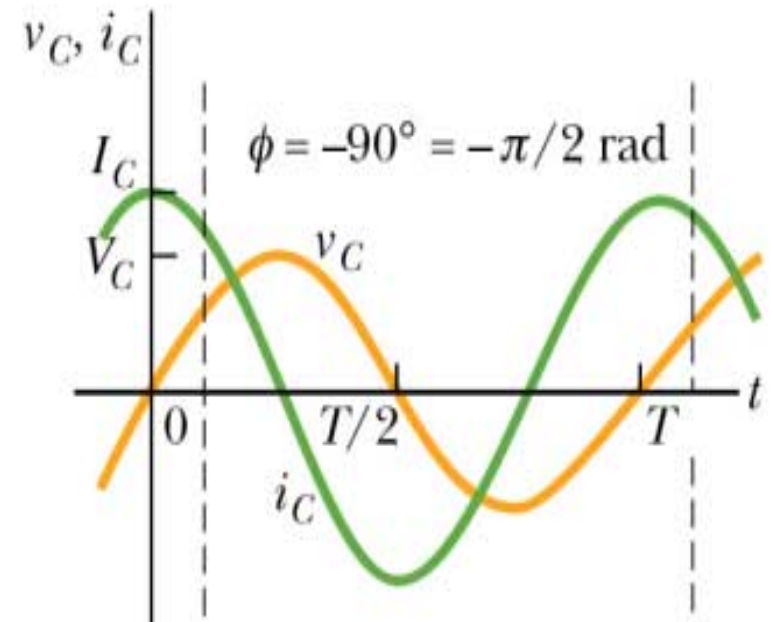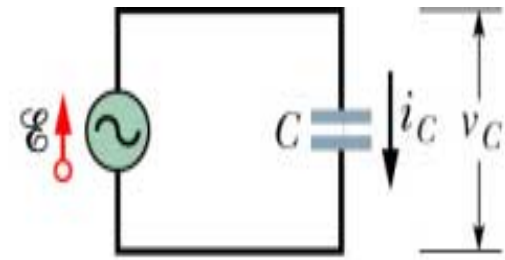
- Voltage and current are out of phase by -90°
- Current leads voltage by $T/4$



Inductive load (skipped in lecture)

- Derivation of current:
- Self-induced emf across an inductor is
- Relate
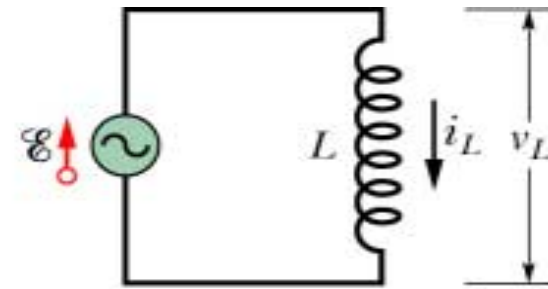
$$\mathcal{E}_L = v_L = L \frac{di}{dt}$$



$$v_L = V_L \sin \omega_d t = L \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{V_L}{L} \sin \omega_d t$$

- Want current so integrate

$$i_L = \frac{V_L}{L} \int \sin(\omega_d t) dt = - \left(\frac{V_L}{\omega_d L} \right) \cos(\omega_d t)$$

- Then use $-\cos(\omega_d t) = \sin(\omega_d t - 90^\circ)$

Inductive load


- Voltage and current relations

$$v_L = V_L \sin \omega_d t$$

$$i_L = \frac{V_L}{\omega_d L} \sin(\omega_d t - 90^\circ) = I_L \sin(\omega_d t - 90^\circ)$$

$$I_L = \frac{V_L}{X_L}$$

$$X_L = \omega_d L$$

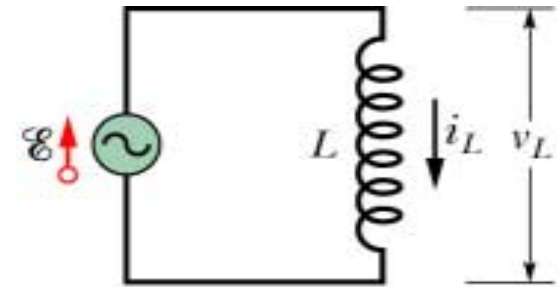


- X_L is called the **inductive reactance** has units of ohms

Inductive load


- Compare v_L and i_L of inductor

$$v_L = V_L \sin \omega_d t$$
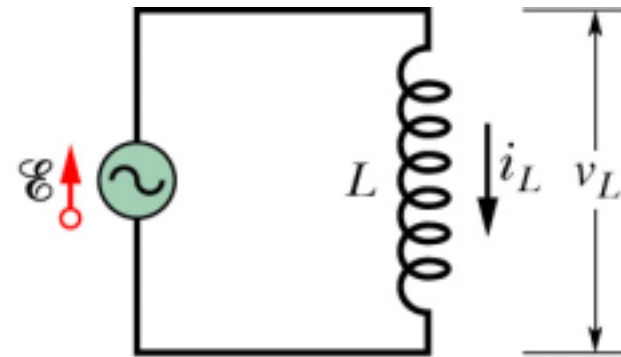
$$i_L = I_L \sin(\omega_d t - 90^\circ)$$



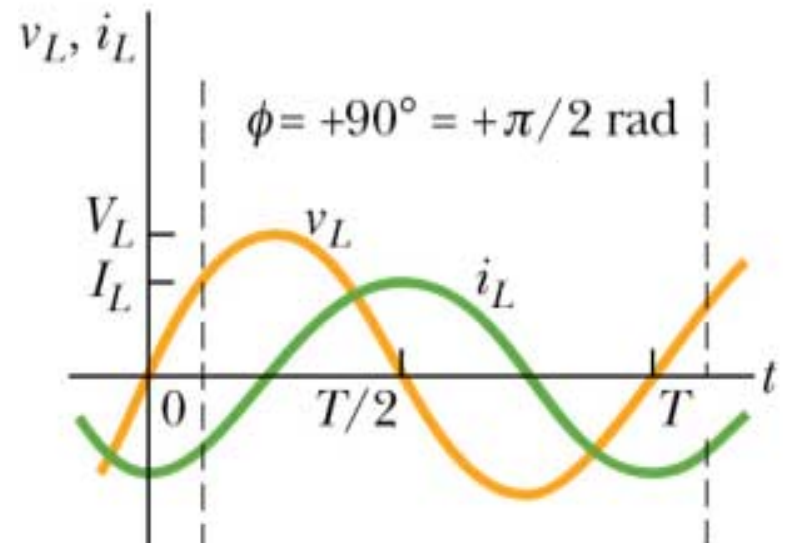- i_L and v_L are $+90^\circ$ out of phase
- Current lags voltage by $T/4$




Summary of Forced Oscillations

Element	Reactance/ Resistance	Phase of Current	Phase angle ϕ	Amplitude Relation
Resistor	R	In phase	0°	$V_R = I_R R$
Capacitor	$X_C = 1/\omega_d C$	Leads v_C (ICE)	-90°	$V_C = I_C X_C$
Inductor	$X_L = \omega_d L$	Lags v_L (ELI)	$+90^\circ$	$V_L = I_L X_L$

- **ELI (positively) is the ICE man**
 - Voltage or emf (E) before current (I) in an inductor (L)
 - Phase constant ϕ is positive for an inductor
 - Current (I) before voltage or emf (E) in capacitor (C)

EM Oscillations

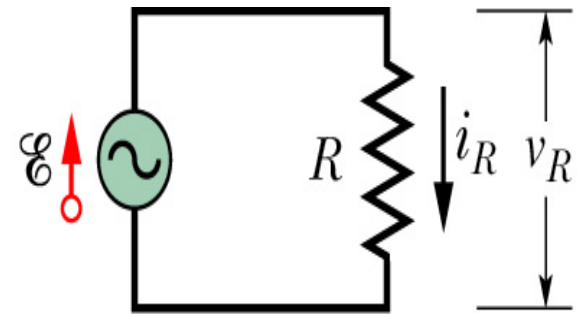- If the driving frequency, ω_d , in a circuit is increased does the amplitude voltage and amplitude current increase, decrease or remain the same?




- For purely resistive circuit
- From loop rule $V_R = \mathcal{E}_m$
- So amplitude voltage, V_L stays the same
- I_R also stays the same -
 I_R only depends on R

$$I_R = \frac{V_R}{R}$$

EM Oscillations

- If the driving frequency, ω_d , in a circuit is increased does the amplitude voltage and amplitude current increase, decrease or remain the same?

- For purely capacitive circuit

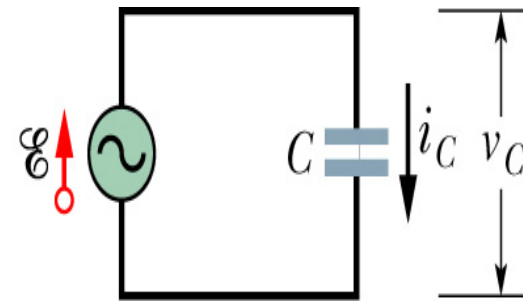


- From loop rule $V_C = \varepsilon_m$
- So amplitude voltage, V_C stays the same
- I_C depends on X_C which depends on ω_d by
- So I_C increases

$$I_C = \frac{V_C}{X_C} = \omega_d C V_C$$

EM Oscillations

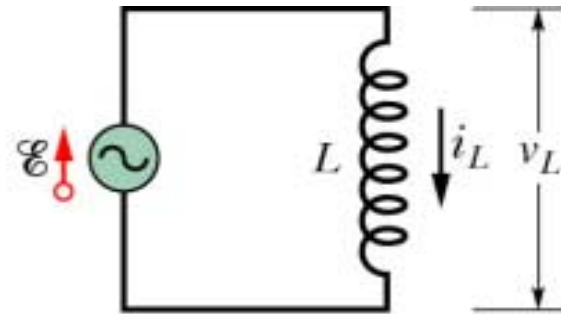- If the driving frequency, ω_d , in a circuit is increased does the amplitude voltage and amplitude current increase, decrease or remain the same?



- For purely inductive circuit
- From loop rule $V_L = \mathcal{E}_m$
- So amplitude voltage, V_L stays the same
- I_L depends on X_L which depends on ω_d by
- So I_L decreases

$$I_L = \frac{V_L}{X_L} = \frac{V_L}{\omega_d L}$$


RLC Circuits

- LC and RLC circuits with no external emf
 - Free oscillations with **natural angular frequency, ω**

$$\omega' = \sqrt{\omega^2 - (R/2L)^2}$$

$$\omega = \sqrt{\frac{1}{LC}}$$

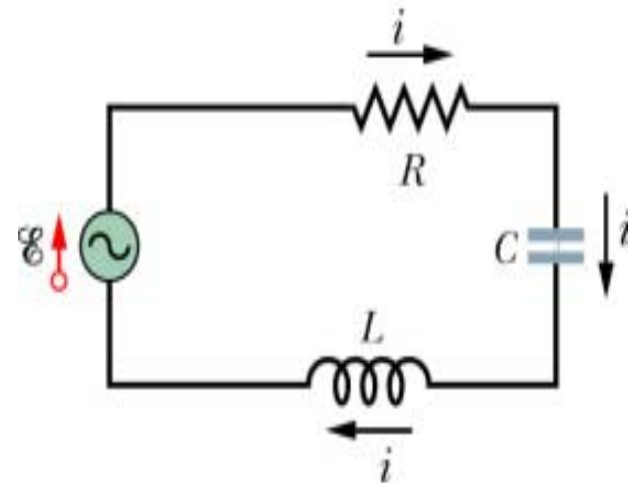
- Add external oscillating emf (e.g. ac generator) to RLC circuit
 - Oscillations said to be **driven or forced**
 - Oscillations occur at **driving angular frequency, ω_d**
 - When **$\omega_d = \omega$, called resonance**, the current amplitude, I , is maximum



RLC circuits

- RLC circuit – resistor, capacitor and inductor in series
- Apply alternating emf
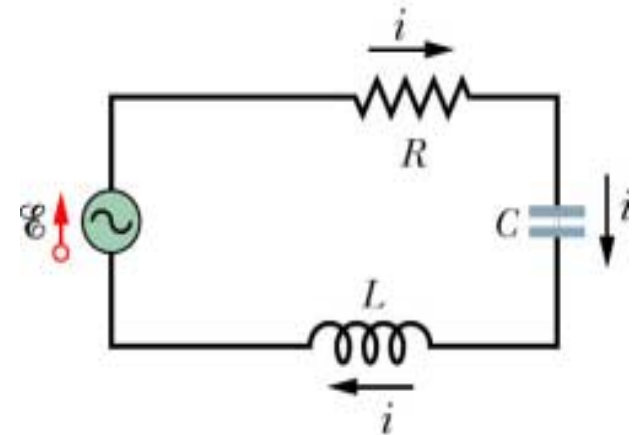
$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t$$



- Elements are in series so same current is driven through each
- From the loop rule, at any time t , the sum of the voltages across the elements must equal the applied emf

$$i = I \sin(\omega_d t - \phi)$$

$$\mathcal{E} = v_R + v_C + v_L$$

RLC circuits

$$\mathcal{E} = iR + iX_C + iX_L$$

- Taking into account the phase find current amplitude to be

$$I = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$

- Write amplitude voltage as

$$\mathcal{E}_m = IZ$$

- Where Z is the **impedance**

- Like resistance and has units of Ohms

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$



$$X_L = \omega_d L$$

$$X_C = \frac{1}{\omega_d C}$$

EM Oscillations

$$\tan \phi = \frac{X_L - X_C}{R}$$

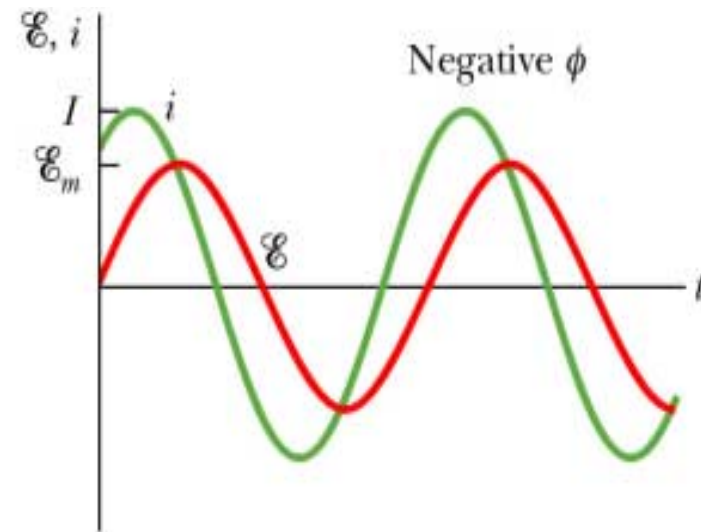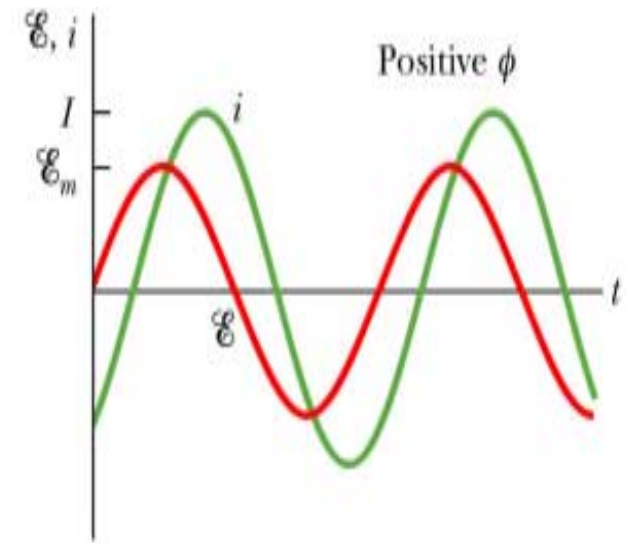
- If $X_L > X_C$ the circuit is more inductive than capacitive
 - ϕ is positive
 - Emf is before current (ELI)
- If $X_L < X_C$ the circuit is more capacitive than inductive
 - ϕ is negative
 - Current is before emf (ICE)



RLC Circuits

$$\tan \phi = \frac{X_L - X_C}{R}$$

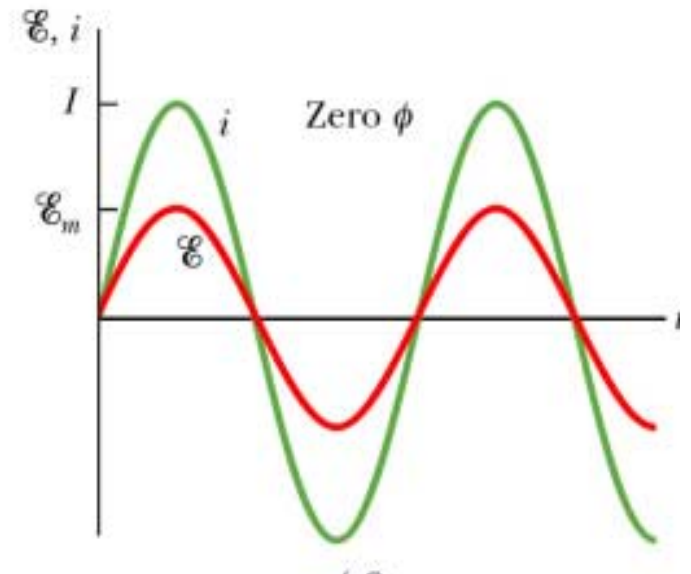- If $X_L = X_C$ the circuit is in **resonance** – emf and current are in phase
- **Current amplitude I is max** when impedance, Z is min



$$I = \frac{\mathcal{E}_m}{Z} = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{\mathcal{E}_m}{R}$$

$$X_L - X_C = 0$$

EM Oscillations

- When $X_L = X_C$ the driving frequency is

$$\omega_d L = \frac{1}{\omega_d C}$$

$$\omega_d = \frac{1}{\sqrt{LC}}$$

- This is the same as the natural frequency, ω

$$\omega_d = \omega = \frac{1}{\sqrt{LC}}$$

- For RLC circuit, resonance and the max current I occurs when $\omega_d = \omega$

RLC circuits

$$I = \frac{E_m}{\sqrt{R^2 + \left(\omega_d L - \frac{1}{\omega_d C} \right)^2}}$$

- I is largest when

$$X_L = X_C$$

- When $\omega_d = \omega$ circuit said to be in **resonance**

- When homework says resonance frequency it means $\omega_d = \omega$

$$\omega = \omega_d = 2\pi f_d$$

