

Problem HH4.10

Design a Schmitt trigger using a 311 comparator (open-collector output) with thresholds at +1.0 volts and +1.5 volts. Use a 1.0k pullup resistor to +5 volts, and assume that the 311 is powered from ± 15 volt supplies.