

## Problem HH 5.2

Show that the circuit in the drawing below is a gyrator, in particular that  $Z_{in} = R^2/Z$ . Hint: you can analyze it as a set of voltage dividers, beginning at the right.

