

Problem HH8.17

Show how to make a 4-input multiplexer using:

- a) Ordinary gates
- b) Gates with 3-state outputs
and
- c) Transmission gates.

Under what circumstances would c) be preferable?