

Problem HH8.8

Using 2-input gates, show how to make:

1. INVERT from NOR
 2. OR from NORs
- and
3. OR from NANDs