



Physics for Scientists & Engineers 2

Spring Semester 2005
Lecture 18

Review



- The resistance R of a device is given by

$$R = \rho \frac{L}{A}$$

- ρ is resistivity of the material from which the device is constructed
- L is the length of the device
- A is the cross sectional area of the device

- The temperature dependence of the resistivity of metals is given by

$$\rho - \rho_0 = \rho_0 \alpha (T - T_0)$$

- ρ is the resistivity at temperature T
- ρ_0 is the resistivity at temperature T_0
- α is the temperature coefficient of electric resistivity for the material under consideration

Review (2)



- The temperature dependence of the resistance of metals is given by


$$R - R_0 = R_0 \alpha (T - T_0)$$

- R is the resistance at temperature T
- R_0 is the resistance at temperature T_0
- α is the temperature coefficient of electric resistivity for the material under consideration

- Ohm's Law for a circuit consisting of a resistor and a battery is given by

$$V_{emf} = iR$$

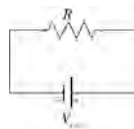
- V_{emf} is the emf or voltage produced by the battery
- i is the current
- R is the resistance of the resistor



Review (3)




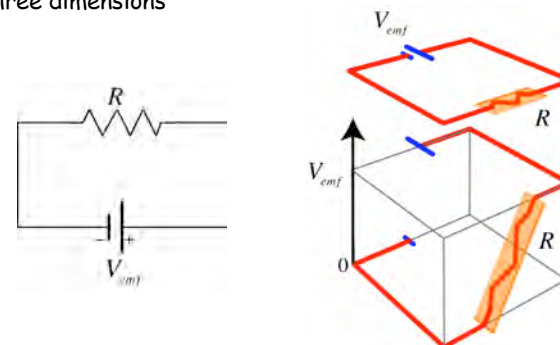- We can visualize a circuit with a battery and a resistor in three dimensions



Resistances in Series

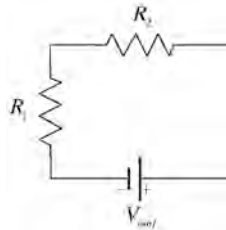- Resistors connected such that all the current in a circuit must flow through each of the resistors are connected in series
- If we connect two resistors R_1 and R_2 in series with one source of emf with voltage V_{emf} , we have the circuit shown below



February 3, 2005


Physics for Scientists&Engineers 2

5

Two Resistors in 3D

- To illustrate the voltage drops in this circuit we can represent the same circuit in three dimensions
- The voltage drop across resistor R_1 is V_1
- The voltage drop across resistor R_2 is V_2
- The sum of the two voltage drops must equal the voltage supplied by the battery

$$V_{emf} = V_1 + V_2$$

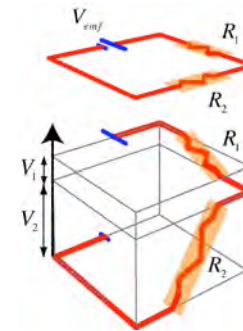

February 3, 2005

Physics for Scientists&Engineers 2

6

Resistors in Series

- The current must flow through all the elements of the circuit so the current flowing through each element of the circuit is the same
- For each resistor we can apply Ohm's Law

$$V_{emf} = iR_1 + iR_2 = iR_{eq}$$

- Where

$$R_{eq} = R_1 + R_2$$

- We can generalize this result for a circuit with two resistors in series to a circuit with n resistors in series

$$R_{eq} = \sum_{i=1}^n R_i$$

February 3, 2005

Physics for Scientists&Engineers 2

7

Example: Internal Resistance of a Battery

- When a battery is not connected in a circuit, the voltage across its terminals is V_f
- When the battery is connected in series with a resistor with resistance R , current i flows through the circuit
- When current is flowing, the voltage, V , across the terminals of the battery is lower than V_f
- This drop occurs because the battery has an internal resistance, R_i , that can be thought of as being series with the external resistor
- We can express this relationship as

$$V_f = iR_{eq} = i(R + R_i)$$

February 3, 2005


Physics for Scientists&Engineers 2

8

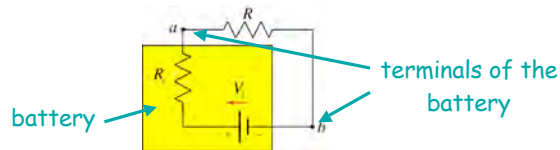Example: Internal Resistance of a Battery (2)



- We can represent the battery, its internal resistance and the external resistance in this circuit diagram



- Consider a battery that has a voltage of 12.0 V when it is not connected to a circuit
- When we connect a 10.0Ω resistor across the terminals, the voltage across the battery drops to 10.9 V
- What is the internal resistance of the battery?

February 3, 2005

Physics for Scientists&Engineers 2

9

Example: Internal Resistance of a Battery (3)



- The current flowing through the external resistor is

$$i = \frac{V}{R} = \frac{10.9 \text{ V}}{10.0 \Omega} = 1.09 \text{ A}$$

- The current flowing in the complete circuit must be the same so

$$V_t = iR_{eq} = i(R + R_i)$$

$$(R + R_i) = \frac{V}{i}$$

$$R_i = \frac{V}{i} - R = \frac{12.0 \text{ V}}{1.09 \text{ A}} - 10.0 \Omega = 1.0 \Omega$$

February 3, 2005


Physics for Scientists&Engineers 2

10

Resistances in Parallel



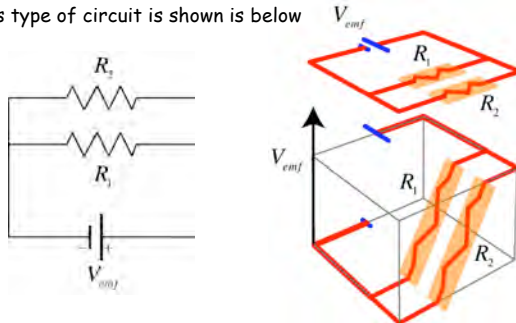- Instead of connecting resistors in series so that all the current must pass through both resistors, we can connect the resistors in **parallel** such that the current is divided between the two resistors
- This type of circuit is shown is below



February 3, 2005

Physics for Scientists&Engineers 2

11

Resistance in Parallel (2)



- In this case the voltage drop across each resistor is equal to the voltage provides by the source of emf
- Using Ohm's Law we can write the current in each resistor

$$i_1 = \frac{V_{emf}}{R_1} \quad i_2 = \frac{V_{emf}}{R_2}$$

- The total current in the circuit must equal the sum of these currents

$$i = i_1 + i_2$$

- Which we can rewrite as

$$i = i_1 + i_2 = \frac{V_{emf}}{R_1} + \frac{V_{emf}}{R_2} = V_{emf} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

February 3, 2005

Physics for Scientists&Engineers 2

12

Resistance in Parallel (3)

- We can then rewrite Ohm's Law as

$$i = V_{emf} \frac{1}{R_{eq}}$$

- Where

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

- We can generalize this result for two parallel resistors to n parallel resistors

$$\frac{1}{R_{eq}} = \sum_{i=1}^n \frac{1}{R_i}$$


February 3, 2005

Physics for Scientists&Engineers 2

13

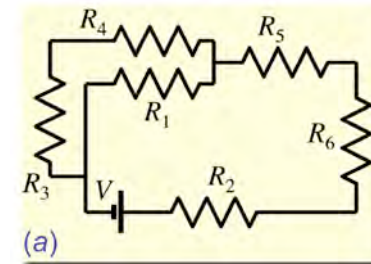Example: Network of Resistors

- Consider a network of resistors as shown below



- What is the current flowing in this circuit?


February 3, 2005

Physics for Scientists&Engineers 2

14


Example: Network of Resistors (2)

- We see that R_3 and R_4 are in series

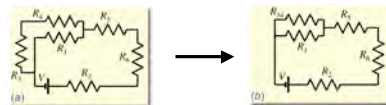

$$R_{34} = R_3 + R_4$$

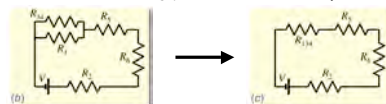- We can see that R_{34} and R_1 are in parallel



$$\frac{1}{R_{134}} = \frac{1}{R_1} + \frac{1}{R_{34}} \quad \text{or} \quad R_{134} = \frac{R_1 R_{34}}{R_1 + R_{34}}$$


February 3, 2005

Physics for Scientists&Engineers 2

15

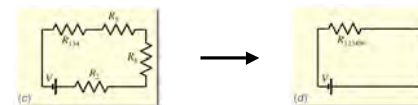Example: Network of Resistors (3)

- We see that R_2 , R_5 , R_6 , and R_{134} are in series



$$R_{123456} = R_2 + R_5 + R_6 + R_{134}$$

$$R_{123456} = R_2 + R_5 + R_6 + \frac{R_1 R_{34}}{R_1 + R_{34}}$$

$$R_{123456} = R_2 + R_5 + R_6 + \frac{R_1 (R_3 + R_4)}{R_1 + R_3 + R_4}$$

$$i = \frac{V_{emf}}{R_{123456}}$$

February 3, 2005

Physics for Scientists&Engineers 2

16

Energy and Power in Electric Circuits



- Consider a simple circuit in which a source of emf with voltage V causes a current i to flow in a circuit
- The work required to move a differential amount of charge dq is equal to the differential electric potential energy dU given by $dU = dqV$
- The definition of current is $i = dq / dt$
- So we can rewrite the differential electric potential energy as $dU = idtV$
- The definition of **power** P is $P = dU / dt$
- Which gives us $P = \frac{dU}{dt} = \frac{idtV}{dt} = iV$

February 3, 2005

Physics for Scientists&Engineers 2

17

Energy and Power



- The power dissipated in a circuit or circuit element is given by the product of the current times the voltage
- Using Ohm's Law we can write equivalent formulations of the power

$$P = iV = i^2R = \frac{V^2}{R}$$

- The unit of power is the watt (W)
- Electrical devices are rated by the amount of power they consume in watts
- Your electricity bill is based on how many kilowatt-hours of electrical energy you consume
- The energy is converted to heat, motion, light, ...

February 3, 2005

Physics for Scientists&Engineers 2

18

Single Loop Circuits



- We have been studying circuits with various networks of resistors but only one source of emf
- Circuits can contain multiple sources of emf as well as multiple resistors
- We begin our study of more complicated circuits by analyzing a circuit with two sources of emf
 - $V_{emf,1}$ and $V_{emf,2}$
- And two resistors
 - R_1 and R_2
- connected in series in a single loop
- We will assume that the two sources of emf have opposite polarity

February 3, 2005


Physics for Scientists&Engineers 2

19

Single Loop Circuits (2)



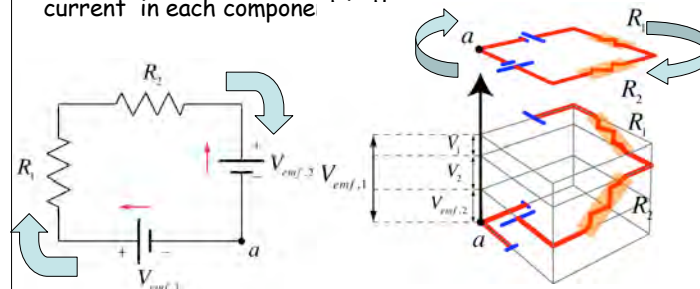- Starting at point a with $V=0$, we proceed around the circuit in a clockwise direction
- Because the components of the circuit are in series, the current in each component is the same



February 3, 2005


Physics for Scientists&Engineers 2

20

Single Loop Circuits (3)



- The first circuit component is a source of emf $V_{emf,1}$, which produces a positive voltage gain of $V_{emf,1}$
- Next we find resistor R_1 , which produces a voltage drop V_1 given by iR_1
- Continuing around the circuit we find resistor R_2 , which produces a voltage drop V_2 given by iR_2
- Next we meet a second source of emf, $V_{emf,2}$
- This source of emf is wired into the circuit with a polarity opposite that of $V_{emf,1}$
- We treat this component as a voltage drop with magnitude of $V_{emf,2}$ rather than a voltage gain
- We now have completed the circuit and we are back at point a

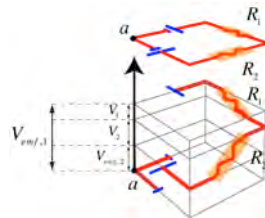

February 3, 2005

Physics for Scientists&Engineers 2

21

Single Loop Circuits (4)



- We can write the analysis of the voltages in this circuit as

$$V_{emf,1} - V_1 - V_2 - V_{emf,2} = V_{emf,1} - iR_1 - iR_2 - V_{emf,2} = 0$$
- We can generalize this result to state that the voltage drops across components in a single loop circuit must sum to zero
- This statement must be qualified with conventions for assigning the sign of the voltage drops around the circuit
- We must define the direction with which we move around the loop and we must define the direction of the current
- If we move around the circuit in the same direction as the current, the voltage drops across resistors will be negative
- If we move around the circuit in the opposite direction from the current, the voltage drops across resistors will be positive

February 3, 2005

Physics for Scientists&Engineers 2

22

Single Loop Circuits (5)



- If we move around the circuit and encounter a source of emf pointing in the same direction, we assume that this component contributes a positive voltage
- If we encounter a source of emf pointing in the opposite direction, we consider that component to contribute a negative voltage
- Thus we will get the same information from the analysis of a simple circuit independent of the direction we choose to analyze the circuit.

February 3, 2005

Physics for Scientists&Engineers 2

23