



Physics for Scientists & Engineers 2

Spring Semester 2005
Lecture 28

Electromagnetic Oscillations



- We have been working with circuits that have
 - a constant current
 - a current that increases to a constant current
 - a current that decreases to zero current
- Now we will introduce circuits that have resistors, capacitors, and inductors as well as time-varying sources of emf
- These types of circuits display different phenomena than the circuits we have been studying, e.g.
 - Resonance
 - Transformers

Energy in Inductors



- Consider a circuit with a resistor R and a capacitor C
 - The current increases or decreases exponentially with a time constant $\tau_C = RC$
- Consider a circuit with an inductor L and a capacitor C
 - The current increases or decreases exponentially with a time constant $\tau_L = L/R$
- Now consider a circuit with an inductor L and a capacitor C
 - We will see that the current and voltage will vary sinusoidally with time
- We call these variations in voltage and current electromagnetic oscillations

Energy in Inductors (2)



- Remember that the energy stored in the electric field of a capacitor with charge q is given by

$$U_E = \frac{1}{2} \frac{q^2}{C}$$

- Remember that the energy stored in the magnetic field of an inductor carrying current i is given by


$$U_B = \frac{1}{2} Li^2$$

- To illustrate electromagnetic oscillations, consider a simple circuit containing a capacitor C and an inductor L

LC Circuit




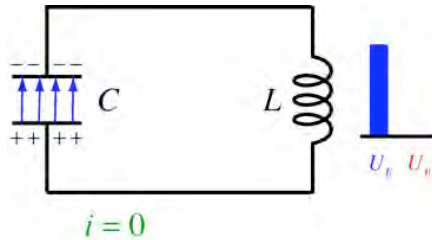- The capacitor is initially fully charged and then connected to the circuit
- The energy in the circuit resides solely in the electric field of the capacitor
- The current is zero



- Now let's follow the evolution with time of the current, charge, magnetic energy, and electric energy in the circuit

LC Circuit Time Evolution

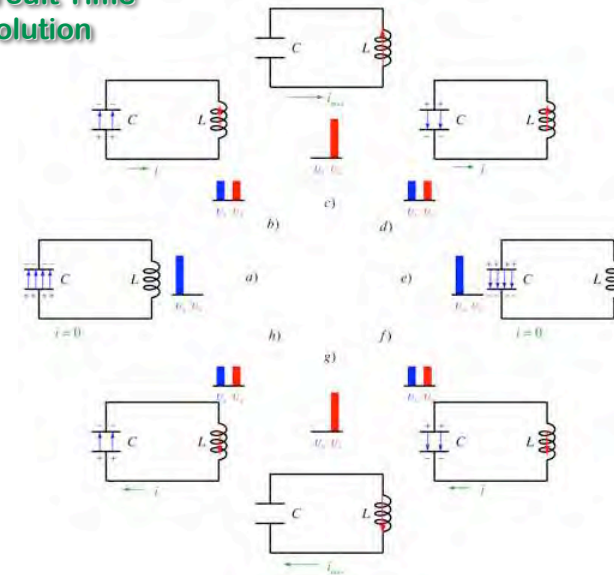


LC Circuits (2)



- The charge on the capacitor varies with time
 - Max positive to zero to max negative to zero back to max positive
- The current in the inductor varies with time
 - Zero to max positive to zero to max negative back to zero
- The energy in the inductor varies with the square of the current and the energy in the capacitor varies with the square of the charge
 - The energies vary between zero and a maximum value

LC Circuits (3)

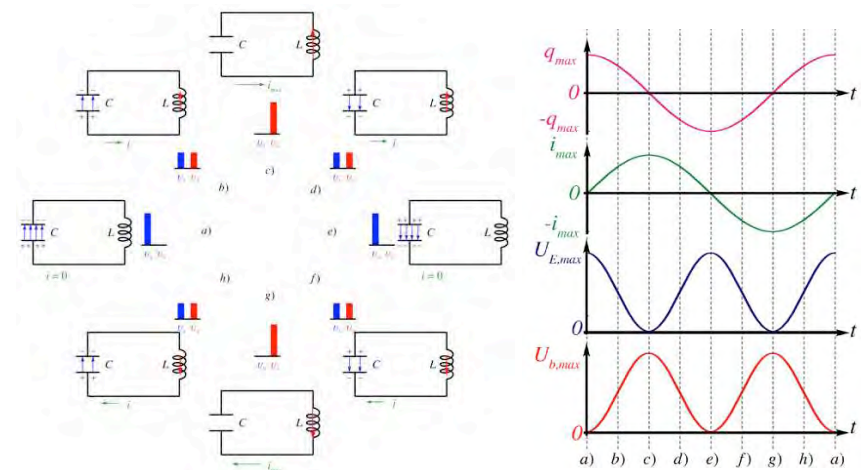

LC Oscillations



- Now we derive a quantitative description of the phenomena we just described qualitatively
- We assume a single loop circuit containing a capacitor C and an inductor L and that there is no resistance in the circuit
- We can write the energy in the circuit U as the sum of the electric energy in the capacitor and the magnetic energy in the inductor

$$U = U_E + U_B$$

- We can re-write the electric and magnetic energies in terms of the charge q and current i

$$U = U_E + U_B = \frac{1}{2} \frac{q^2}{C} + \frac{1}{2} Li^2$$

LC Oscillations (2)



- Because we have assumed that there is no resistance and the electric field and magnetic field are conservative, the energy in the circuit will be constant
- Thus the derivative of the energy in the circuit with respect to time will be zero
- We can then write

$$\frac{dU}{dt} = \frac{d}{dt} \left(\frac{1}{2} \frac{q^2}{C} + \frac{1}{2} Li^2 \right) = \frac{q}{C} \frac{dq}{dt} + Li \frac{di}{dt} = 0$$

- Remembering that $i = dq/dt$ we can write

$$\frac{di}{dt} = \frac{d}{dt} \left(\frac{dq}{dt} \right) = \frac{d^2q}{dt^2}$$

LC Oscillations (3)



- We can then write

$$\frac{q}{C} \frac{dq}{dt} + L \frac{dq}{dt} \frac{d^2q}{dt^2} = \frac{q}{C} + L \frac{d^2q}{dt^2} = 0$$

- Which we can rewrite as

$$\frac{d^2q}{dt^2} + \frac{q}{LC} = 0$$

- This differential equation has the same form as that of simple harmonic motion describing the position x of an object with mass m connected to a spring with spring constant k

$$\frac{d^2x}{dt^2} + \frac{k}{m}x = 0$$

LC Oscillations (4)



- The solution to the differential equation describing simple harmonic motion was

$$x = x_{\max} \cos(\omega_0 t + \phi)$$

- where ϕ is the phase and ω_0 is the angular frequency

$$\omega_0 = \sqrt{\frac{k}{m}}$$

- By analogy we can get the charge as a function of time

$$q = q_{\max} \cos(\omega_0 t + \phi)$$

- where ϕ is the phase and ω_0 is the angular frequency

$$\omega_0 = \sqrt{\frac{1}{LC}} = \frac{1}{\sqrt{LC}}$$

LC Oscillations (5)



- The current is then given by

$$i = \frac{dq}{dt} = \frac{d}{dt} (q_{\max} \cos(\omega_0 t + \phi)) = -\omega_0 q_{\max} \sin(\omega_0 t + \phi)$$

- Realizing that the magnitude of the maximum current in the circuit is given by $\omega_0 q_{\max}$ we get

$$i = -i_{\max} \sin(\omega_0 t + \phi)$$

- Having expression for the charge as a function of time we can write an expression for the electric energy

$$U_E = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} \frac{(q_{\max} \cos(\omega_0 t + \phi))^2}{C} = \frac{q_{\max}^2}{2C} \cos^2(\omega_0 t + \phi)$$

LC Oscillations (6)



- Having expression for the current as a function of time we can write an expression for the magnetic energy

$$U_B = \frac{1}{2} L i^2 = \frac{L}{2} (-i_{\max} \sin(\omega_0 t + \phi))^2 = \frac{L}{2} i_{\max}^2 \sin^2(\omega_0 t + \phi)$$

- Remembering that

$$i_{\max} = \omega_0 q_{\max} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

- We can write

$$\frac{L}{2} i_{\max}^2 = \frac{L}{2} \omega_0^2 q_{\max}^2 = \frac{q_{\max}^2}{2C}$$

LC Oscillations (7)



- Now we can write an expression for the magnetic energy as a function of time

$$U_B = \frac{q_{\max}^2}{2C} \sin^2(\omega_0 t + \phi)$$

- We can write an expression for the energy in the circuit by adding the electric energy and the magnetic energy

$$U = U_E + U_B = \frac{q_{\max}^2}{2C} \cos^2(\omega_0 t + \phi) + \frac{q_{\max}^2}{2C} \sin^2(\omega_0 t + \phi)$$


$$U = \frac{q_{\max}^2}{2C} (\sin^2(\omega_0 t + \phi) + \cos^2(\omega_0 t + \phi)) = \frac{q_{\max}^2}{2C}$$

- Thus the energy in the circuit remains constant with time and is proportional to the square of the original charge put on the capacitor

LC Circuit Example



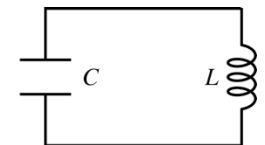- Consider a circuit containing a capacitor $C = 1.50 \mu\text{F}$ and an inductor $L = 3.50 \text{ mH}$. The capacitor is fully charged using a battery with $V_{emf} = 12.0 \text{ V}$ and then connected to the circuit.



- What is the oscillation frequency of the circuit?
- What is the energy stored in the circuit?
- What is the charge on the capacitor after $t = 2.50 \text{ s}$?


LC Circuit Example (2)



- The oscillation frequency of the circuit is given by

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(3.50 \cdot 10^{-3} \text{ H})(1.50 \cdot 10^{-6} \text{ F})}}$$
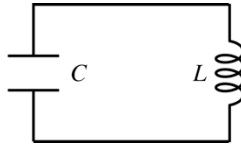
$$\omega_0 = 1.38 \cdot 10^5 \text{ Hz}$$



- The energy stored in the circuit is given by

$$U = \frac{q_{\max}^2}{2C}$$

LC Circuit Example (3)




- The maximum charge on the capacitor is given by

$$q_{\max} = CV_{emf} = (1.50 \cdot 10^{-6} \text{ F})(12.0 \text{ V})$$

$$q_{\max} = 1.80 \cdot 10^{-5} \text{ C}$$
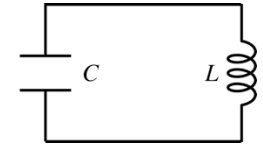
$$U = \frac{q_{\max}^2}{2C} = \frac{(1.80 \cdot 10^{-5} \text{ C})^2}{2 \cdot 1.50 \cdot 10^{-6} \text{ F}} = 1.08 \cdot 10^{-4} \text{ J}$$



LC Circuit Example (4)



- The charge on the capacitor as a function of time is given by

$$q = q_{\max} \cos(\omega_0 t + \phi)$$

$$\text{at } t = 0, q = q_{\max} \Rightarrow \phi = 0$$

$$q = q_{\max} \cos(\omega_0 t)$$

$$q_{\max} = 1.80 \cdot 10^{-5} \text{ C}$$

$$\omega_0 = 1.38 \cdot 10^5 \text{ Hz}$$

at $t = 2.50 \text{ s}$, we have

$$q = (1.80 \cdot 10^{-5} \text{ C}) \cos([1.38 \cdot 10^5 \text{ Hz}][2.50 \text{ s}])$$

$$q = -1.21 \cdot 10^{-5} \text{ C}$$

