

Problem HH 1.5

Show that it is not possible to exceed the power rating of a $\frac{1}{4}$ watt resistor of resistance greater than $1\text{ k}\Omega$, no matter how you connect it, in a circuit operating from a 15 volt battery.