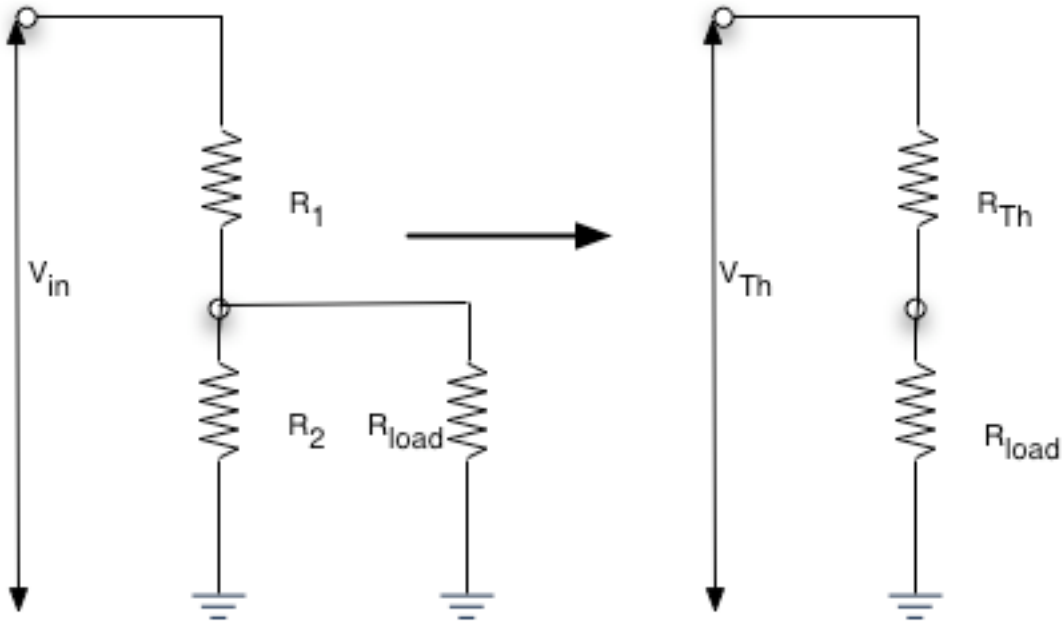


Problem HH 1.9

For the circuit shown in the Figure below, with $V_{in} = 30V$ and $R_1 = R_2 = 10k\Omega$, find:



1. The output voltage with no load attached (this is the open-circuit voltage).
2. The output voltage with a $10k\Omega$ load (treat as voltage divider, with R_2 and R_{load} combined into a single resistor)
3. The Thevenin equivalent circuit.

