

Problem HH 5.1

Show that the circuit in the Figure below is a negative impedance converter (NIC), in particular that $Z_{in} = -Z$. Hint: Apply some input voltage V , and compute the input current I . Then take the ratio to find $Z_{in} = V/I$.

