

Problem HH8.9

Show how to make:

- a) A 3-input AND from 2-input ANDs
- b) A 3-input OR from 2-input ORs
- c) A 3-input NOR from 2-input NORs
and
- d) A 3-input AND from 2-input NANDs