

Problem HH 1.10

Show that setting $R_{\text{load}} = R_{\text{source}}$ in the circuit below, maximizes the power in the load for a given source resistance.

