

Problem HH 1.14

In the circuit below, $R_1 = R_2 = 10\text{k}\Omega$, and $C = 0.1\ \mu\text{F}$. Plot $V_{\text{out}}(t)$ if the input, V_{in} , is a step function of height V_0 at $t = 0$.

