

Problem HH8.17

Show how to make a 4-input multiplexer using:

- a) Ordinary gates
- b) Gates with 3-state outputs and
- c) Transmission gates.

Transmission gates act as logic operated switches. They are usually made out of MOSFETs whose gates are connected to the outputs of logical gates.

Under what circumstances would c) be preferable?