

Problem HH8.32

Draw a state diagram and transition rules for an electronic combination lock: It should open only if four digits are entered in the correct order. Any error in the sequence should reset it and the entry process should proceed from the beginning.