

- (a) Draw a state diagram for a state machine that asserts output whenever a sequence ...101... appears in the input bit stream.
- (b) Produce a transition table for this state machine.
- (c) Design the circuit using JK Flip-flops.