

- (a) Draw a state diagram for a state machine which asserts output whenever the input bit stream has an odd number of 1's.
- (b) Produce a transition table for the state machine in (a).
- (c) Design the state machine using a DFF.
- (d) Design the state machine using a TFF.