

Design a circuit to generate a 20 kHz train of pulses with width proportional to an input voltage in the 0 – 5V range. You may use digital components such as clocks, counters and comparators.