

The circuit below shows a four-bit Digital to Analog Converter (DAC) using an R-2R network. Find the output current,  $I$ , in terms of  $V_{ref}$  and  $R_f$  when the inputs are 0101, as shown.

