

Design a modulo-5 counter that will count up to 4 and then on the 5th pulse resets all flip-flops to zero. Use either toggle or JK flip-flops with CLEAR capability.