

Analyze the operation of the circuit below. Do you know any other circuit that fulfills a similar role? What are the differences and similarities in design and operation? Which circuit might be preferable in practice?

