

A low-pass active filter is supposed to have a low frequency voltage gain $A = |V_{out}/V_{in}| = 100$, an input impedance of $1\text{k}\Omega$ and break-point frequency of 500 Hz . Determine component values for the circuit below to meet these requirements.

