

Use only NAND gates to construct a logic circuit for each of the Boolean functions given below.

(a) $F = A + B$

(b) $F = A \cdot (B + C)$

(c) $F = A \otimes B$