

Combinations of differentiating, integrating, summing etc. amplifiers may be used to solve differential equations. Determine what differential equation yields a solution for $y(t)$ using the circuit below.

