

Design an op-amp based circuit for solving the differential equation:

$$\frac{d^2y}{dt^2} + 3y = \cos(\omega t)$$

Assume that a voltage source $V(t) = 1V \cos(\omega t)$ is available.