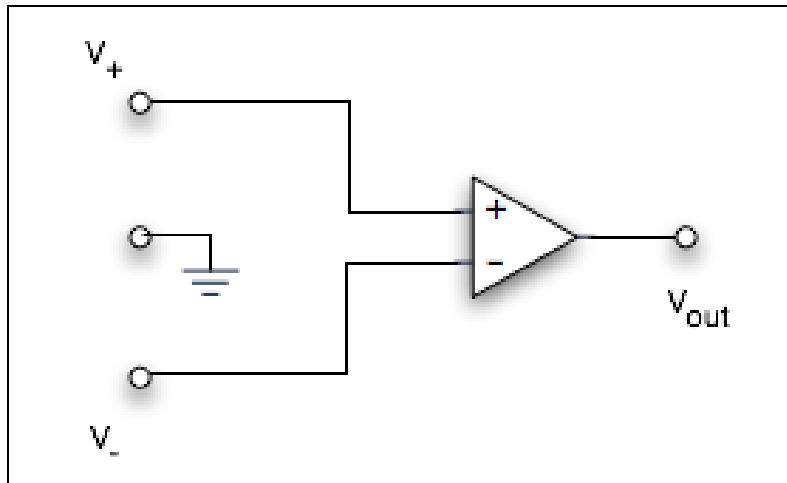


Real operational amplifiers produce an output voltage even when the input voltages are equal (c.f. Diefenderfer and Holton Sec. 9.10) The output voltage in the open-loop configuration shown below may be described in terms of the equation:

$$V_{out} = A(V_+ - V_-) + \frac{A}{CMRR}(V_+ + V_-)$$



CMRR is the Common Mode Rejection Ratio. Given $CMR = 20\log_{10}(CMRR) = 90$ dB and open-loop gain of $A = 2 \times 10^5$ for the 741 op-amp (Diefenderfer and Holton p. D-70), find V_{out} for the differential amplifier shown if $V_1 = 9V$, $V_2 = 9.02$ V, $R = 1k\Omega$ and $R_F = 120$ k Ω . How is V_{out} different from the output for an ideal operational amplifier?

