

Consider the circuit below.

- (a) What is its purpose and why? What is the role of the diode D_1 ?
- (b) Design an opamp circuit without the transistor T_1 that fulfills the same role as the circuit below.
- (c) What advantages does the circuit below have over the circuit without the transistor?

