



Use Kirchoff's laws to write two loop equations for currents I_1 and I_2 .

- Solve these for currents I_1 and I_2 .
- Find the current through and the voltage across the 10Ω resistor.
- Calculate the current through and voltage across the 2Ω resistor.