

Audio amplifiers use transformer coupling between the final amplifier stage and a speaker to match impedances and in order to avoid having the DC current of the final stage flow through the speaker coil. We wish to connect an 8Ω speaker to an $8k\Omega$ amplifier. Calculate the turn ratio of the output transformer.