



For the circuit shown, draw the phasor diagram including all voltages. Assume  $\omega = 100$  rad/s,  $L = 1\text{H}$ ,  $C = 50\ \mu\text{F}$ ,  $R = 100\ \Omega$  and source voltage  $V = 200\ \text{V} \sin\omega t$ .